

5. Design and Analysis of Common Emitter Amplifier

Course: ECE1008 – Electronic Hardware Troubleshooting LAB

-Dr Richards Joe Stanislaus

Assistant Professor - SENSE

Email: 51749@vitstudent.ac.in




VIT[®]

Vellore Institute of Technology
(Deemed to be University under section 3 of UGC Act, 1956)
CHENNAI





1. Voltage Divider Bias

- $V_{BB} =$

 

  
1. Voltage Divider Bias

- $$V_{BB} = V_{CC} \frac{R_2}{R_1 + R_2}$$



 1. Voltage Divider Bias

- $V_{BB} = V_{CC} \frac{R_2}{R_1 + R_2}$
- $V_{EE} =$




1. Voltage Divider Bias

- $V_{BB} = V_{CC} \frac{R_2}{R_1 + R_2}$
- $V_{EE} = V_{BB} - V_{BE}$
- $I_E =$


Silicon: $V_{BE} = 0.7V$

Germanium: $V_{BE} = 0.3V$

 

 
1. Voltage Divider Bias

- $V_{BB} = V_{CC} \frac{R_2}{R_1 + R_2}$
- $V_{EE} = V_{BB} - V_{BE}$
- $I_E = V_{EE} / R_E$
- $I_C \approx$



 
1. Voltage Divider Bias

- $V_{BB} = V_{CC} \frac{R_2}{R_1 + R_2}$
- $V_{EE} = V_{BB} - V_{BE}$
- $I_E = V_{EE} / R_E$
- $I_C \approx I_E$
- $V_C =$



 
1. Voltage Divider Bias

- $V_{BB} = V_{CC} \frac{R_2}{R_1 + R_2}$
- $V_{EE} = V_{BB} - V_{BE}$
- $I_E = V_{EE} / R_E$
- $I_C \approx I_E$
- $V_C = V_{CC} - I_C R_C$
- $V_{CE} =$



 1. Voltage Divider Bias

- $V_{BB} = V_{CC} \frac{R_2}{R_1 + R_2}$
- $V_{EE} = V_{BB} - V_{BE}$
- $I_E = V_{EE} / R_E$
- $I_C \approx I_E$
- $V_C = V_{CC} - I_C R_C$
- $V_{CE} = V_C - V_E$



2. Q point(operating point along load line)



quiescent

- Q point is generally moved by varying R_E :

- $I_E =$



- $V_C =$

- $V_{CE} =$

  

 
 
2. Q point(operating point along load line)

- Q point is generally moved by varying R_E :
- $I_E = V_{EE}/R_E$
- $V_C = V_{CC} - I_C R_C \approx V_{CC} - I_E R_C$
- $V_{CE} = V_C - I_E R_E$



 
 
2. Q point(operating point along load line)

- V_{CC} , R_1 , R_2 and R_C control the saturation current and cutoff voltage.



  2. Q point(operating point along load line)

- V_{CC} , R_1 , R_2 and R_C control the saturation current and cutoff voltage.
- A change in any of the values, results in change in $I_{C(sat)}$ and $V_{CE(cutoff)}$





2. Q point(operating point along load line)

- V_{CC} , R_1 , R_2 and R_C control the saturation current and cutoff voltage.
- A change in any of the values, results in change in $I_{C(sat)}$ and $V_{CE(cutoff)}$
- $V_{CE} = V_C - I_E R_E$



If R_E is too large.
Q point \rightarrow cutoff

  If R_E is too small,
Q point \rightarrow saturation



  2. Q point(operating point along load line)



- For Maximum output signal, Q point is in middle of the Load line



3. Instructions for CE Amplifier design with Voltage Divider Bias

- Circuit is normally biased for V_{CE} to be at midpoint with specified I_C . Follow the steps below:

1) $V_E =$

 
 


3. Instructions for CE Amplifier design with Voltage Divider Bias

- Circuit is normally biased for V_{CE} to be at midpoint with specified I_C . Follow the steps below:

1) $V_E = 0.1V_{CC}$

2) $R_E = V_E / I_E$

  

3. Instructions for CE Amplifier design with Voltage Divider Bias

- Circuit is normally biased for V_{CE} to be at midpoint with specified I_C . Follow the steps below:

1) $V_E = 0.1V_{CC}$



2) $R_E = V_E / I_E$

- 3) For Q point at center,

$$V_{CE} \approx 0.5V_{CC}$$

Remaining voltage across collector: $0.4V_{CC}$

  Collector resistance: $R_C = 0.4V_{CC} / I_C$ ($I_C \approx I_E$)



3. Instructions for CE Amplifier design with Voltage Divider Bias

- Circuit is normally biased for V_{CE} to be at midpoint with specified I_C . Follow the steps below:

1) $V_E = 0.1V_{CC}$

2) $R_E = V_E / I_E$

3) $R_C = 0.4V_{CC} / I_C$ ($I_C \approx I_E$)



4) Stiff voltage divider:

$$R_2 \leq 0.01 \beta_{dc} R_E$$

Firm voltage divider:

$$R_2 \leq 0.1 \beta_{dc} R_E$$

  Note: β_{dc} is current gain: I_C / I_B and is provided by manufacturer



3. Instructions for CE Amplifier design with Voltage Divider Bias

- Circuit is normally biased for V_{CE} to be at midpoint with specified I_C . Follow the steps below:

1) $V_E = 0.1V_{CC}$

2) $R_E = V_E / I_E$

3) $R_C = 0.4V_{CC} / I_C$ ($I_C \approx I_E$)


4) Stiff voltage divider:

$$R_2 \leq 0.01 \beta_{dc} R_E$$


Firm voltage divider:

$$R_2 \leq 0.1 \beta_{dc} R_E$$

5) $R_1 = \frac{V_1}{V_2} R_2$

 

Where β_{dc} : minimum of range

 

4. Task 1.1: Stiff voltage divider

- **Design the VDB circuit for Stiff Voltage divider**


$V_{CC} = 10V$, V_{CE} at midpoint

$$I_C = 10mA$$

Transistor: 2N3904's $\beta_{dc} = 100 - 300$

Find all the resistor values and write it down.

 Note: For this task, No need to simulate in LT Spice.



4. Task 1.2: Firm Voltage divider

- **Design the VDB circuit for Firm Voltage divider**


$V_{CC} = 10V$, V_{CE} at midpoint

$$I_C = 10mA$$

Transistor: 2N3904's $\beta_{dc} = 100 - 300$



Find all the resistor values and write it down.

 Note: For this task, No need to simulate in LT Spice.



  5. Amplifier types



- **Class A operation**: the transistor operates in the active region at all times. This implies that collector current flows for 360° of the ac cycle. With a Class-A amplifier, the designer usually tries to locate the Q point somewhere near the middle of the load line.
- This way, the signal can swing over the maximum possible range without saturating or cutting off the transistor, which would distort the signal.



  5. Amplifier types



Class-B operation

- It means that collector current flows for only half the cycle (180°).
- To have this kind of operation, a designer locates the Q point at cutoff.
- Then, only the positive half-cycle of ac base voltage can produce collector current. This reduces the wasted heat in power transistors.



  5. Amplifier types



- **Class-C operation** means that collector current flows for less than 180° of the ac cycle.
- With Class-C operation, only part of the positive half-cycle of ac base voltage produces collector current.



6. Types of Coupling

Transmits ac voltage to next stage

 
 
- a) Capacitive coupling
- b) Inductive coupling



6. Types of Coupling


Transmits ac voltage to next stage

  - a) Capacitive coupling
- b) Inductive coupling




To transmit both ac and dc:

- a) Direct coupling


 


7. VDB amplifier

 


 
 
7. VDB amplifier: DC load line

- **DC Load line**: When **no ac input**:
Connect points $V_{CE} = V_{CC}$ (Cutoff – Open transistor)
and
 $I_C = \frac{V_{CC}}{R_C + R_E}$ (Saturation – Short transistor)



 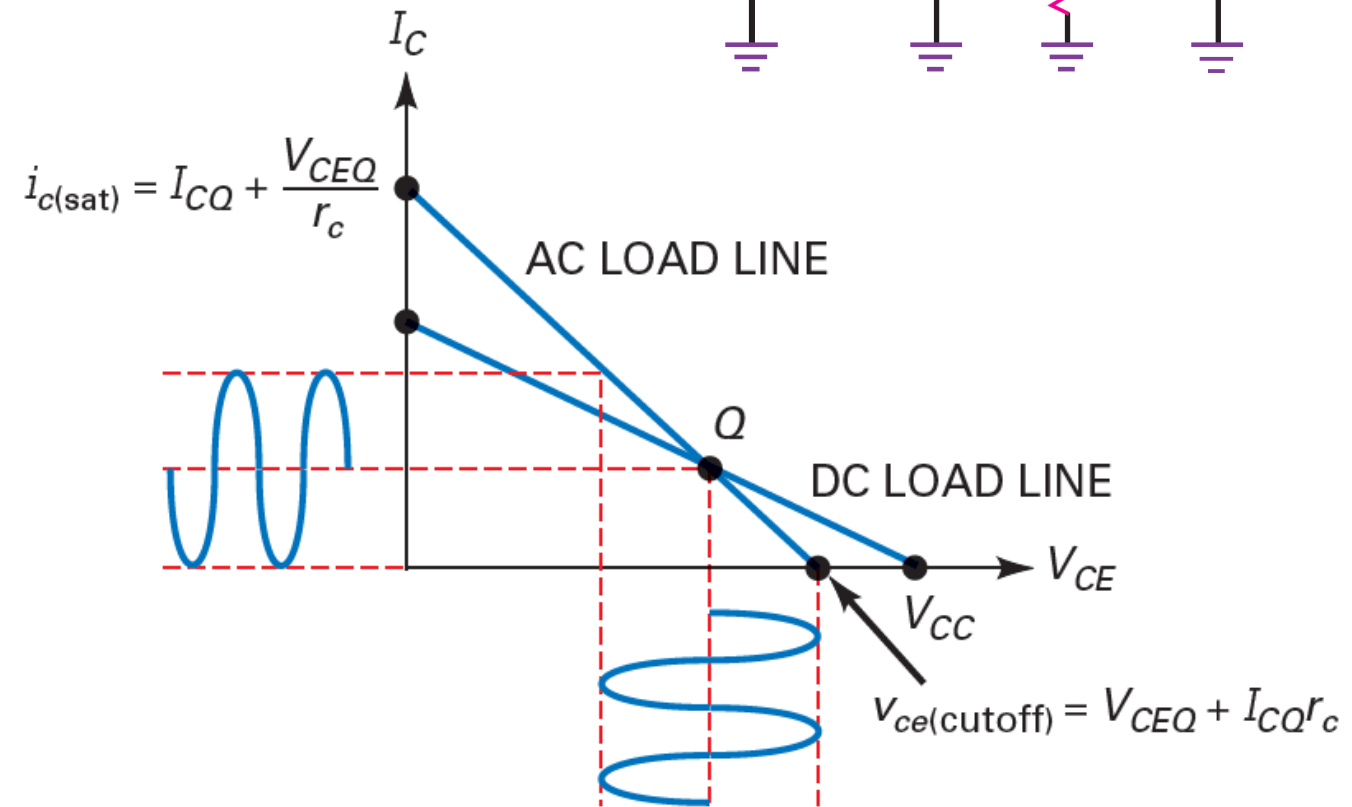 
7. VDB amplifier: AC load line

- AC equivalent and AC Load line:
In the presence of ac.



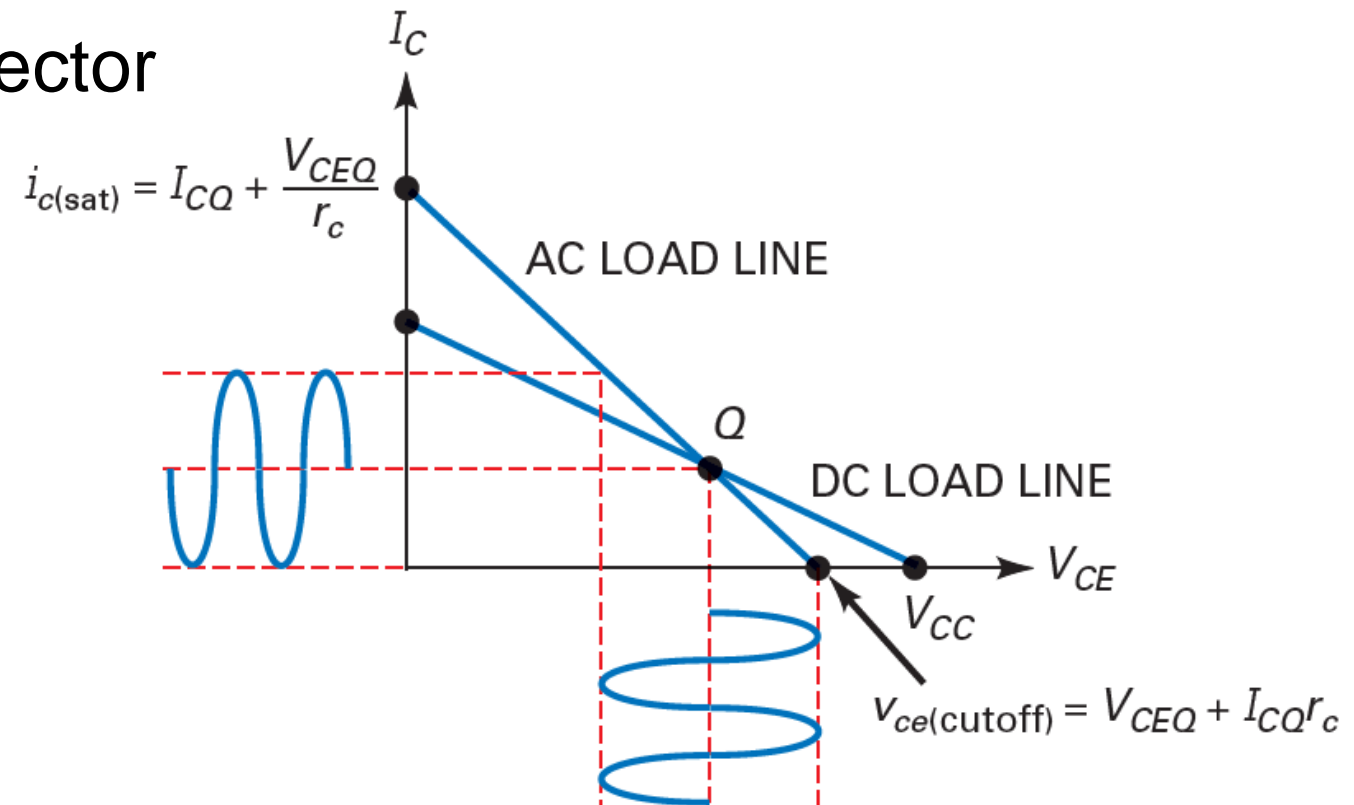
7. VDB amplifier: AC load line

- I_{CQ} = dc collector current
- V_{CEQ} = dc collector-emitter voltage
- r_c = ac resistance seen by collector



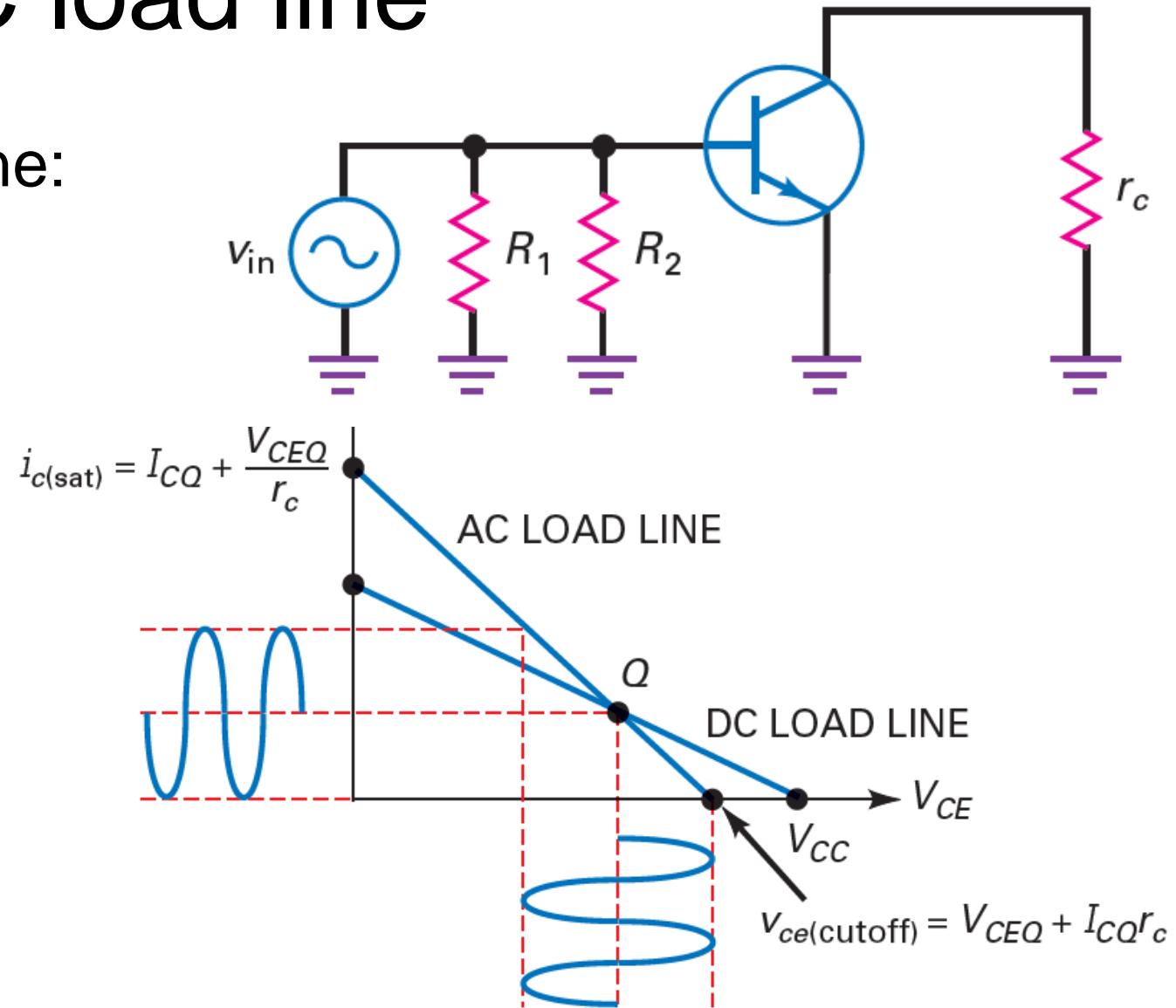
7. VDB amplifier: AC load line

- AC equivalent and AC Load line:
In the presence of ac.



 
7. VDB amplifier: AC load line

- AC equivalent and AC Load line:
In the presence of ac.
- AC Collector current
 $i_c = \Delta I_C = I_C - I_{CQ}$
- AC Collector voltage:
 $v_{ce} = \Delta V_{CE} = V_{CE} - V_{CEQ}$



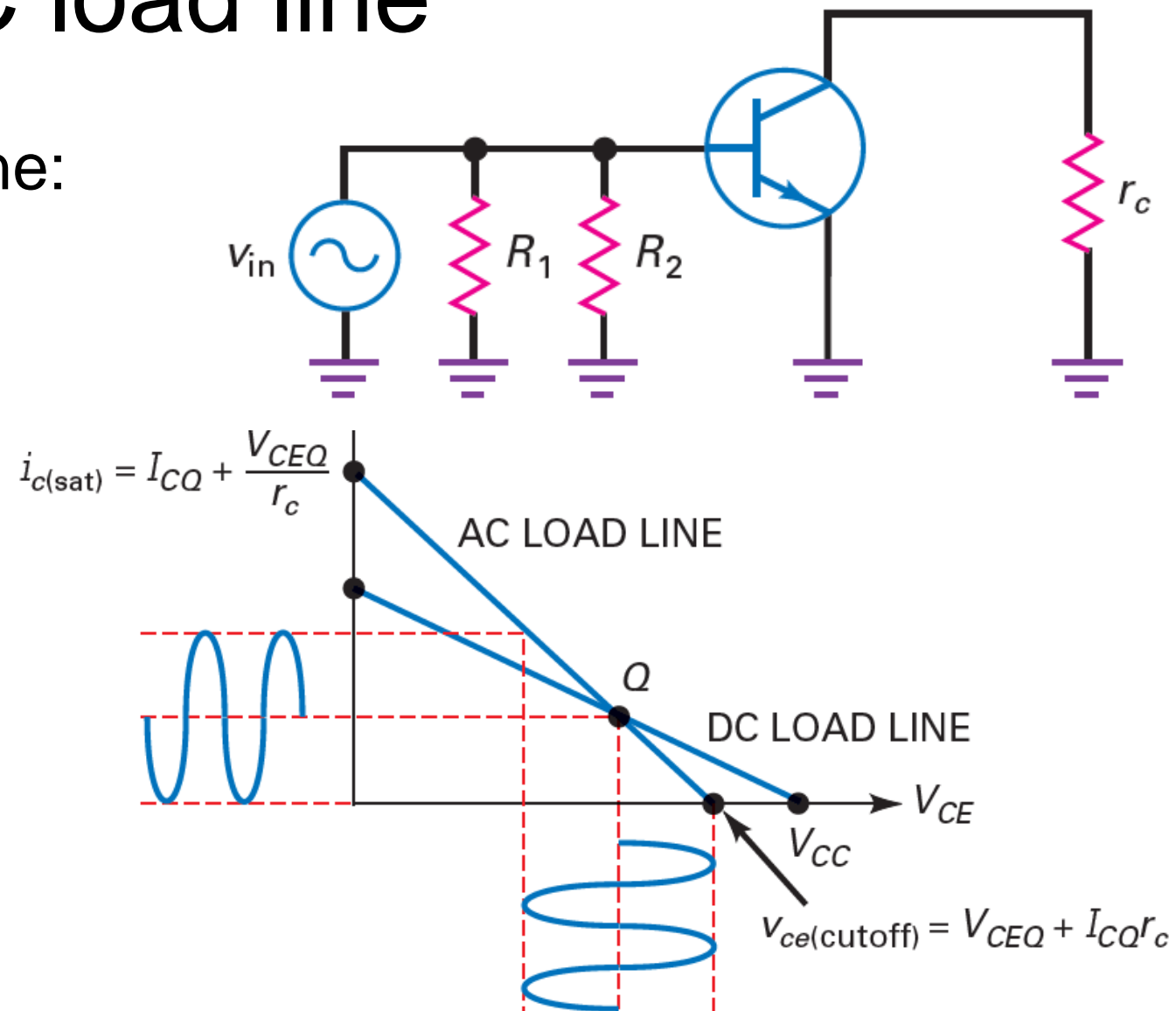7. VDB amplifier: AC load line

- AC equivalent and AC Load line:
In the presence of ac.
- AC Collector current
 $i_c = \Delta I_C = I_C - I_{CQ}$
- AC Collector voltage:
 $v_{ce} = \Delta V_{CE} = V_{CE} - V_{CEQ}$
- $v_{ce} + i_c r_c = 0$
 $i_c = -v_{ce}/r_c$



7. VDB amplifier: AC load line

- AC equivalent and AC Load line:
In the presence of ac.

- Ac Collector current

$$i_c = \Delta I_C = I_C - I_{CQ}$$


- Ac Collector voltage:

$$v_{ce} = \Delta V_{CE} = V_{CE} - V_{CEQ}$$

- $v_{ce} + i_c r_c = 0$

$$i_c = -v_{ce}/r_c$$

 - $I_C = I_{CQ} - \frac{V_{CE}}{r_c} + \frac{V_{CEQ}}{r_c}$




7. VDB amplifier: AC load line

- AC equivalent and AC Load line:
In the presence of ac.

- $I_C = I_{CQ} - \frac{V_{CE}}{r_c} + \frac{V_{CEQ}}{r_c}$

 - At saturation, $V_{CE} = 0$
 $i_{c(sat)} = I_{CQ} + \frac{V_{CEQ}}{r_c}$




7. VDB amplifier: AC load line

- AC equivalent and AC Load line:
In the presence of ac.

- $I_C = I_{CQ} - \frac{V_{CE}}{r_c} + \frac{V_{CEQ}}{r_c}$

- At saturation, $V_{CE} = 0$
 $i_{c(sat)} = I_{CQ} + \frac{V_{CEQ}}{r_c}$

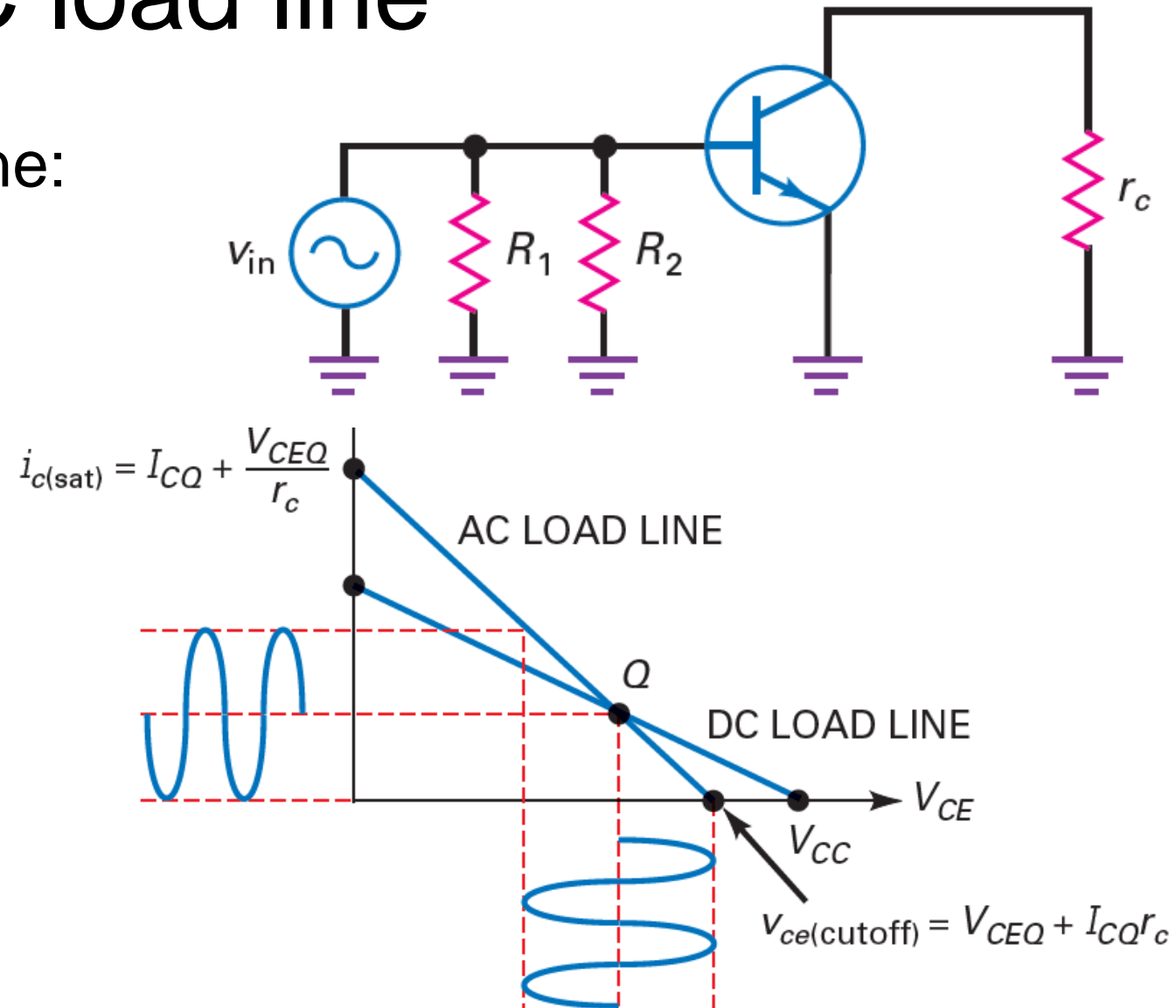- At cutoff, $I_C = 0$
 $v_{ce(cutoff)} = I_{CQ}r_c + V_{CEQ}$



7. VDB amplifier: AC load line

- AC equivalent and AC Load line:
In the presence of ac.

- $I_C = I_{CQ} - \frac{V_{CE}}{r_c} + \frac{V_{CEQ}}{r_c}$


- At saturation, $V_{CE} = 0$

$$i_{c(sat)} = I_{CQ} + \frac{V_{CEQ}}{r_c}$$





- At cutoff, $I_C = 0$

$$v_{ce(cutoff)} = I_{CQ}r_c + V_{CEQ}$$

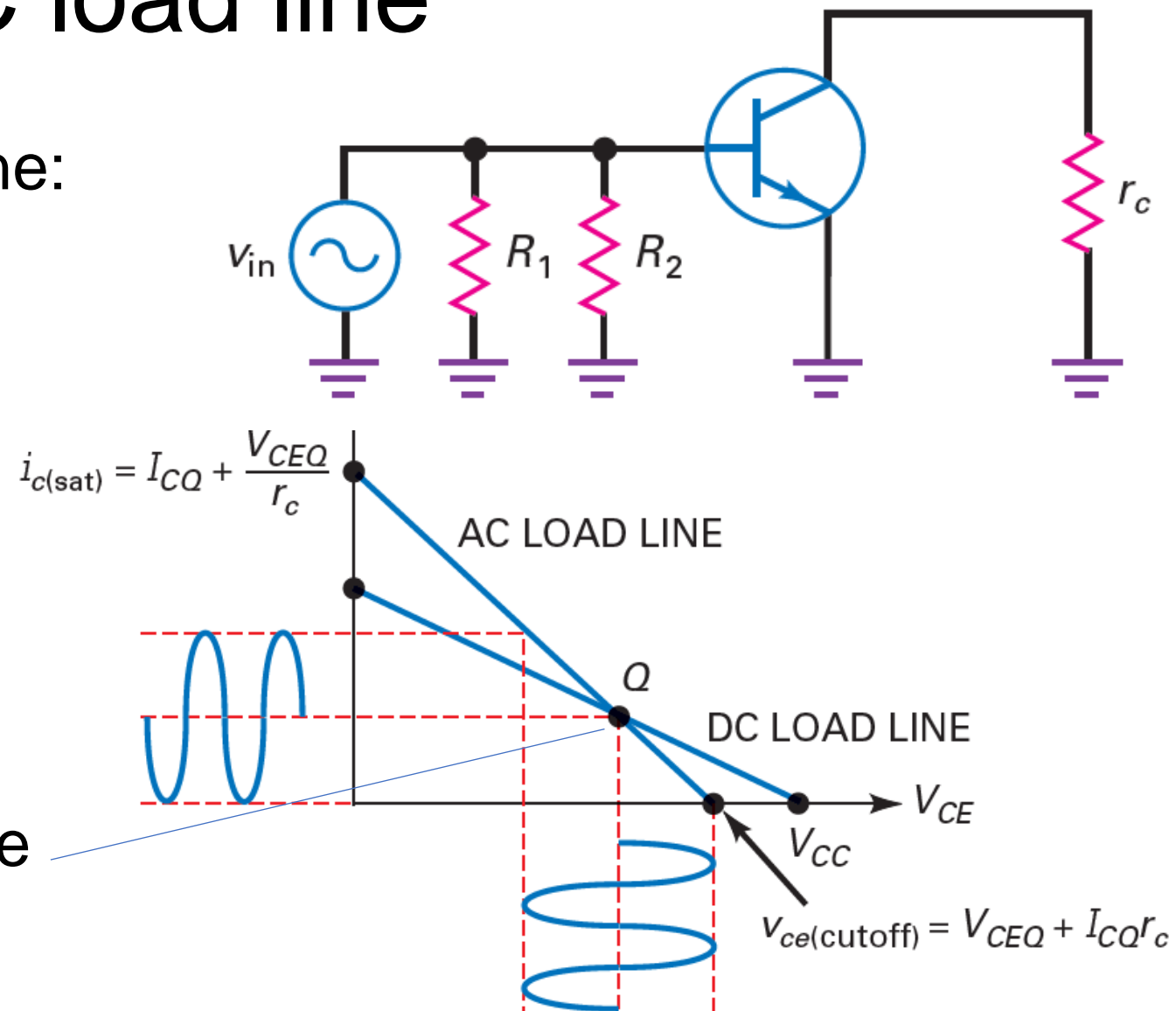- Maximum peak to peak voltage
 $MPP < V_{CC}$






 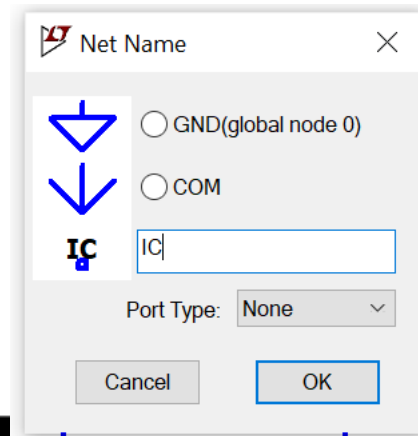  8. Task 2: Operating point of the amplifier



8. Task 2: Operating point of the amplifier

p_analysis]

 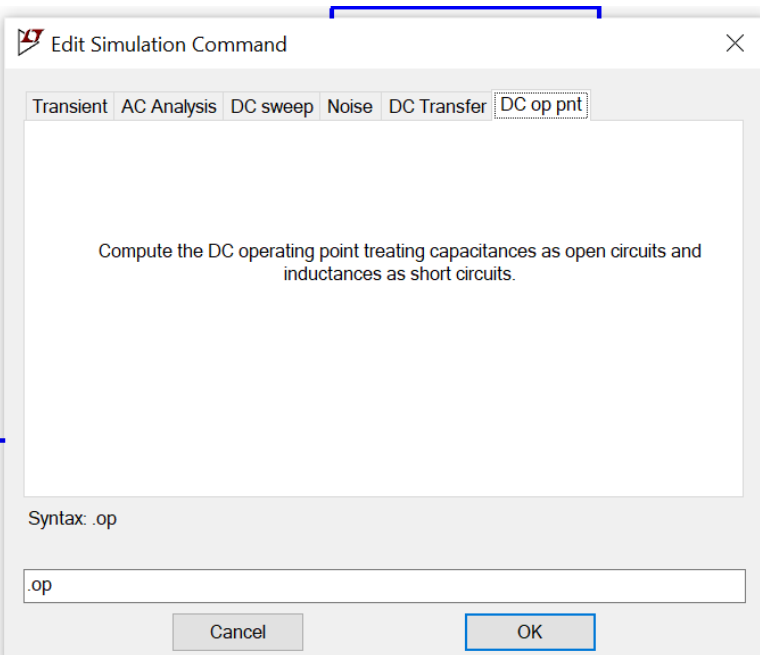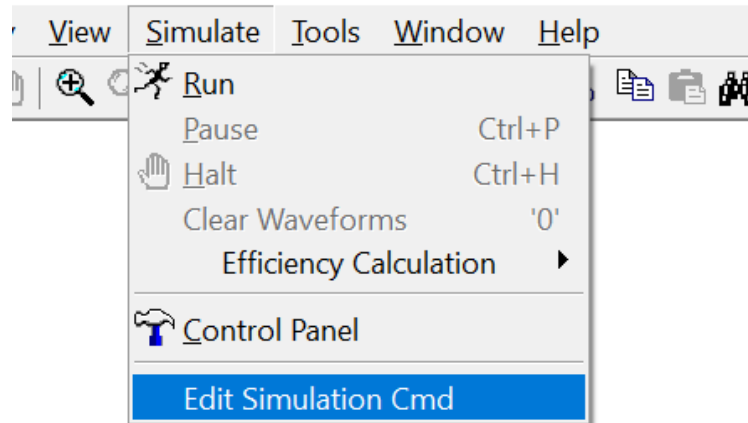

8. Task 2: Operating point of the amplifier

- Click RUN,
- You will find right operating point values


* E:\VIT Data\Academics\2021-22 FALL\ECE1008 EHT\Exp 05\01_dc_op_analysis.asc

--- Operating Point ---


V(ic) :	7.73536	voltage
V(vb) :	1.35665	voltage
V(ve) :	0.728793	voltage
V(n001) :	15	voltage
V(vout) :	7.73536e-013	voltage
V(vin) :	0	voltage
Ic(Q1) :	0.000726464	device_current
Ib(Q1) :	2.3284e-006	device_current
Ie(Q1) :	-0.000728793	device_current
I(C3) :	3.42533e-017	device_current
I(C2) :	1.35665e-017	device_current
I(C1) :	-7.73536e-017	device_current
I(R5) :	7.73536e-017	device_current
I(R4) :	0.000728793	device_current
I(R3) :	0.000411106	device_current
I(R2) :	0.000413435	device_current
I(R1) :	0.000726464	device_current
I(V2) :	1.35665e-017	device_current
I(V1) :	-0.0011399	device_current

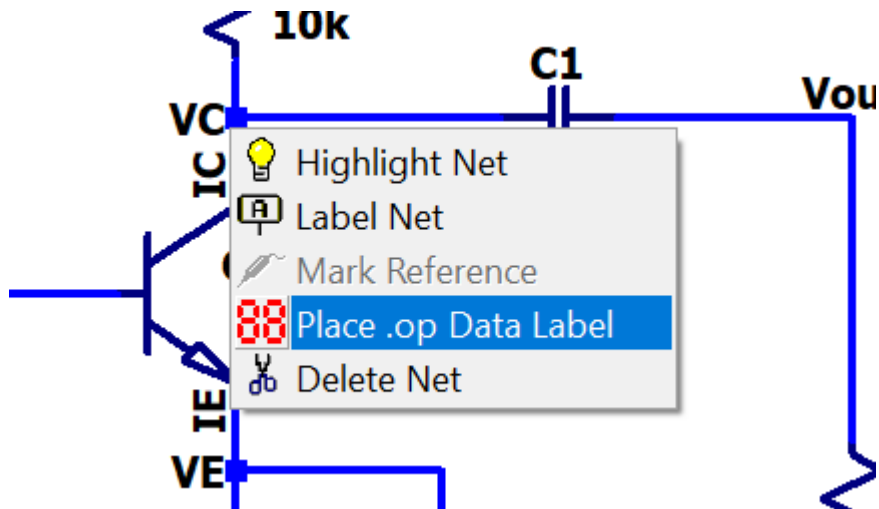8. Task 2: Operating point of the amplifier

- After clicking RUN, right click at Collector wire,





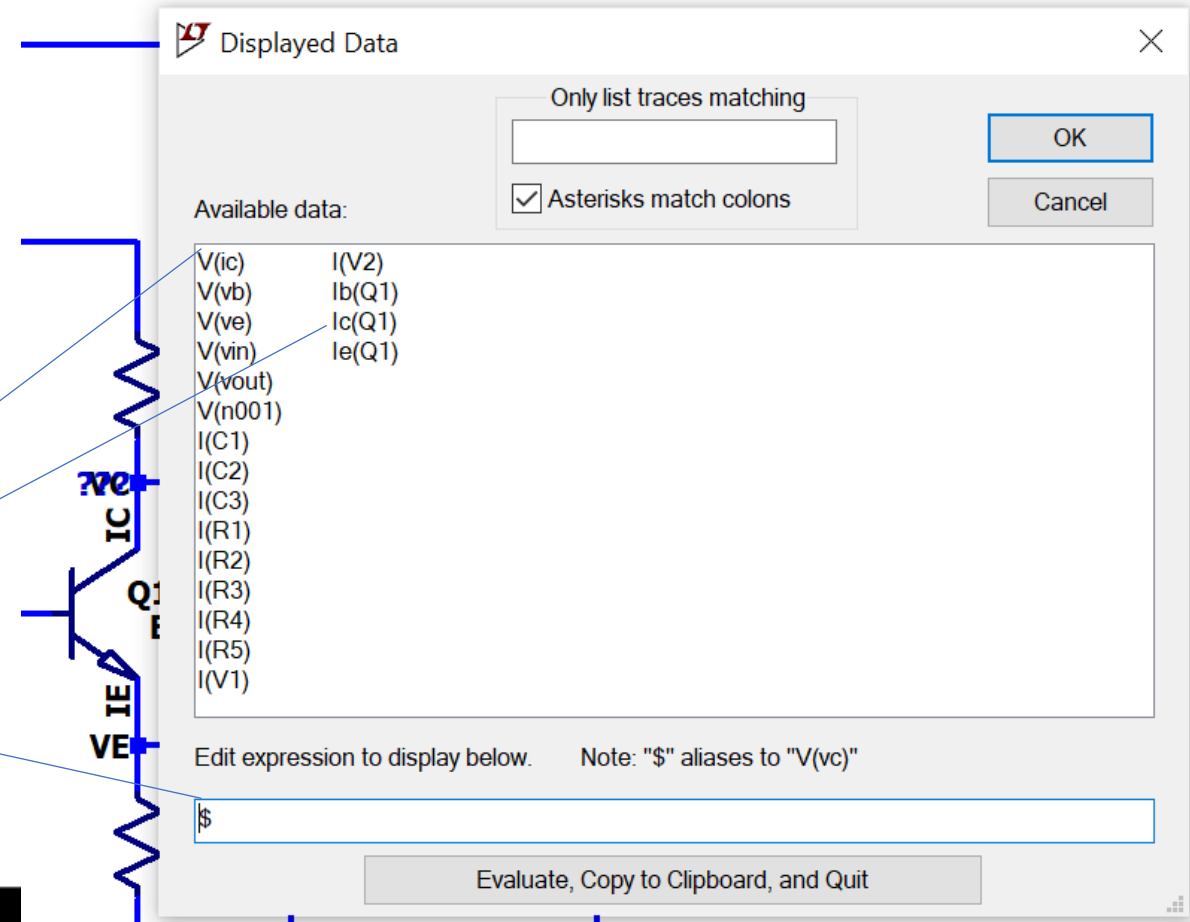- Right click at question marks, Remove "\$" and replace with "V(ic)" or "Ic(Q1)"



 
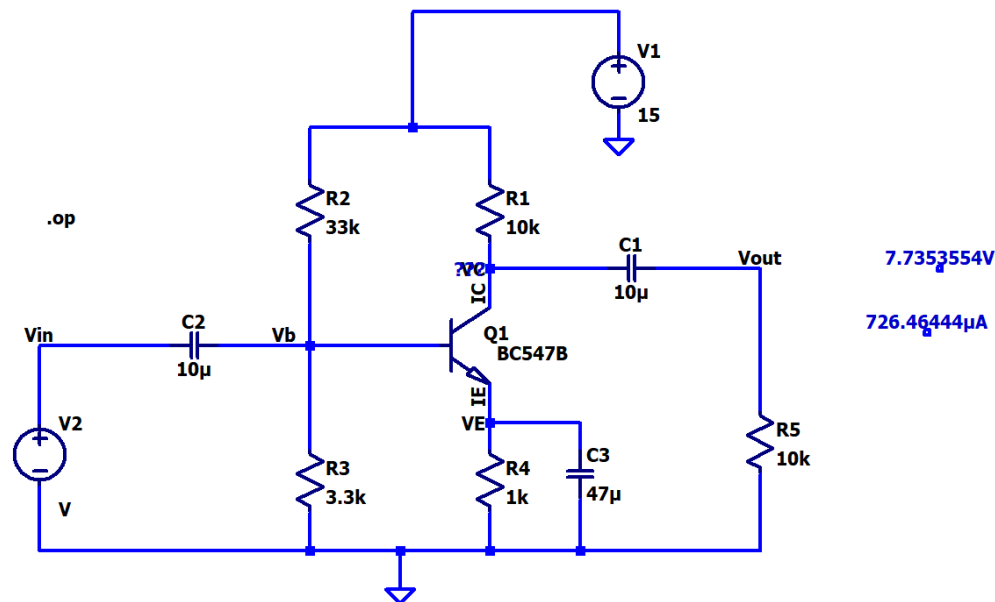
8. Task 2: DC Operating point of the amplifier

- Place the values nearby
- Or move separately the DC operating point



  9. Task 3: AC transient analysis

- Select input voltage source and advanced -> sine wave -> 20mV and 1kHz .op



Independent Voltage Source - V2

Functions

- ☐ (none)
- ☐ PULSE(V1 V2 Tdelay Trise Tfall Ton Period Ncycles)
- ☒ SINE(Voffset Vamp Freq Td Theta Phi Ncycles)
- ☐ EXP(V1 V2 Td1 Tau1 Td2 Tau2)
- ☐ SFFM(Voff Vamp Fcar MD1 Fsig)
- ☐ PWL(t1 v1 t2 v2...)
- ☐ PWL FILE: Browse

DC offset[V]:

Amplitude[V]:

Freq[Hz]:

Tdelay[s]:

Theta[1/s]:

Phi[deg]:

Ncycles:

Additional PWL Points

Make this information visible on schematic: ☒

DC Value

DC value:

Make this information visible on schematic: ☒

Small signal AC analysis(.AC)

AC Amplitude:

AC Phase:

Make this information visible on schematic: ☒

Parasitic Properties

Series Resistance[Ω]:


Parallel Capacitance[F]:

Make this information visible on schematic: ☒


Cancel OK

9. Task 3: AC transient analysis

- For the circuit,

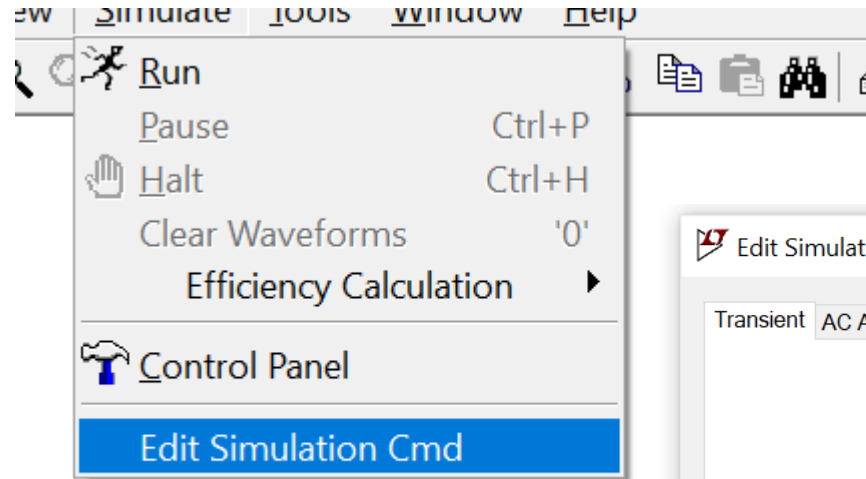


- Delete the .op command

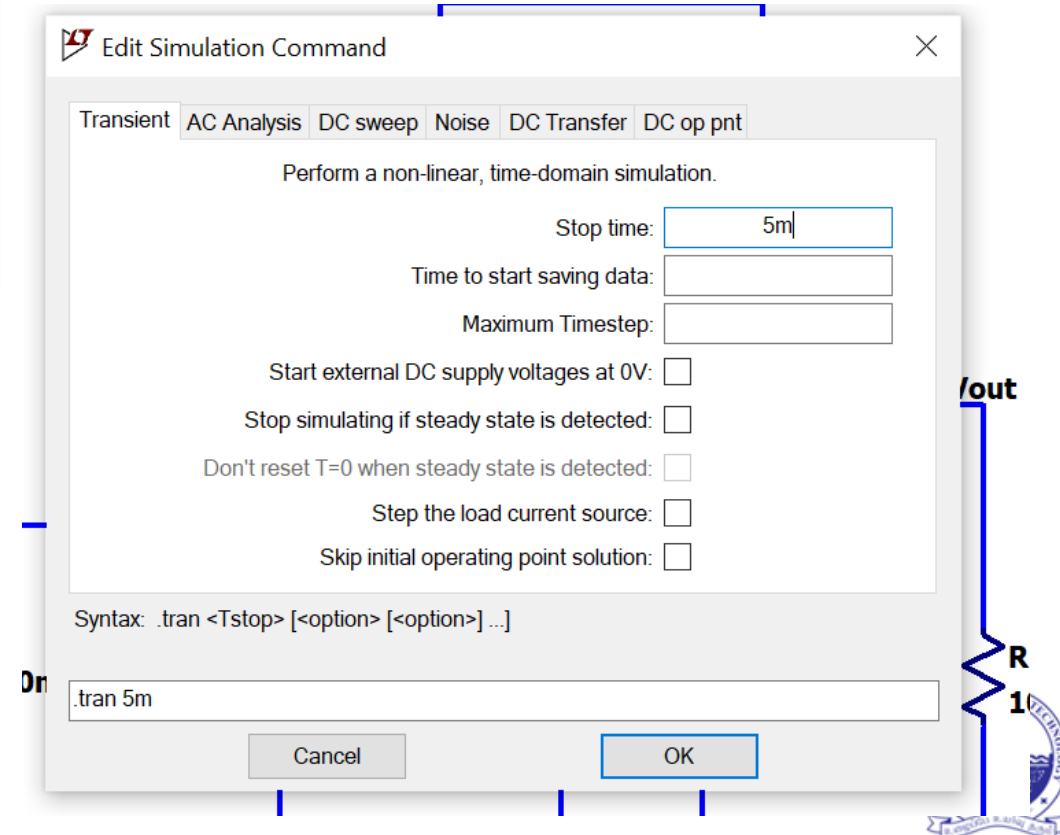


9. Task 3: AC transient analysis

- Plot input and output:

 



10. Task 4: AC Analysis – Frequency sweep

- For the circuit, obtain Bode plot.

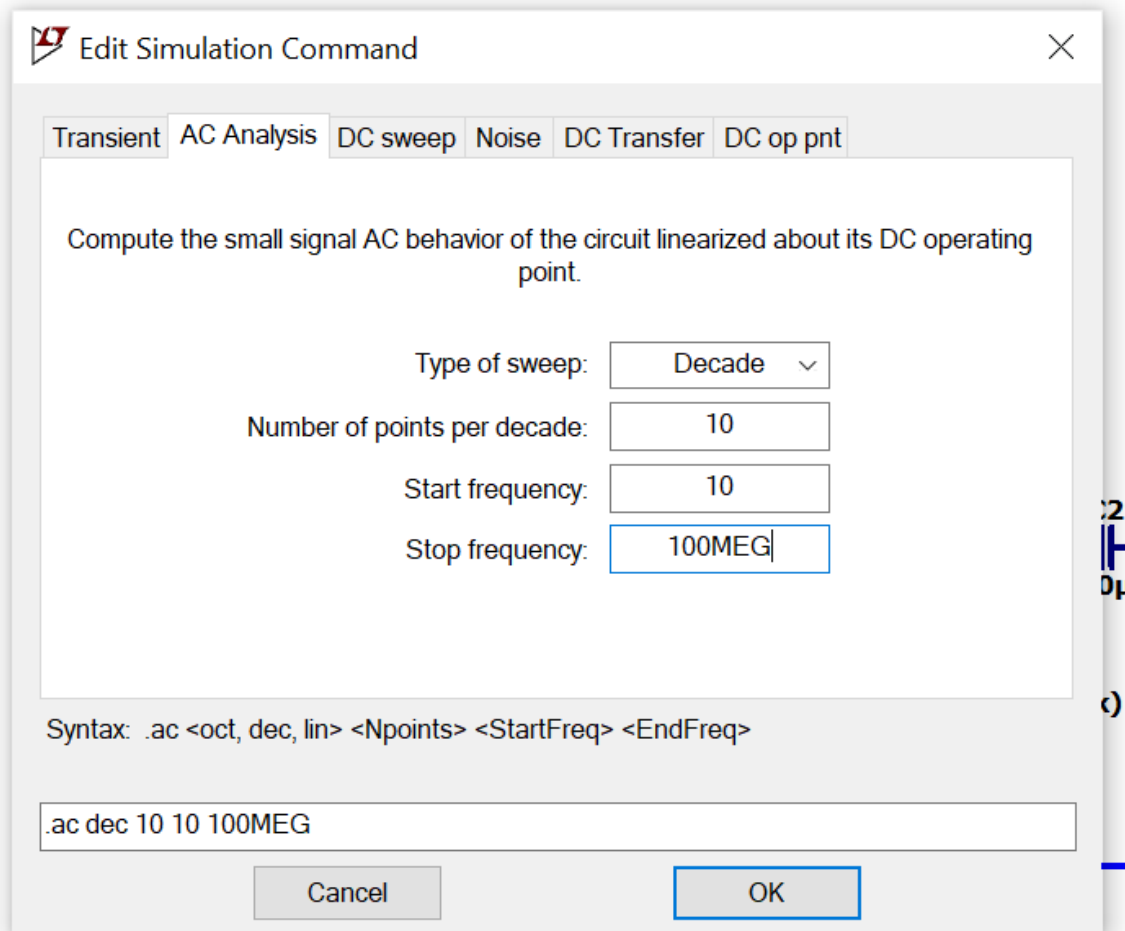


10. Task 4: AC Analysis – Frequency sweep

- Change input voltage source to

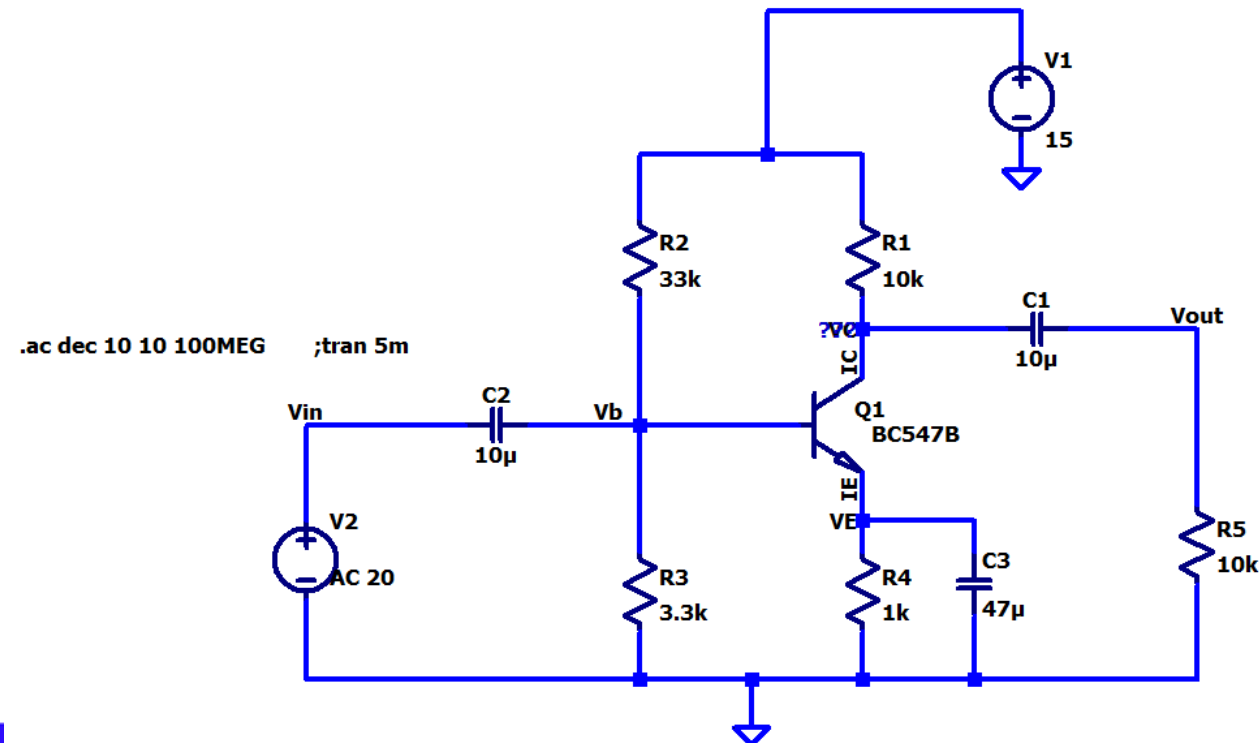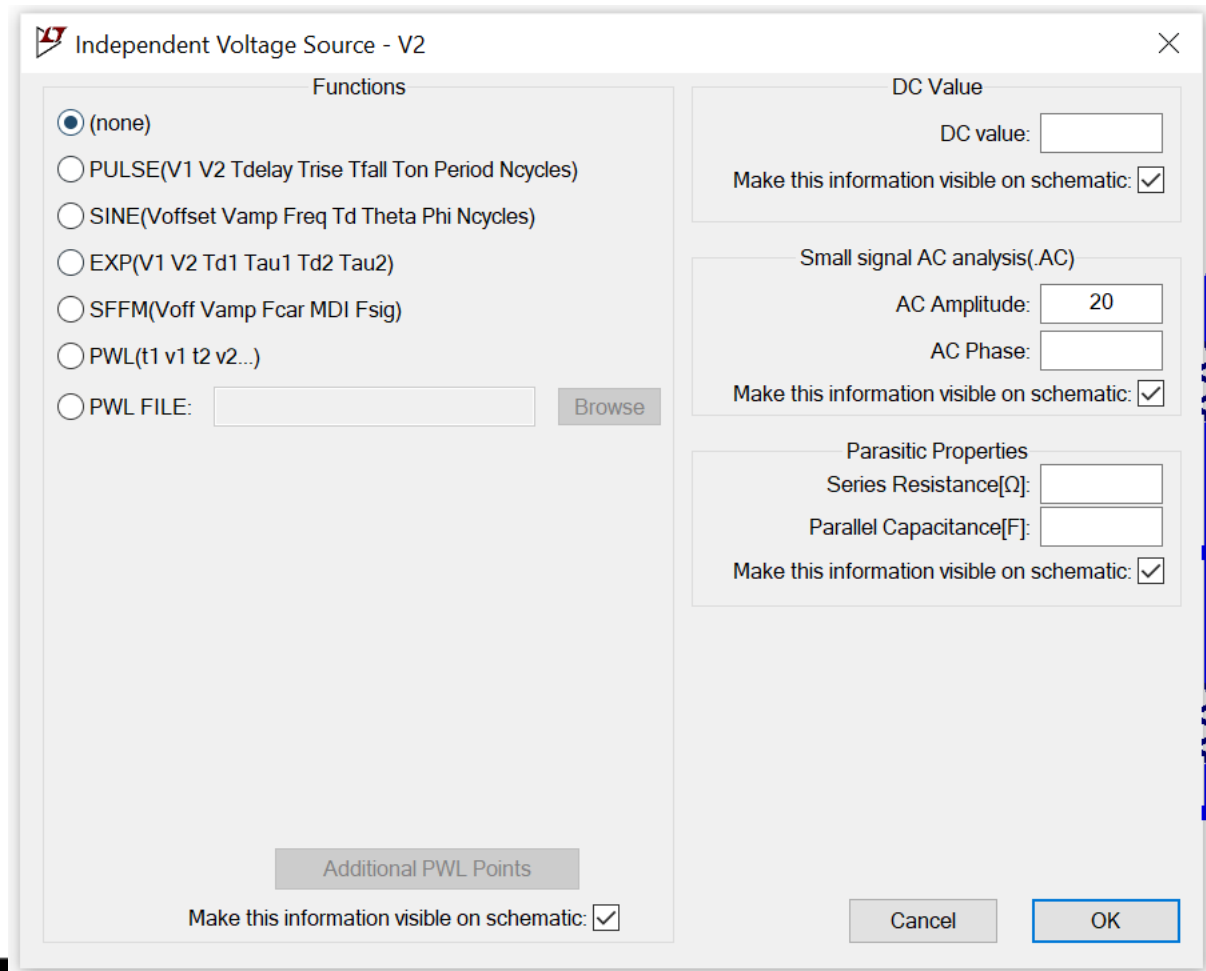

 10. Task 4: AC Analysis – Frequency sweep

- Run and select output
- Left: Magnitude
Right: Phase response.



Important NOTE

- Enter your **registration number** and **Full Name** next to **all your circuits** and the **output plots**.
- Keep the background of circuit and plot as white.



LAB record instructions:

For the lab experiment,

- Write the **Aim**.
- Complete the **Software/Hardware components used**.
- **Obtain the expression for the outputs.**
- Place the respective **circuits in LT Spice**.
- Connect the inputs and outputs. Name them and **write the same in the lab copy(inputs and outputs section)**.
- Use probe in LT spice to plot all possible combinations.
- Write a **concluding statement for each circuit**.
- **Submit** the document's soft copy **on time** in lms.vit.ac.in when available.

