

11. Design and analysis of Emergency Lamp

Course: ECE1008 – Electronic Hardware Troubleshooting LAB

-Dr Richards Joe Stanislaus

Assistant Professor - SENSE

Email: 51749@vitstudent.ac.in



VIT[®]

Vellore Institute of Technology
(Deemed to be University under section 3 of UGC Act, 1956)
CHENNAI



Aim

- To design the an emergency lamp with the following specifications:
Input: 230V 50Hz ac supply
Battery: 4.8V (four 1.2 V batteries connected in series)
2 LEDs (in series): NSCW100 with 5 V breakdown voltage
- S1: The charging has to be controlled with an input power supply switch
- S2: A switch to control the emergency lamp settings.




Design cases:

- S1: The charging has to be controlled with an input power supply switch
- S2: A switch to control the emergency lamp settings.
- Cases:
 - S1 ON: Charging of batteries from power supply and LEDs are OFF.
 - S1 OFF: The charging of batteries stop. Check the switch control of Emergency lamp settings if lamp should be ON or OFF.
 - S1 OFF: S2 OFF: LEDs are OFF
 - S1 OFF: S2 ON: LEDs are ON (take supply from Battery)




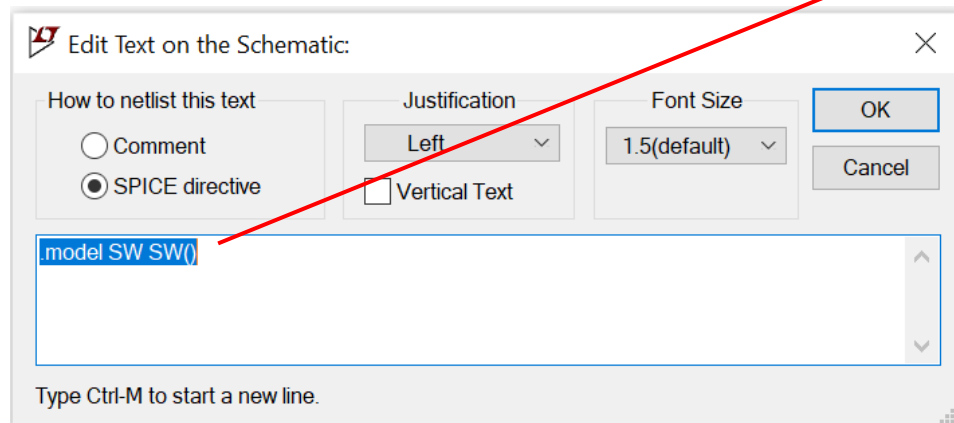Task 1: Design the input Supply unit with switch control

- Design the following circuit and plot the voltage at V1 w.r.t ground.
- For Switch, Go to component library and type SW. Then, in spice directive, enter “.model SW SW()”



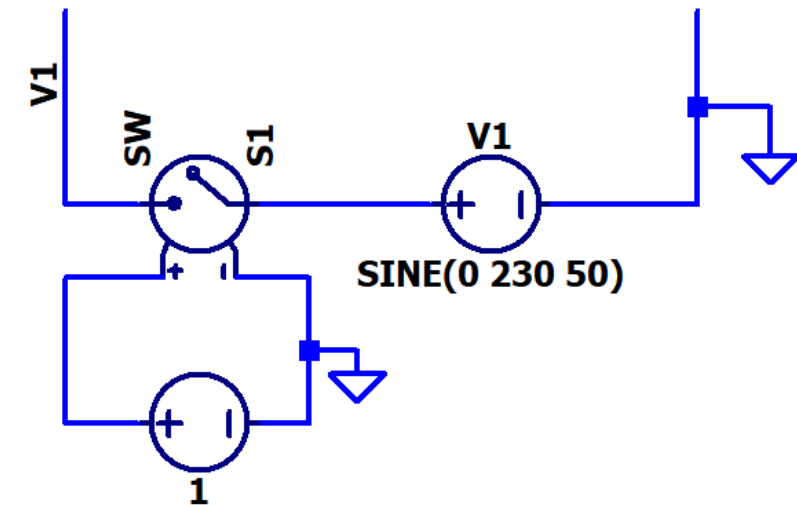
```
.tran 0 30 25 0.1  
.model SW SW()
```



SwitchControl_S1_PowerSupply

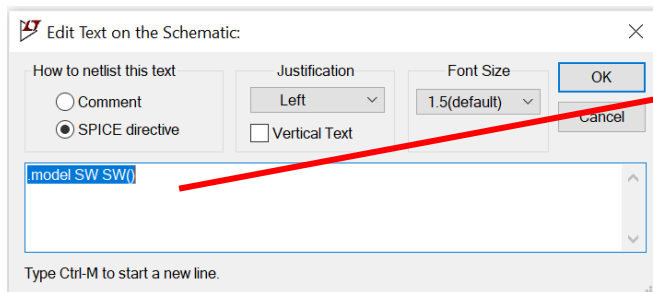
Task 1: Design the input Supply unit with switch control

- Design the following circuit and plot the voltage at V1 w.r.t ground.
- For Switch,
Go to component library and type SW.
Then, in spice directive, enter `".model SW SW()"`



- This power supply is equivalent for controlling the switch.
When 1, S1 will be ON
When 0, S1 will be OFF

```
.tran 0 30 25 0.1
.model SW SW()
```

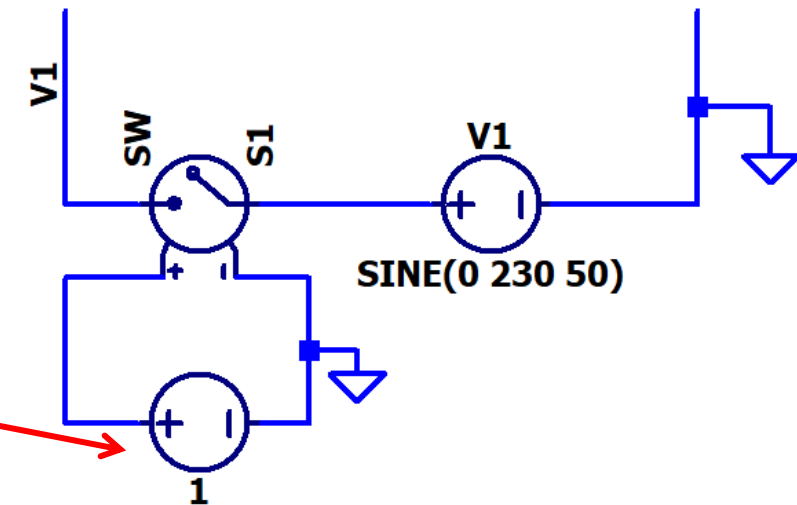


SwitchControl_S1_PowerSupply

Task 2: Design the step down transformer for reduced V2 voltage

- The transformer inductance values are such that $L1=325H$ and $L2=1H$
- Both the coils have **series resistance** of 0.1Ω (Right click at inductor)
- Using Spice directive, enter:
K L1 L2 1
to mention the coupling between coils.


```
.tran 0 30 25 0.1
.model SW SW()
K L1 L2 1
```

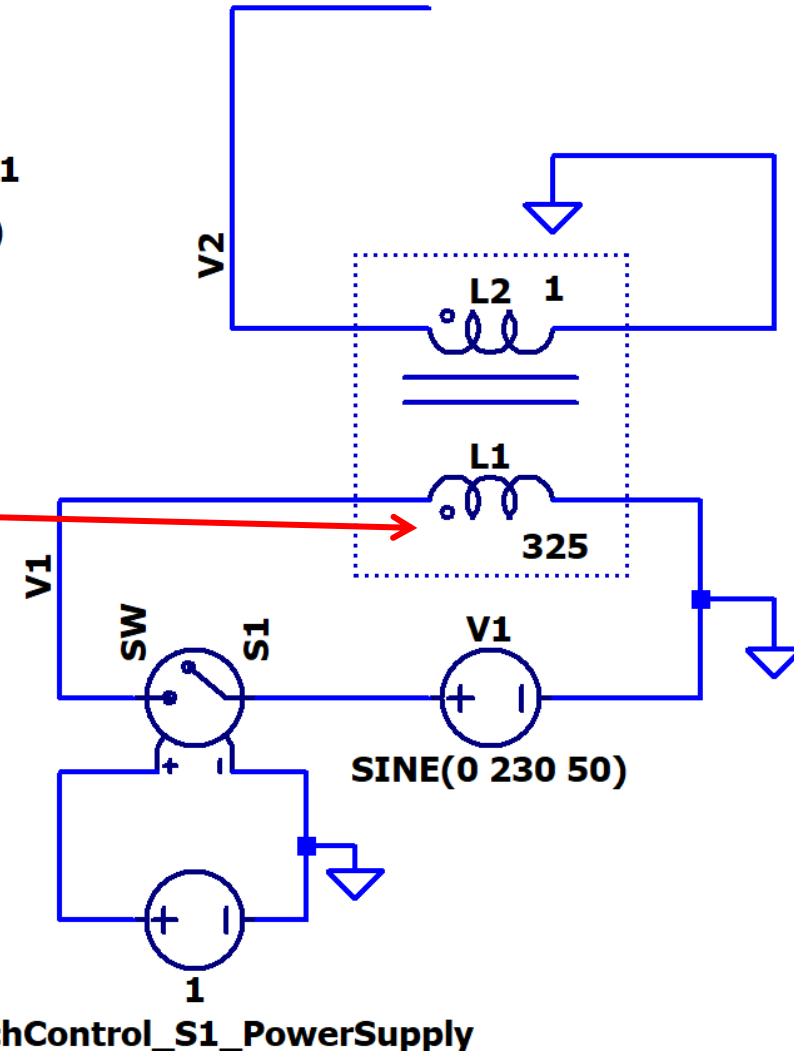

Task 2: Design the step down transformer for reduced V2 voltage

- The transformer inductance values are such that $L1=325H$ and $L2=1H$
- Both the coils have **series resistance** of 0.1Ω (Right click at inductor)
- Using Spice directive, enter:
K L1 L2 1
to mention the coupling between coils.
- Right click on screen, to draw two lines and box
- **Plot the voltage at V2 (stepped down voltage)**

```
.tran 0 30 25 0.1
.model SW SW()
K L1 L2 1
```

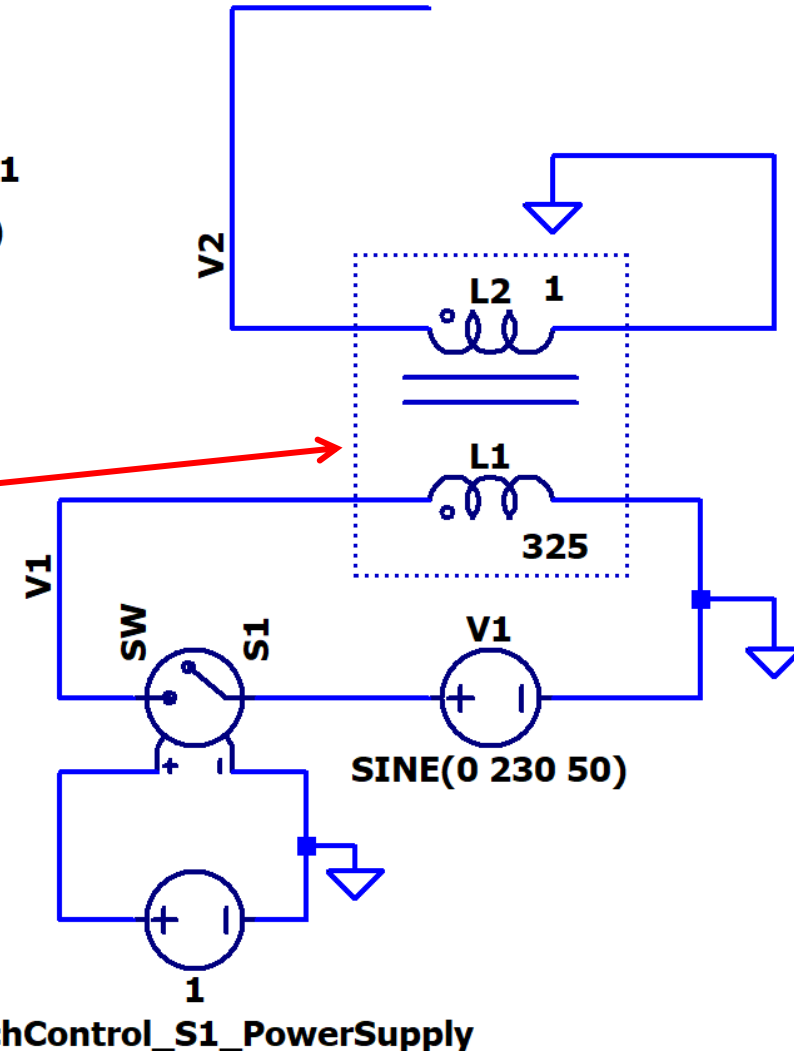


Task 3: Design of Bridge rectifier circuit (without Capacitor)

- Design the bridge rectifier circuit

Note: After placing diodes, right click and select 1N4148 diode.


- Plot the voltage at VDC (without capacitor across load)

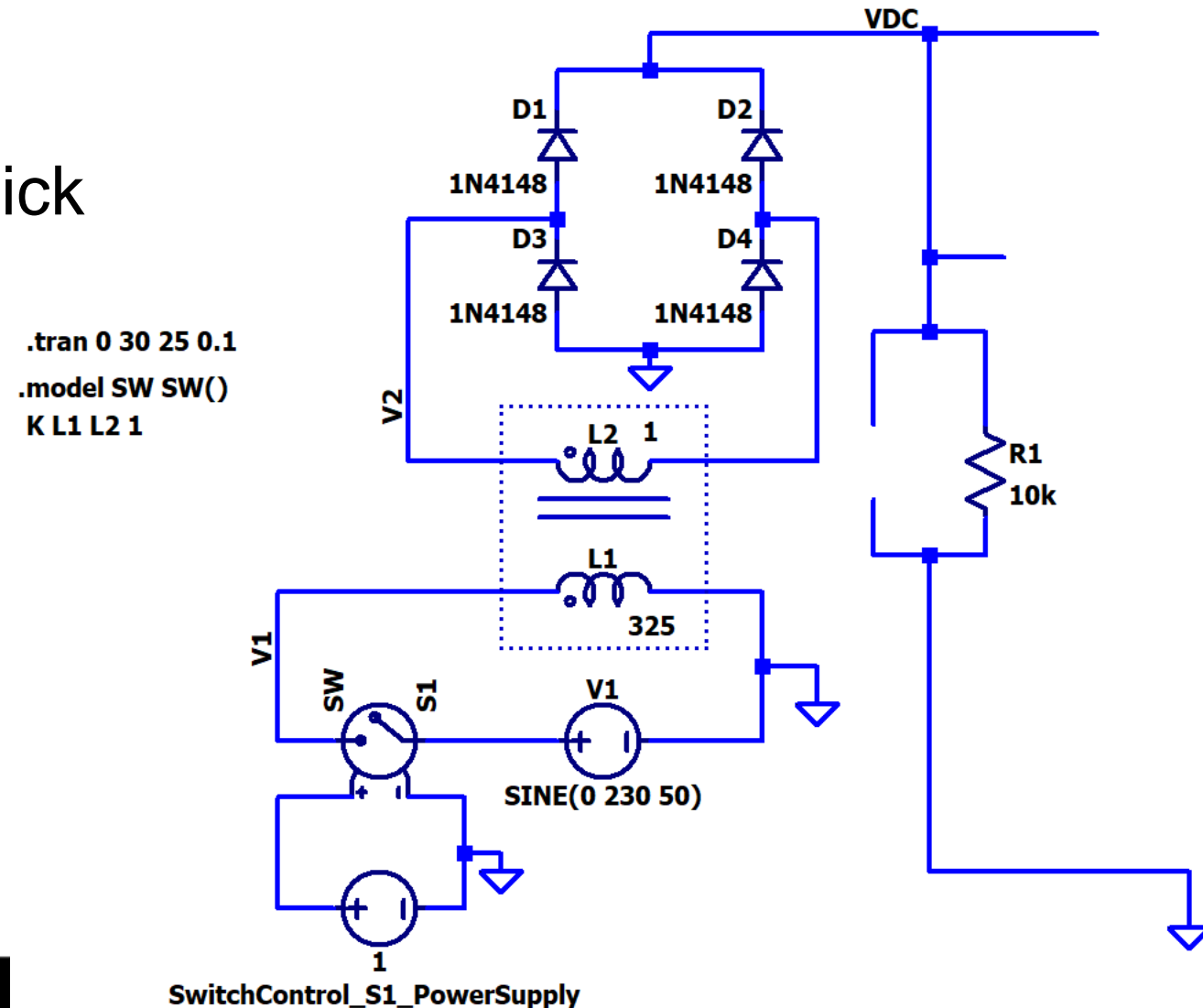

Task 4: Design of Bridge rectifier circuit (with Capacitor)

- Design the bridge rectifier circuit with the capacitor (100uF)
- Plot the voltage at VDC (voltage across the load $R1=10k\Omega$)

```
.tran 0 30 25 0.1
.model SW SW()
K L1 L2 1
```

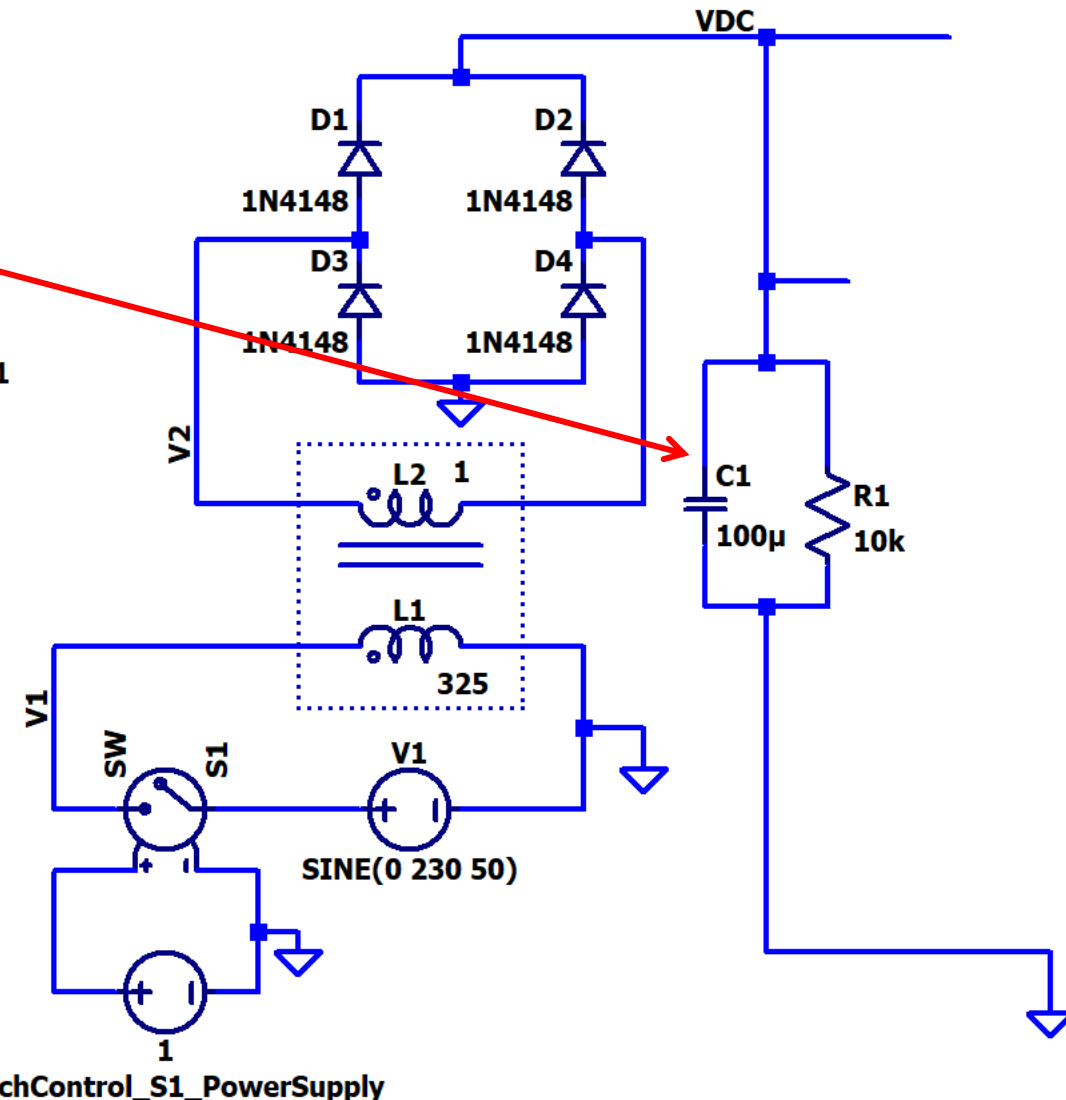

Task 5: Design of Charging circuit from 12V DC input supply

- Design the circuit as shown below and also name the nodes using Label

VDC


VB

VE

VC


Vbattery

VLED

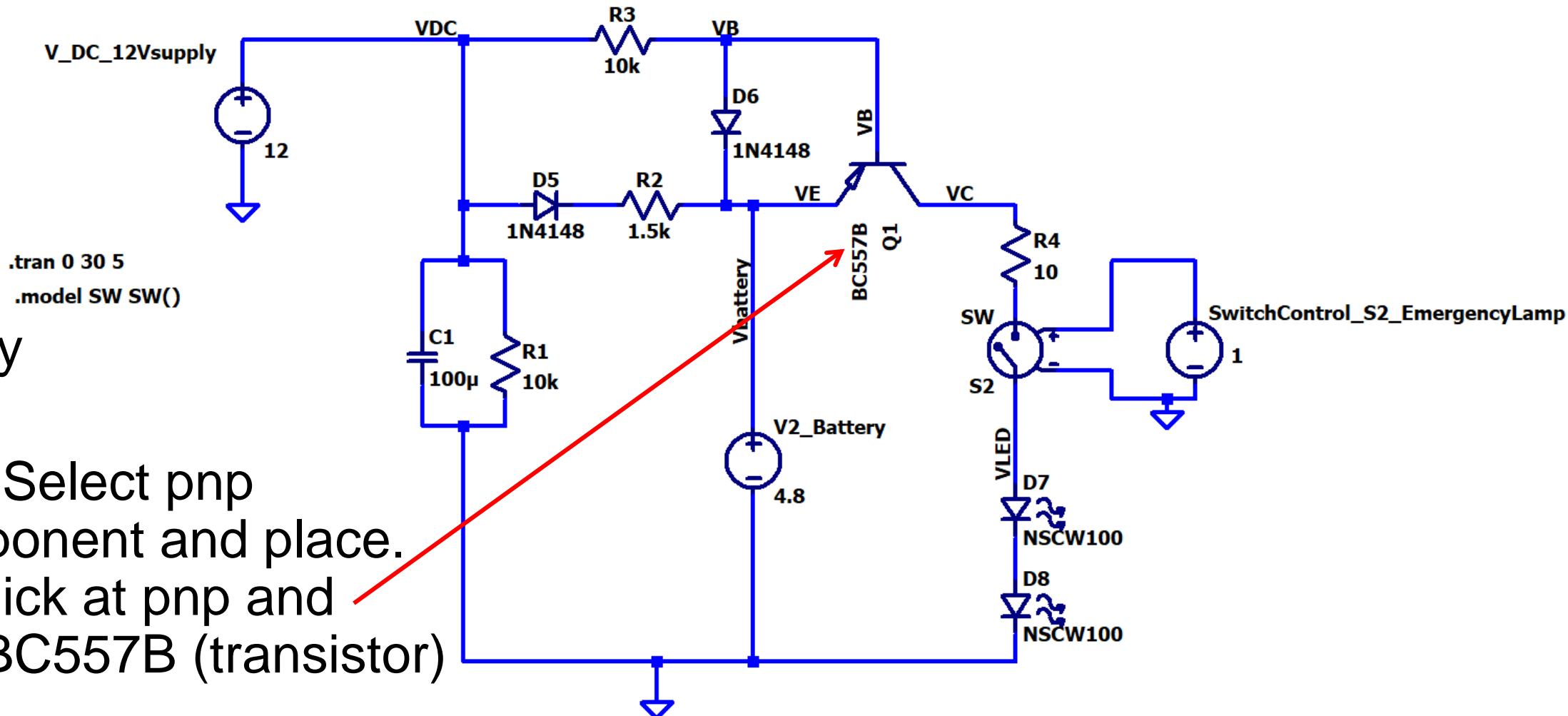

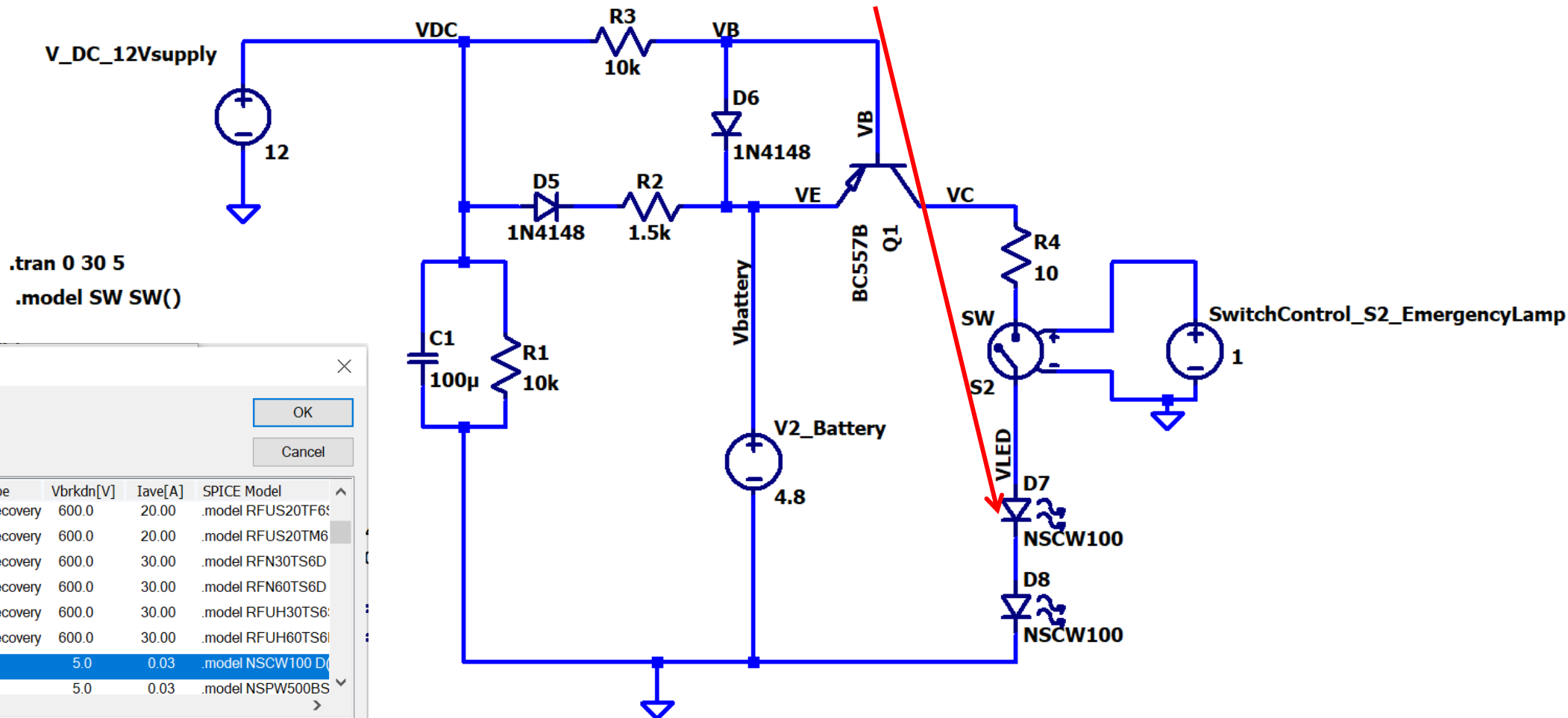Task 5: Design of Charging circuit from 12V DC input supply

- For LEDs: Select diode in component library and place two diodes, Right click and select diode – Select NSCW100




Select Diode

Part No.	Mfg.	type	Vbrkdn[V]	Iave[A]	SPICE Model
RFUS20TF6S	Rohm	FastRecovery	600.0	20.00	.model RFUS20TF6S
RFUS20TM6S	Rohm	FastRecovery	600.0	20.00	.model RFUS20TM6S
RFN30TS6D	Rohm	FastRecovery	600.0	30.00	.model RFN30TS6D
RFN60TS6D	Rohm	FastRecovery	600.0	30.00	.model RFN60TS6D
RFUH30TS6S	Rohm	FastRecovery	600.0	30.00	.model RFUH30TS6S
RFUH60TS6D	Rohm	FastRecovery	600.0	30.00	.model RFUH60TS6D
NSCW100	Nichia	LED	5.0	0.03	.model NSCW100 D
NSPW500BS	Nichia	LED	5.0	0.03	.model NSPW500BS

Task 5: Design of Charging circuit from 12V DC input supply


- Switch S2 has a control source with 1V for S2 ON.

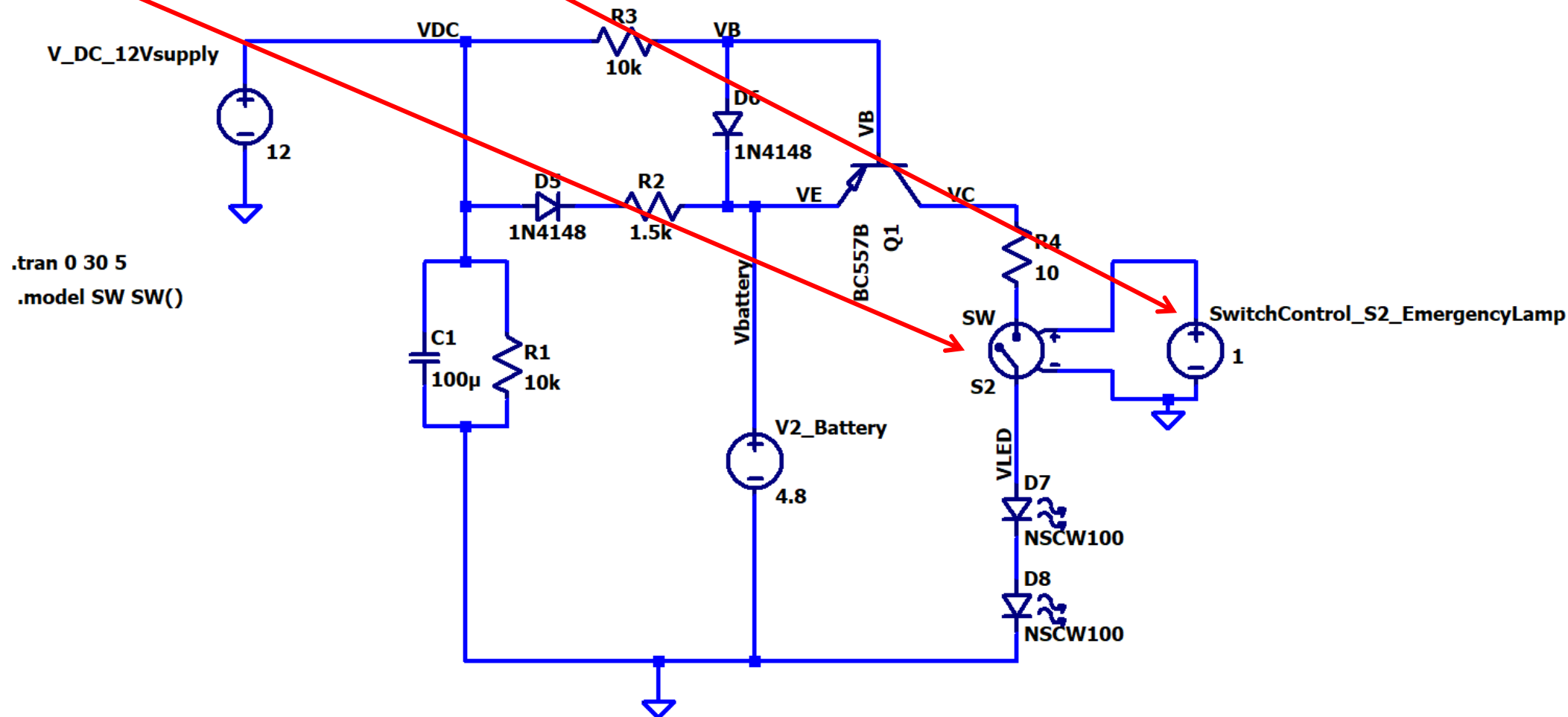

Task 5: Design of Charging circuit from 12V DC input supply

Case 1: Input DC is ON.


- When $V_{DC}=12V$,
 $V_E=4.8V$
 Voltage between V_{DC} and V_E is $7.2V$.
 This is across $D5$, $R2$ and across $R3$, $D6$.

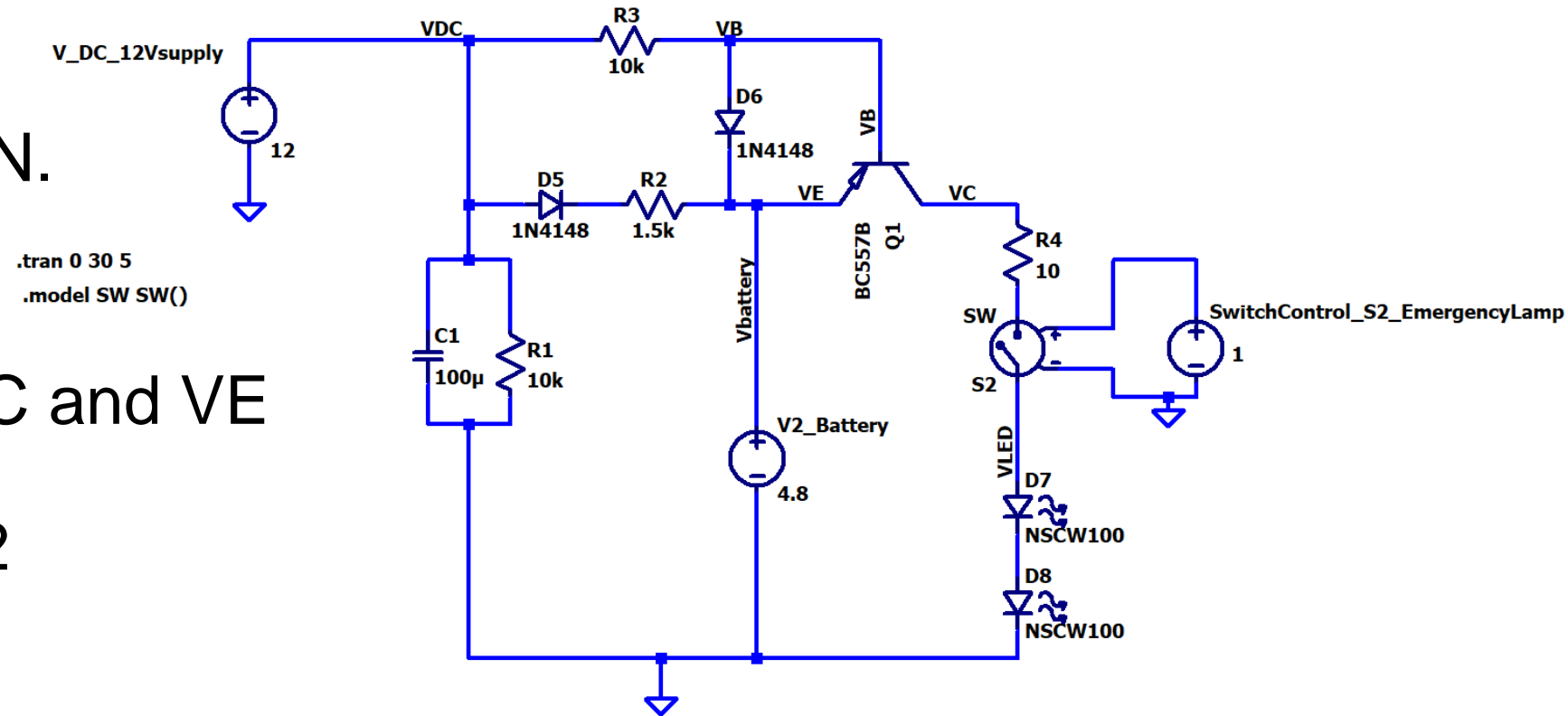

Task 5: Design of Charging circuit from 12V DC input supply

Case 1: Input DC is ON.


- When $V_{DC}=12V$, $V_E=4.8V$
Voltage between V_{DC} and V_E is $7.2V$.
This is across $D5$, $R2$ and across $R3$, $D6$.
- Both diodes are forward biased, and **V2 battery is charging.**
Hence Voltage between V_B and V_E is positive. (V_{BE} is positive)
- In **PNP transistor**, V_{BE} should be negative for transistor to be ON. But here V_{BE} is positive, hence transistor is in CUTOFF. Hence No supply to LEDs, **LEDs are OFF when input supply exists.**

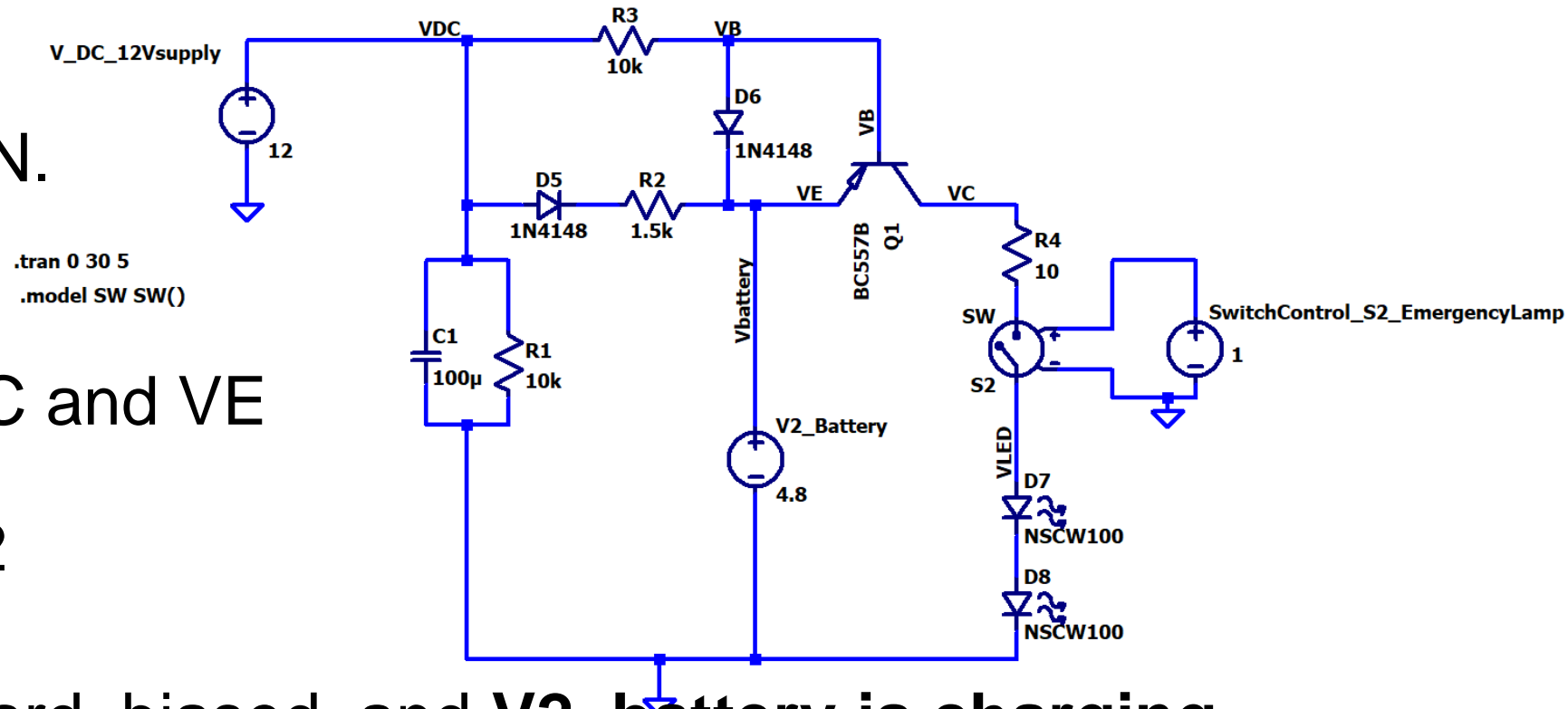

Task 5: Design of Charging circuit from 12V DC input supply

Case 1: Input DC is ON.

- With
DC ON,
Plot VDC
Plot Vbattery
Plot VE
Plot VB
Plot VC
Plot VLED

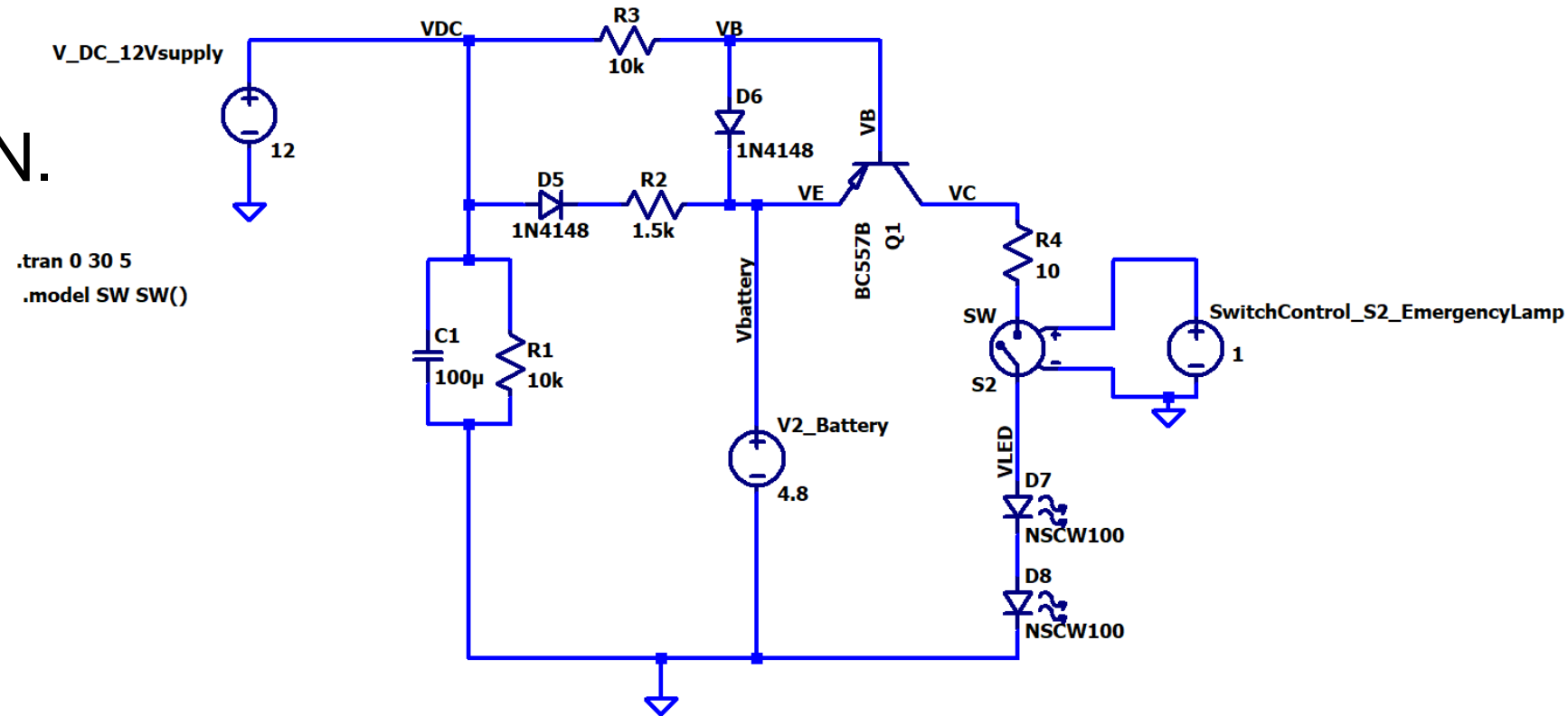


Task 5: Design of Charging circuit from 12V DC input supply

Case 2: Input DC is OFF.

$V_{DC}=0V$

$V_E=4.8V$

D5 and D6 are reverse biased.

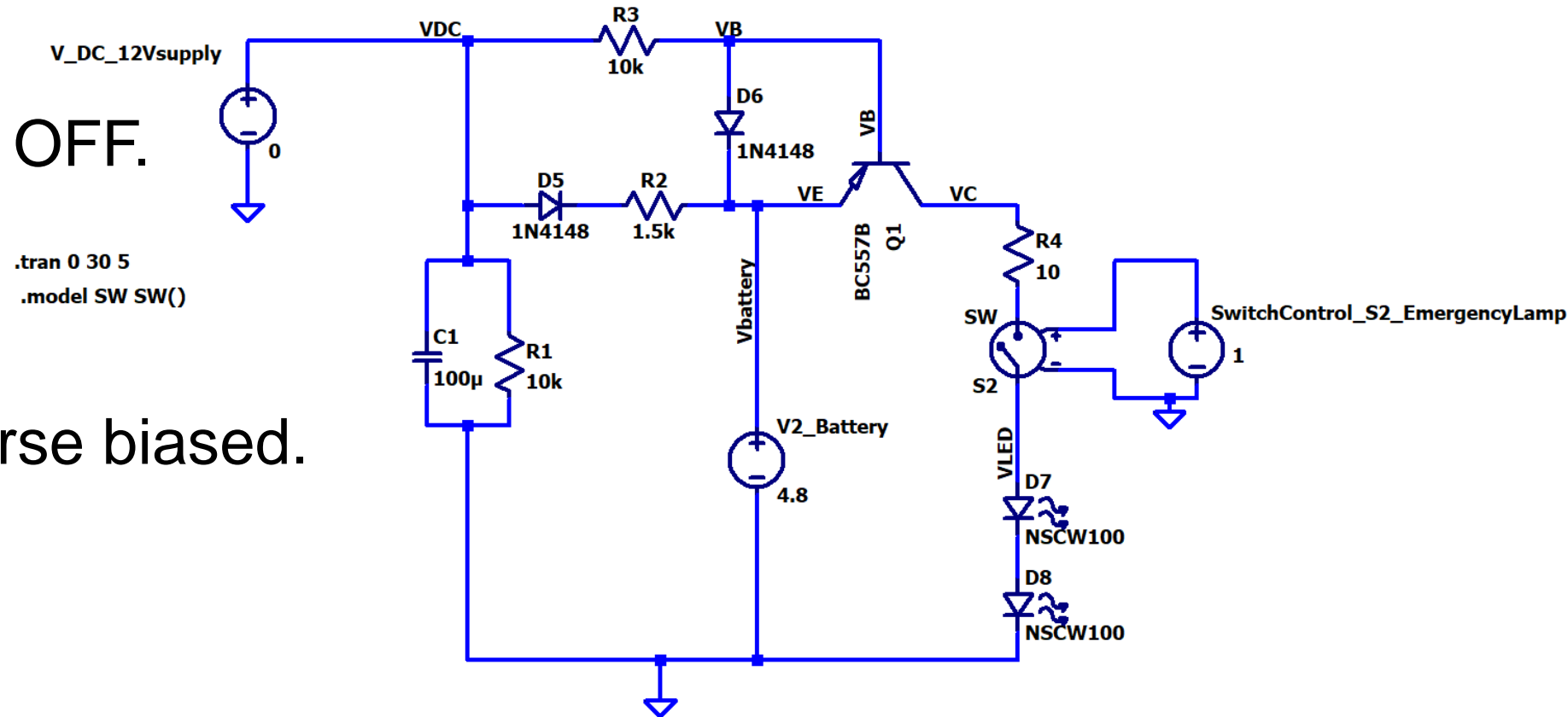

Task 5: Design of Charging circuit from 12V DC input supply



Case 2: Input DC is OFF.

$V_{DC}=0V$

$V_E=4.8V$

D5 and D6 are reverse biased.

The circuit has equivalent like:

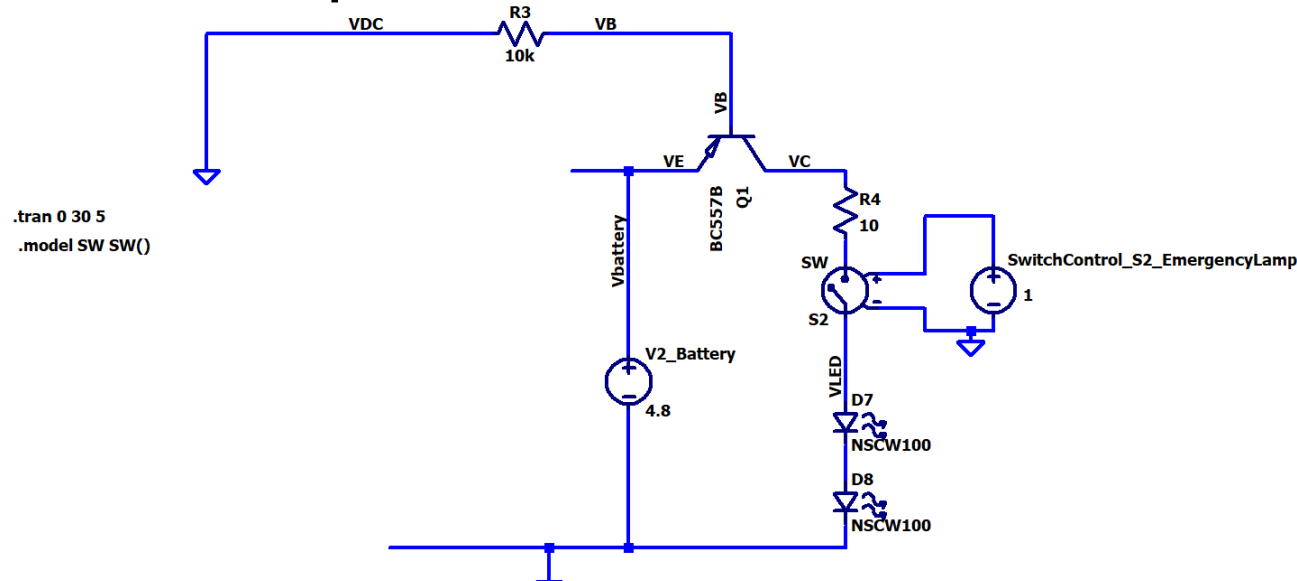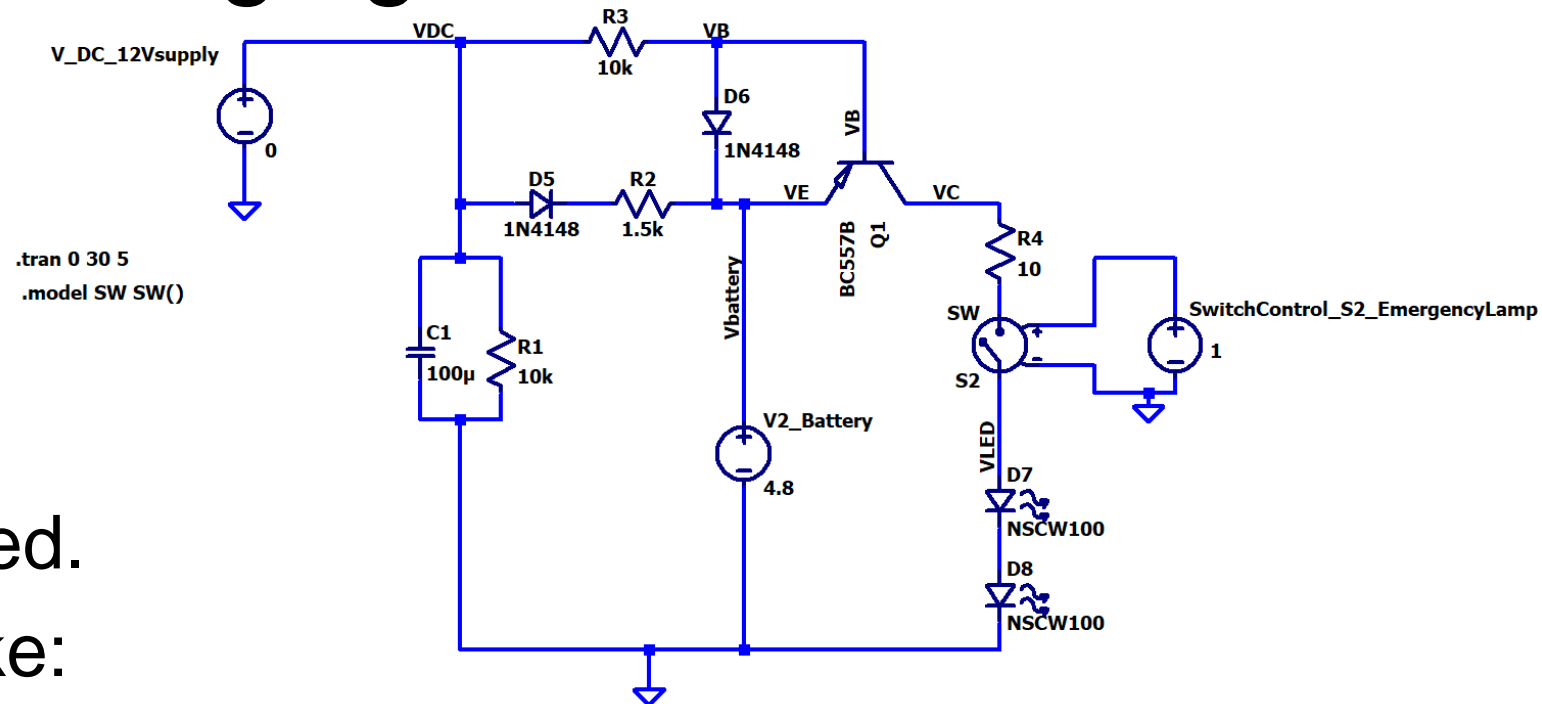



Task 5: Design of Charging circuit from 12V DC input supply

Case 2: Input DC is OFF.
 $V_{DC}=0V$

$V_E=4.8V$

D5 and D6 are reverse biased.

The circuit has equivalent like:

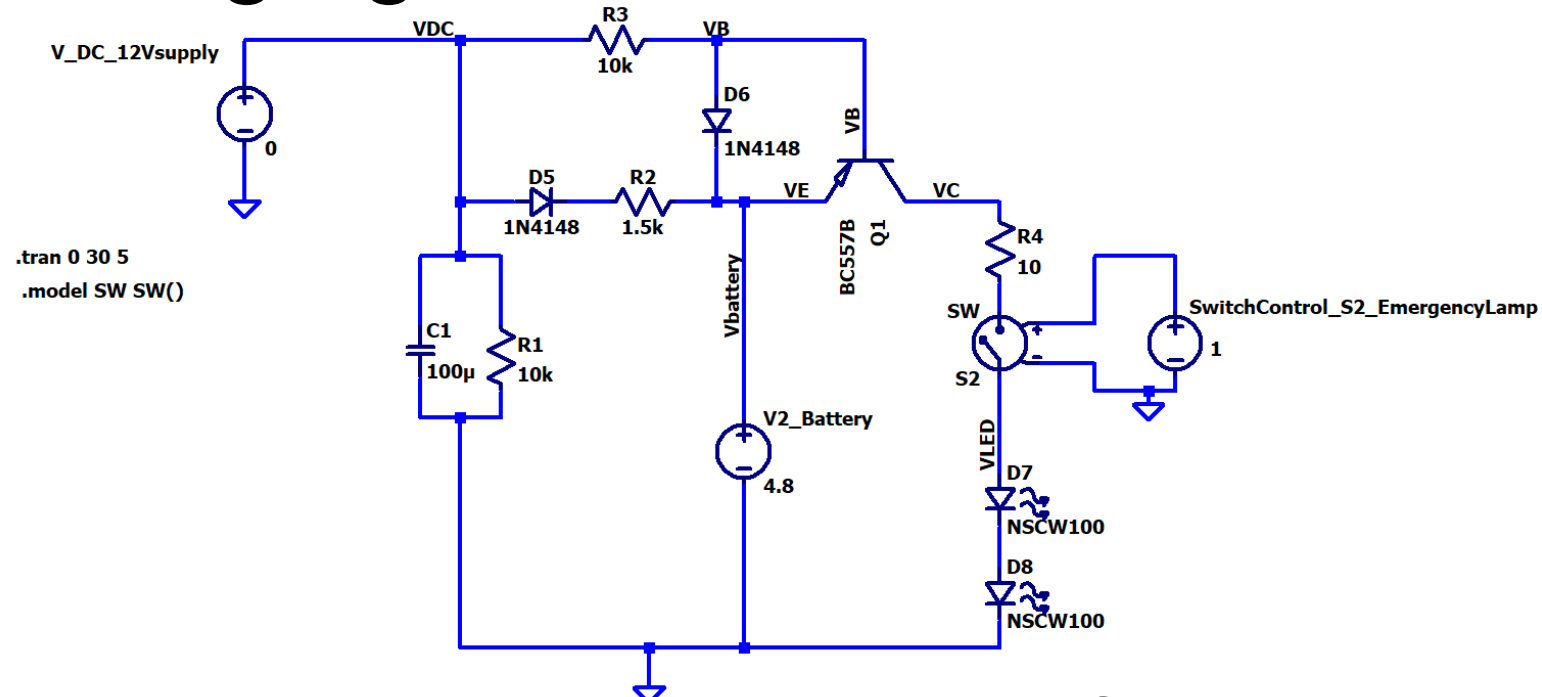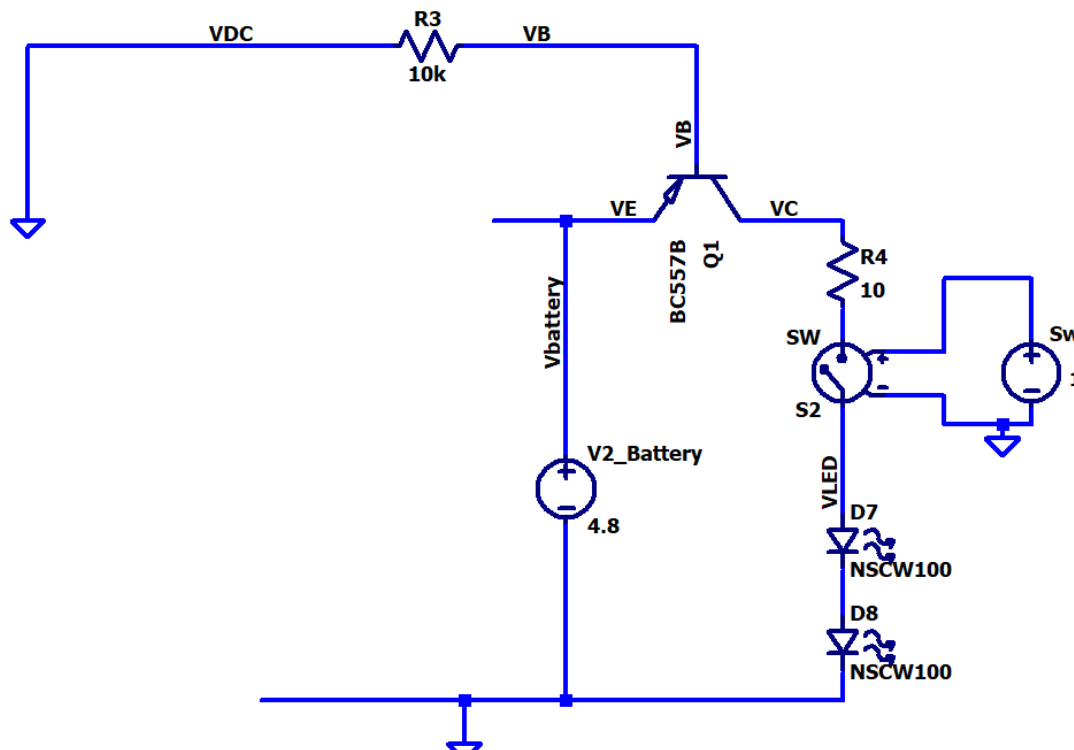

Note: V_E is 4.8V, $V_{DC}=0V$
 V_{BE} is negative

PNP: V_{EB} is positive (V_{BE} is -ve)
 Transistor conducts:
 4.8V across VC. With S2 ON,
 LEDs are ON


Task 5: Design of Charging circuit from 12V DC input supply

Case 2: Input DC is OFF.
 $V_{DC}=0V$

$V_E=4.8V$

D5 and D6 are reverse biased.

The circuit has equivalent like:

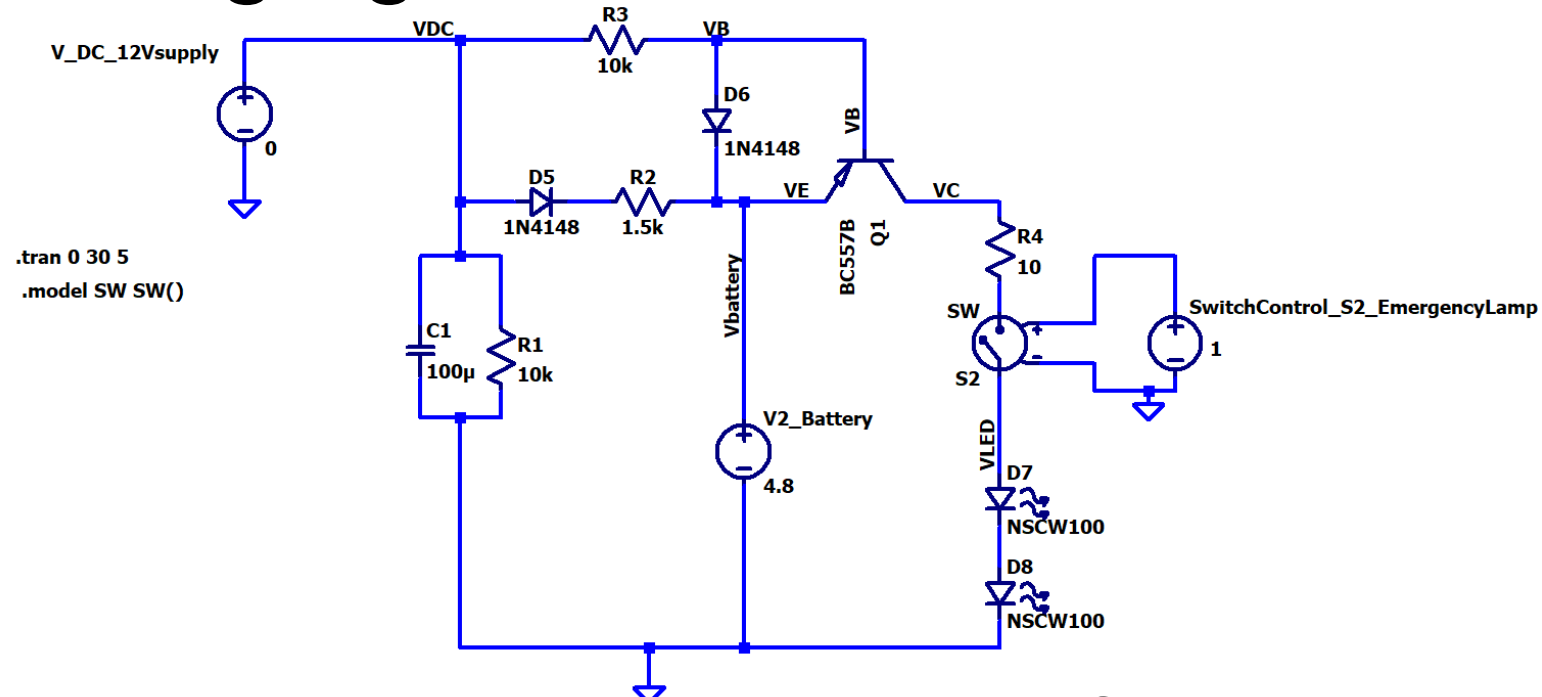

Note: V_E is 4.8V, $V_{DC}=0V$
 V_{BE} is negative

PNP: V_{EB} is positive (V_{BE} is -ve)
 Transistor conducts:
 4.8V across VC. With S2 ON,
 LEDs are ON



Task 5: Design of Charging circuit from 12V DC input supply

Case 2: Input DC is OFF.
VDC=0V


Plot VB

Plot VE


Plot VC

Plot VE


Plot VLED

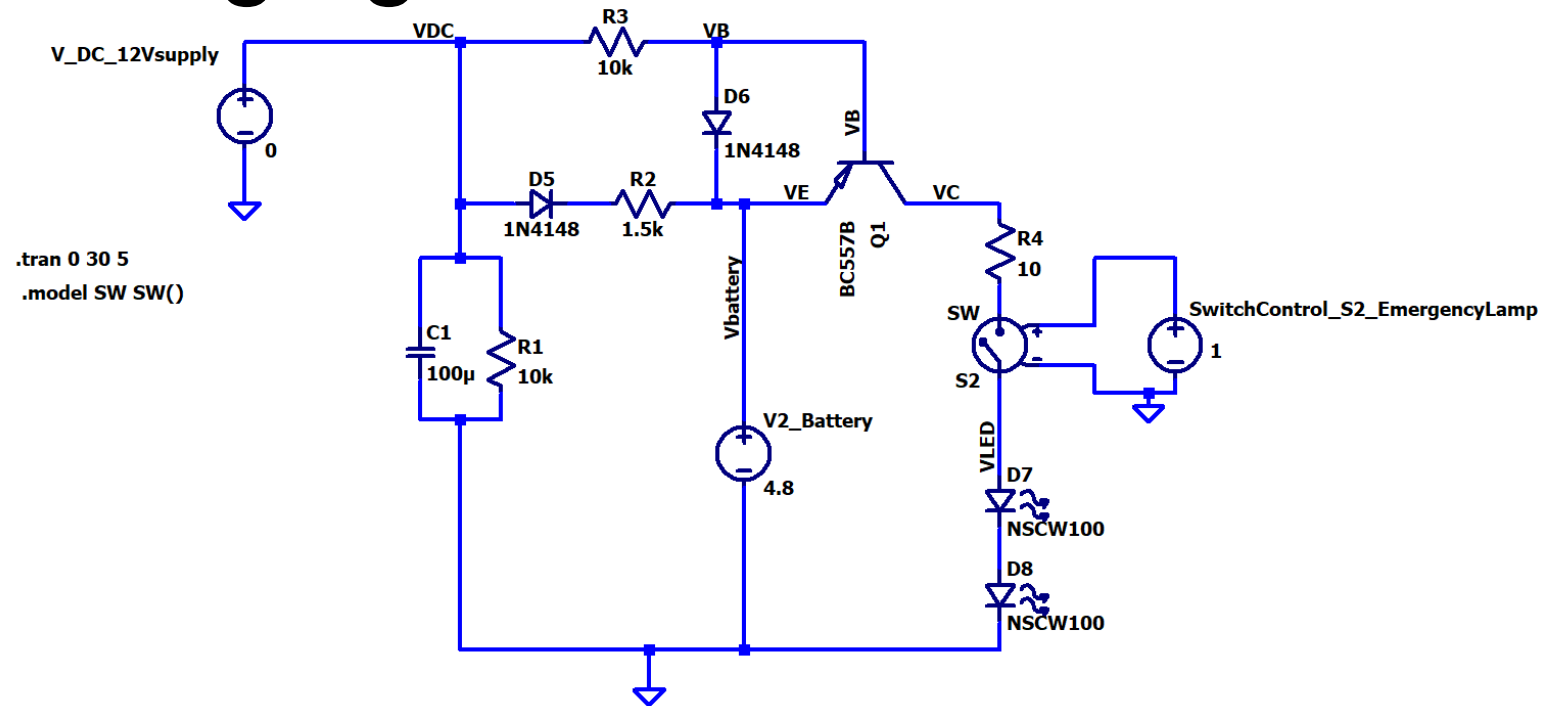

Task 6: Integrate Bridge circuit to Emergency Lamp: Complete the circuit

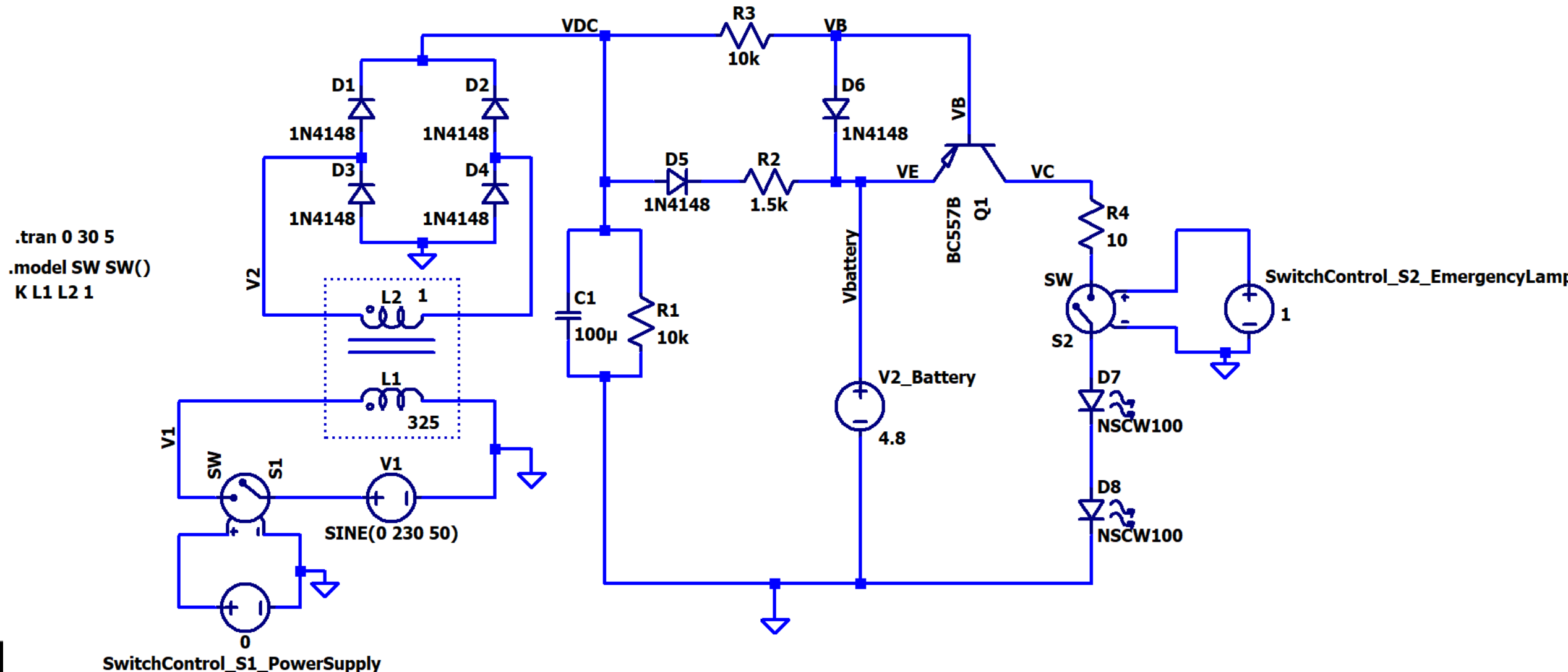

Task 6: Integrate Bridge circuit to Emergency Lamp: Complete the circuit

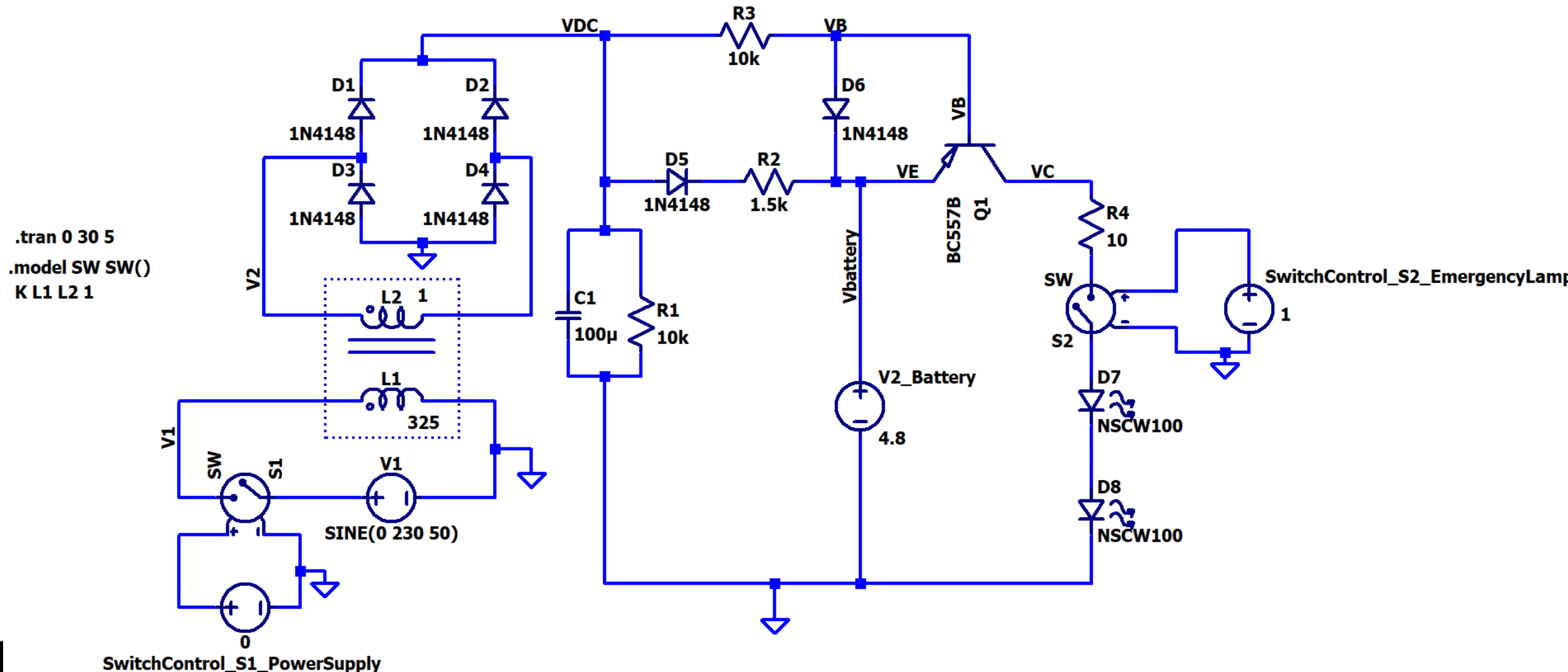

Task 6: Integrate Bridge circuit to Emergency Lamp: Complete the circuit

a) With S1 ON, S2 ON, Plot the following:

V1

V2

VDC

Vbattery


VB

VE,

VC,

VLED

Comment on VC,
VLED

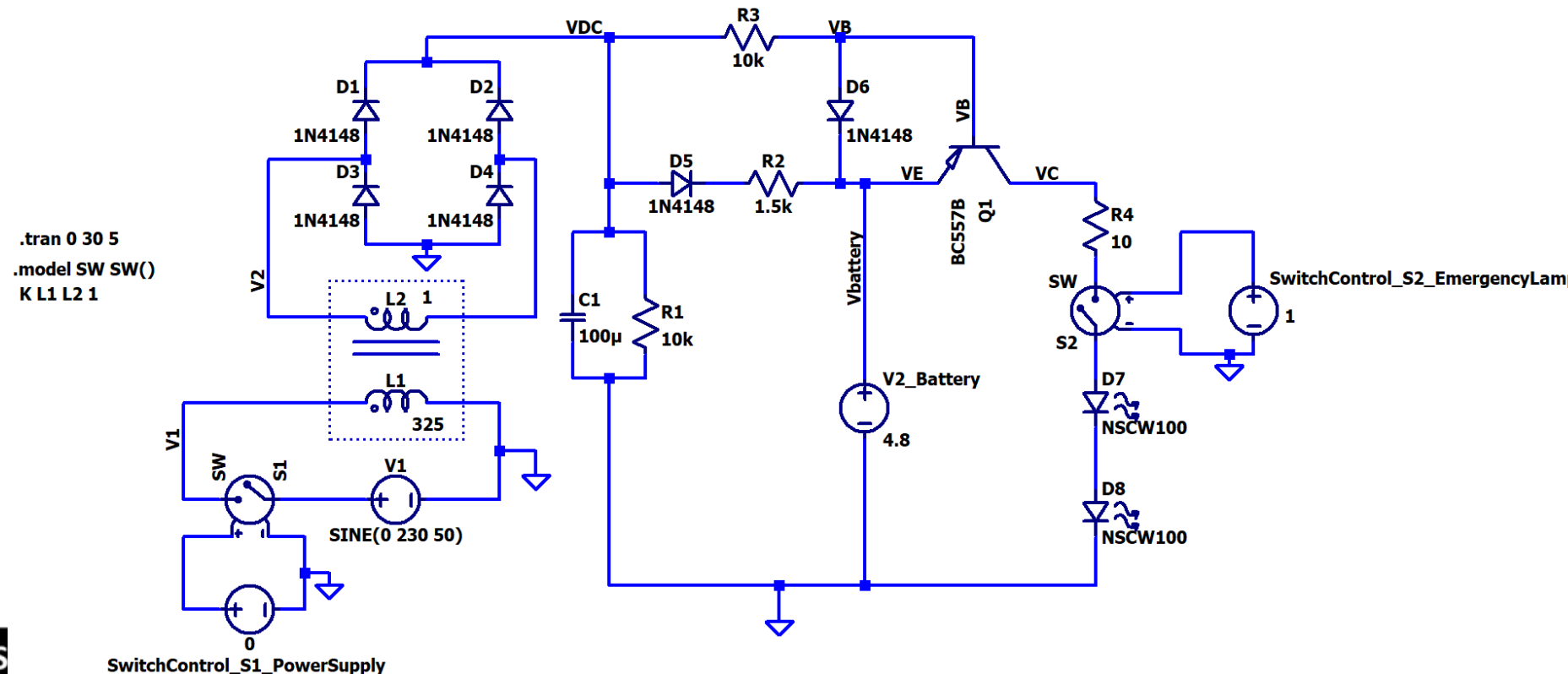

Task 6: Integrate Bridge circuit to Emergency Lamp: Complete the circuit

b) With S1 OFF, S2 ON, Plot the following:

V1

V2

VDC

Vbattery


VB

VE,

VC,

VLED


Comment on
VLED

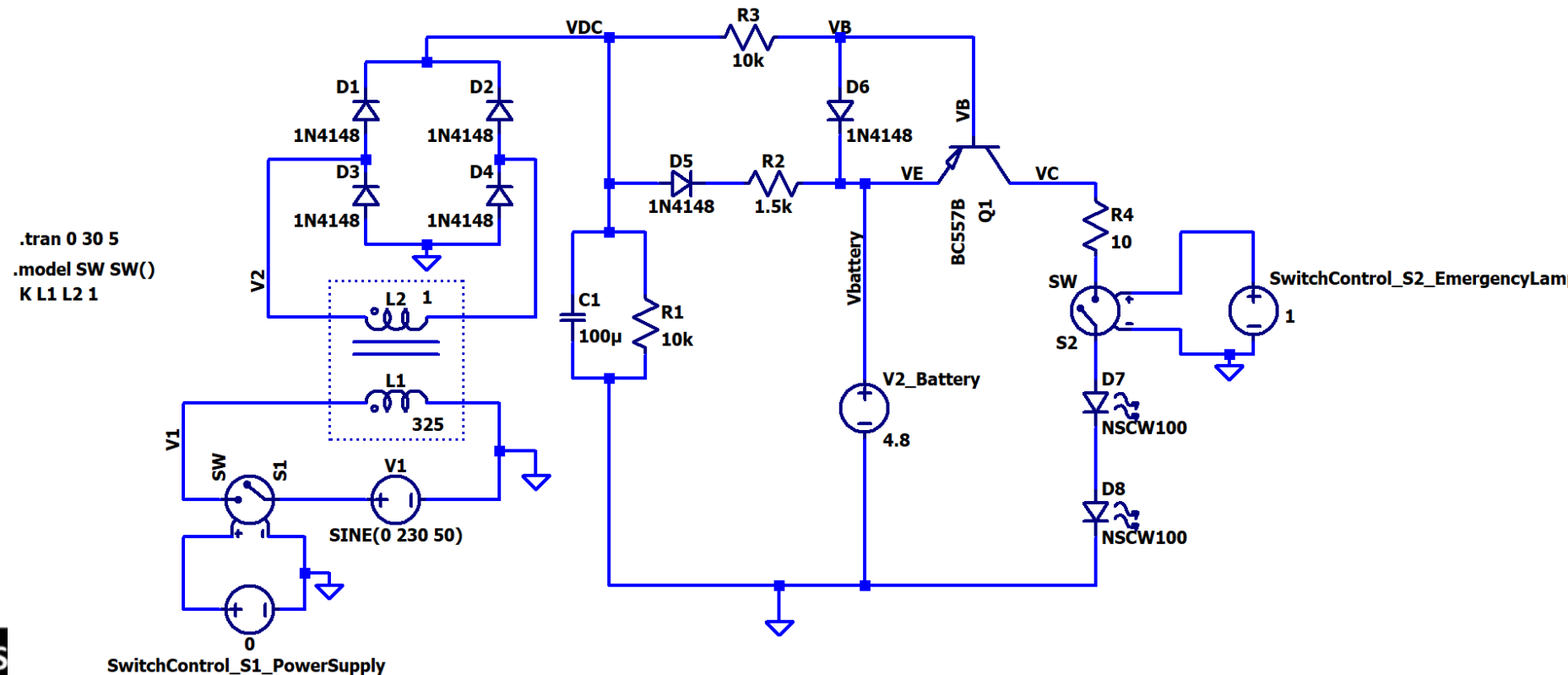

Task 6: Integrate Bridge circuit to Emergency Lamp: Complete the circuit

c) With S1 OFF, S2 OFF, Plot the following:

VLED
Comment on VLED

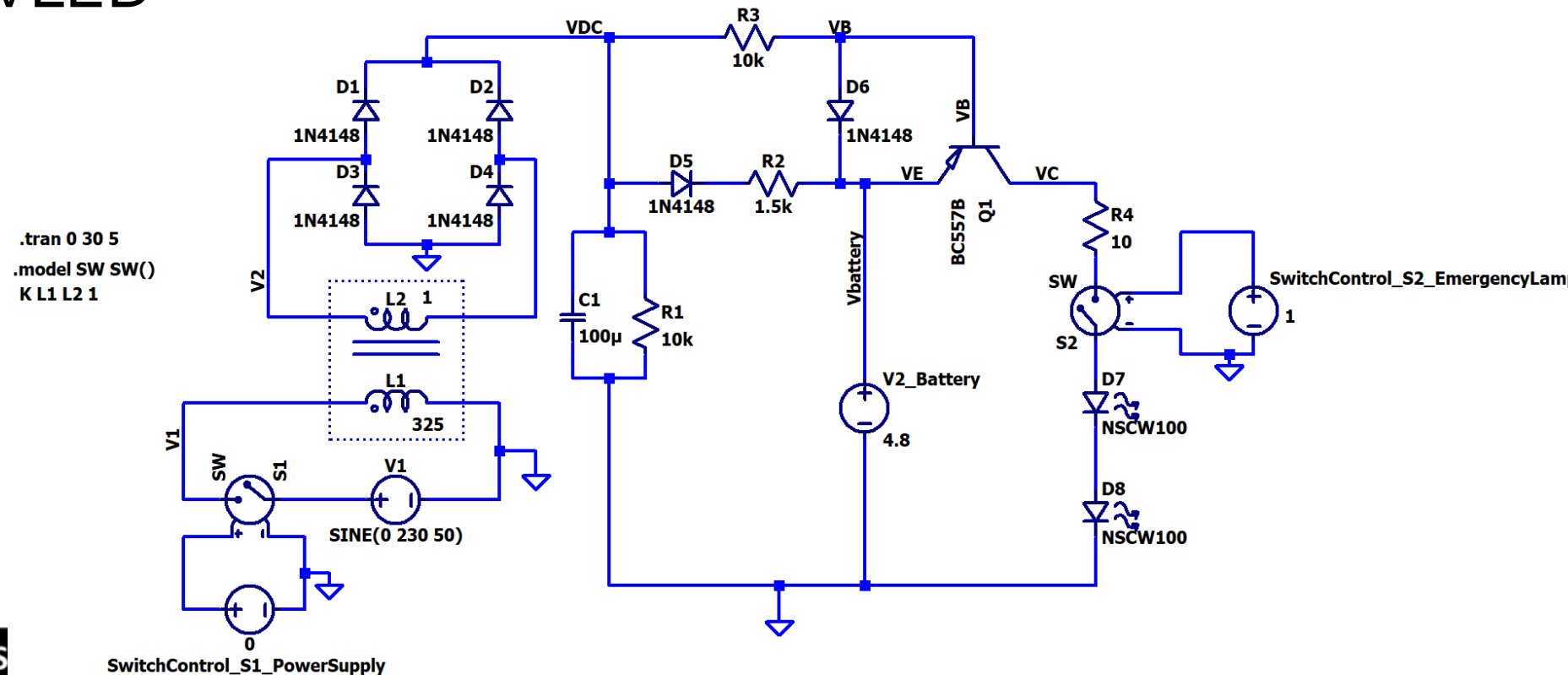

Important NOTE

- Enter your **registration number** and **Full Name** next to
all your circuits and
the **output plots**.
- Keep the background of circuit and plot
as white.



LAB record instructions:

For the lab experiment,

- Write the **Aim**.
- Complete the **Software/Hardware components used**.
- **Obtain the expression for the outputs.**
- Place the respective **circuits in LT Spice**.
- Connect the inputs and outputs. Name them and **write the same in the lab copy(inputs and outputs section)**.
- Use probe in LT spice to plot all possible combinations.
- Write a **concluding statement for each circuit**.
- **Submit** the document's soft copy **on time** in lms.vit.ac.in when available.

