

Date: 09/08/2021 Exp. 2 Testing and Troubleshooting of Diodes, Zener Diodes and Transistors


1)

Aim: To learn the testing and trouble shooting of Diodes and to obtain diode characteristics (V-I).


Software/Hardware Components used: LTSpice, 1 Resistor, 1 Voltmeter, 1 Diode, Ground, Wire

Circuits and Plots:

Circuit

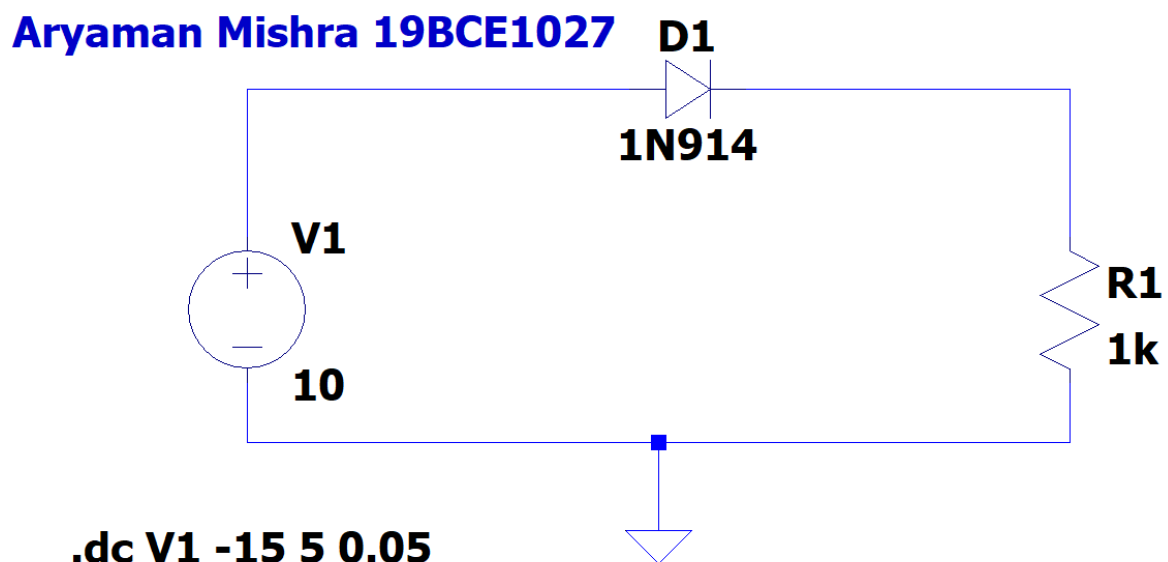

Plot

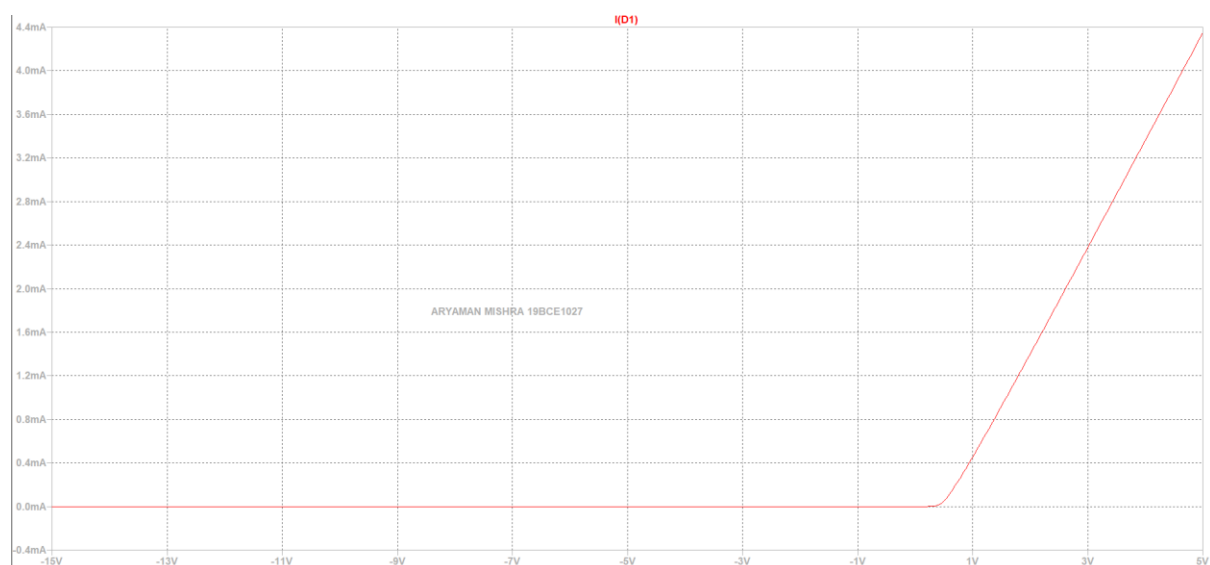

INPUTS AND OUTPUTS:**Inputs**

Components Used	Input Value
V1	10V
R1	1K Ohm
D1	1N914

Conclusion: Hence we are able to obtain the diode characteristics. (V-I)


2)




Aim: To learn the testing and trouble shooting of Zener Diodes and to obtain VI characteristics of Zener Diodes (2 diodes).

Software/Hardware Components used: LTSpice, 1Resistor, 1 Voltmeter, 2 Diodes, Ground, Wire

Circuits and Plots:**Circuit 1**

Aryaman Mishra
19BCE1027

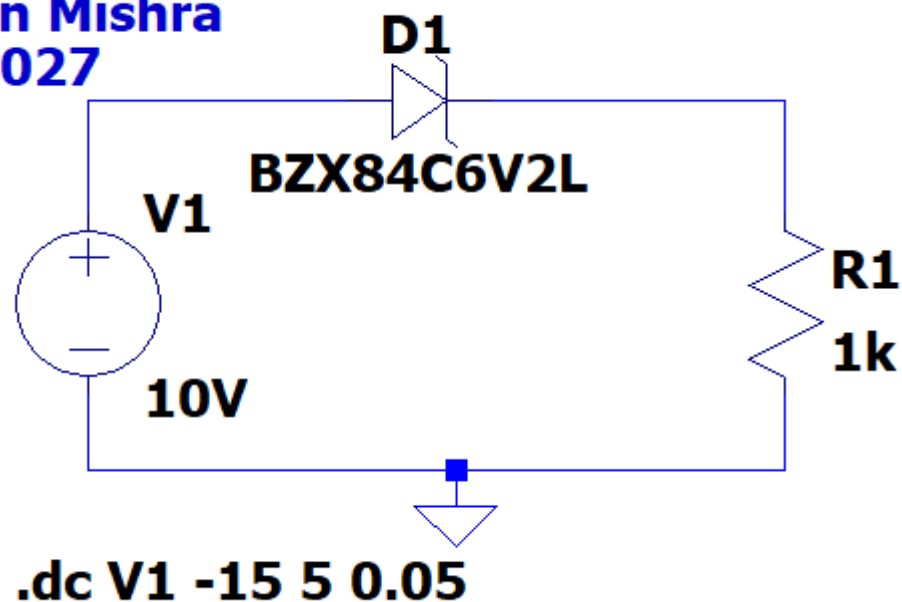

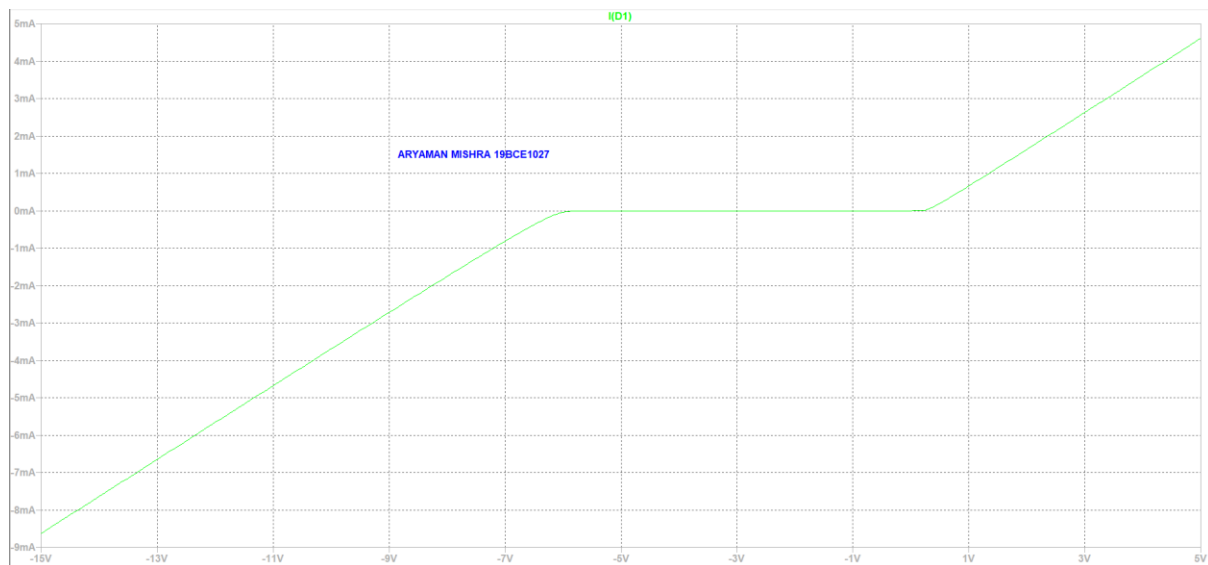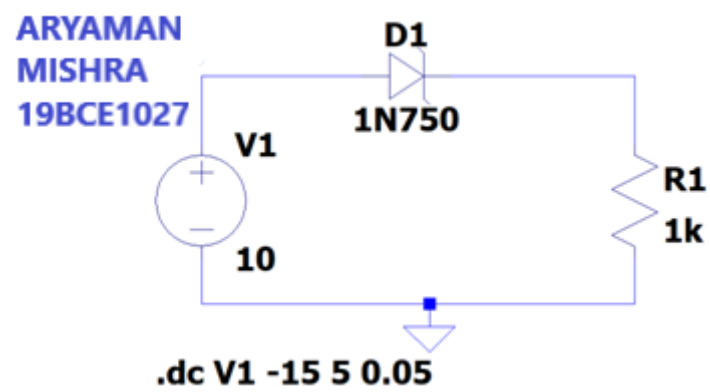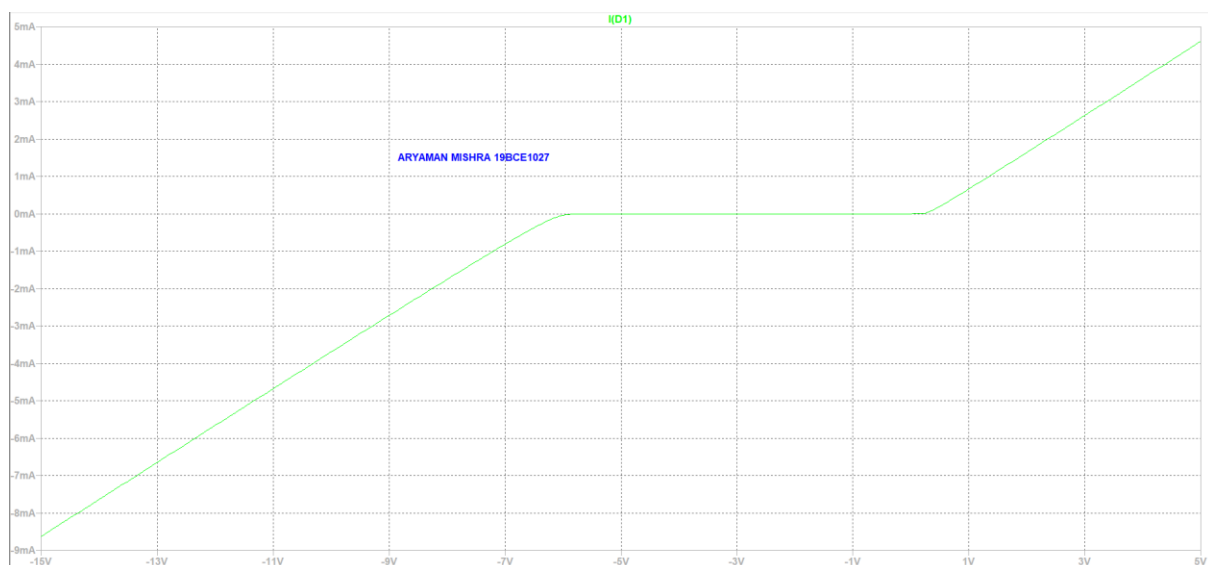Plot 1**Circuit 2****Plot 2**

INPUTS AND OUTPUTS:**Inputs**

Components Used	Input Value
V1	10V
R1	1K Ohm
D1	BZX84C6V2L, 1N750


Conclusion: Hence we obtain the VI Characteristics of the zener diode.



3)


Aim: To learn the testing and trouble shooting of Transistors and obtain Input and output characteristics of NPN Transistor circuit with:

- CE configuration
- CB configuration
- CC configuration

Software/Hardware Components used: LTSpice, 2 Resistors, 2 Voltmeters, 1 Diode, Ground, Wire

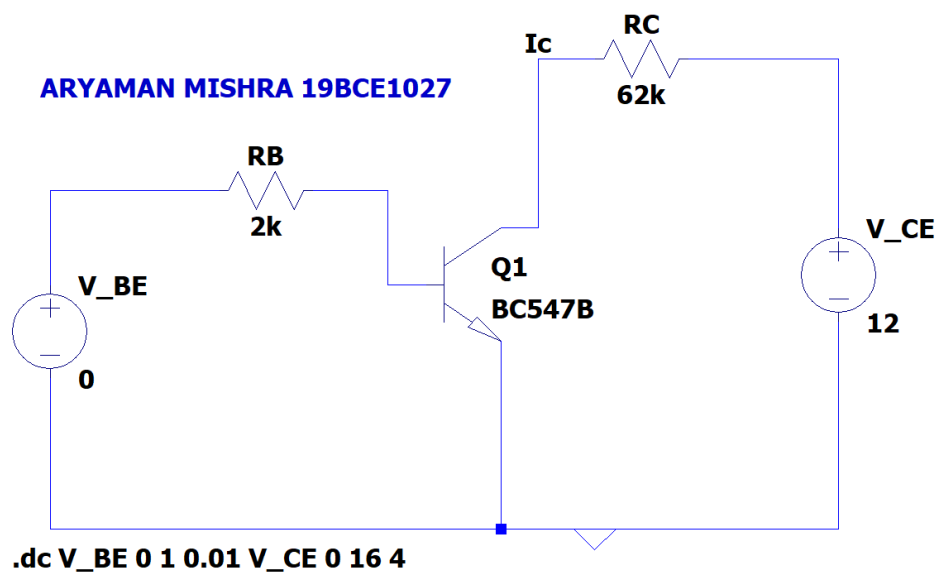
Circuits and Plots:**Circuit 1 (Transistor in CE: Input Characteristics)**

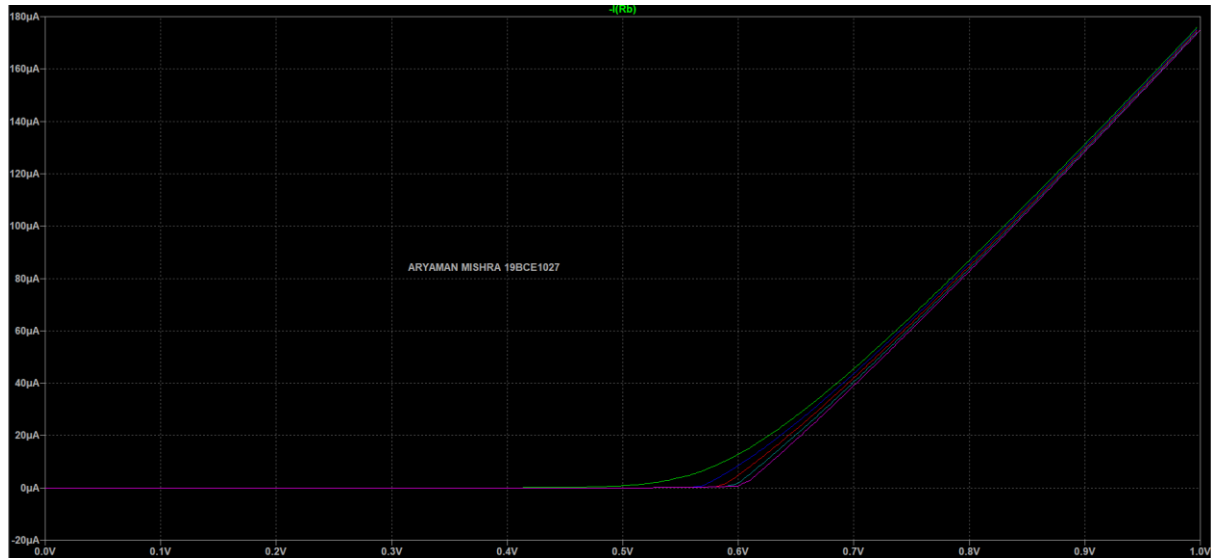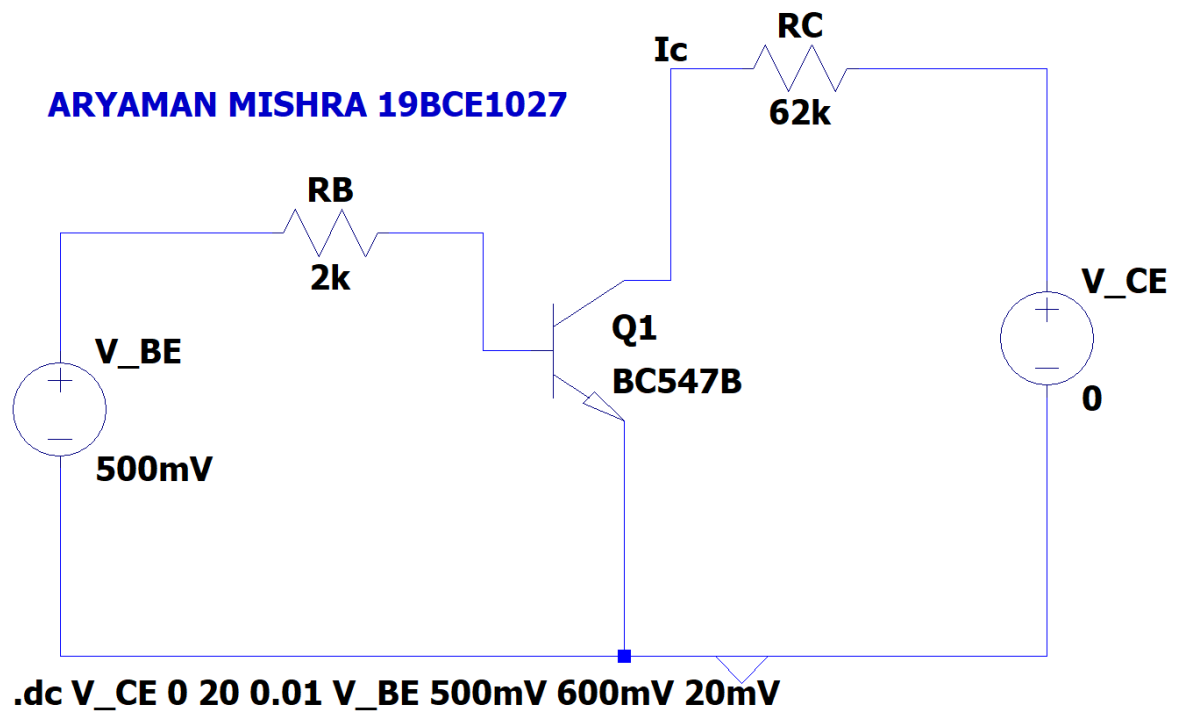
Plot 1 (Transistor in CE: Input Characteristics)**Circuit 2 (Transistor in CE: Output Characteristics)**

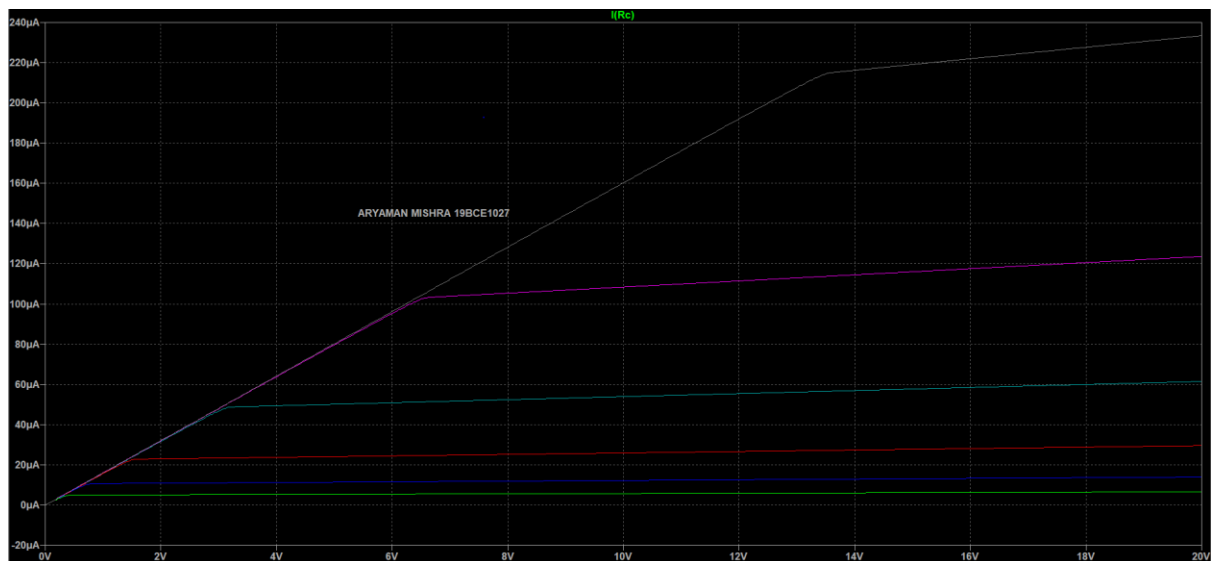Plot 2 (Transistor in CE: Output Characteristics)**Circuit 3 (Transistor in CB: Input Characteristics)**

19BCE1027 Aryaman Mishra


.dc V_EE 0 5V 0.01 V_CC 0 4 1


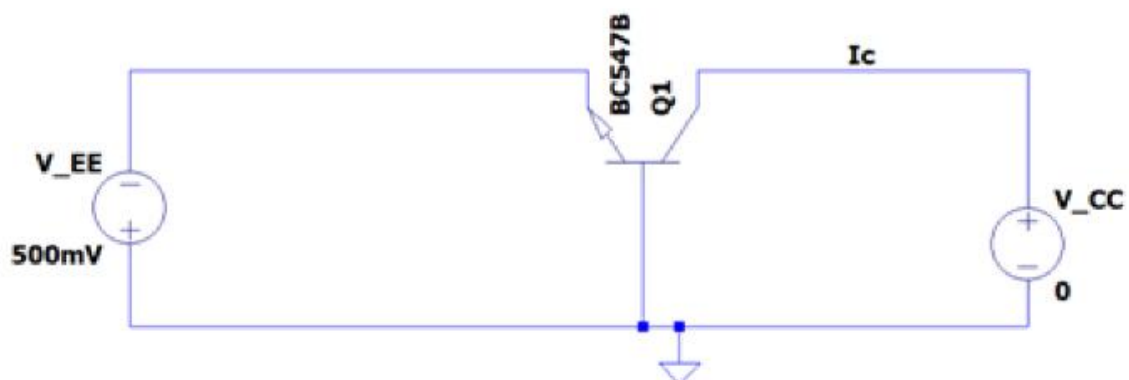


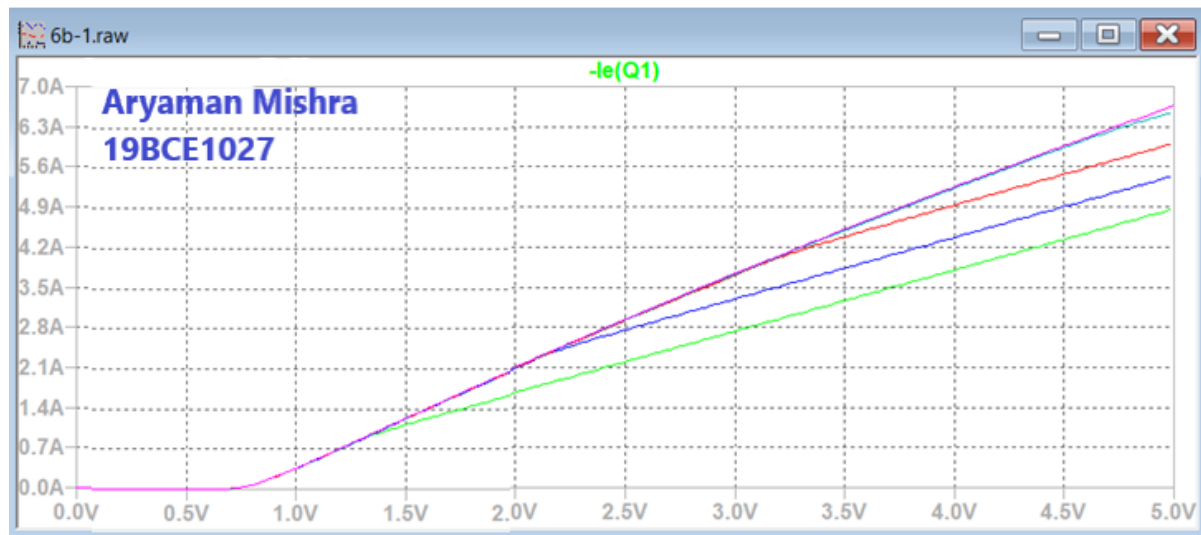
Plot 3 (Transistor in CB: Input Characteristics)**Circuit 4 (Transistor in CB: Output Characteristics)**

19BCE1027
Aryaman Mishra

.dc V2 -1 20 0.01 V1 500m 600m 20m

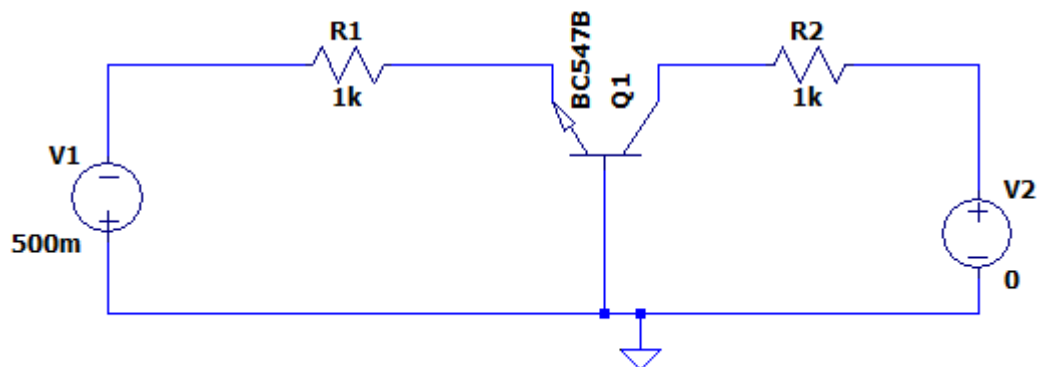

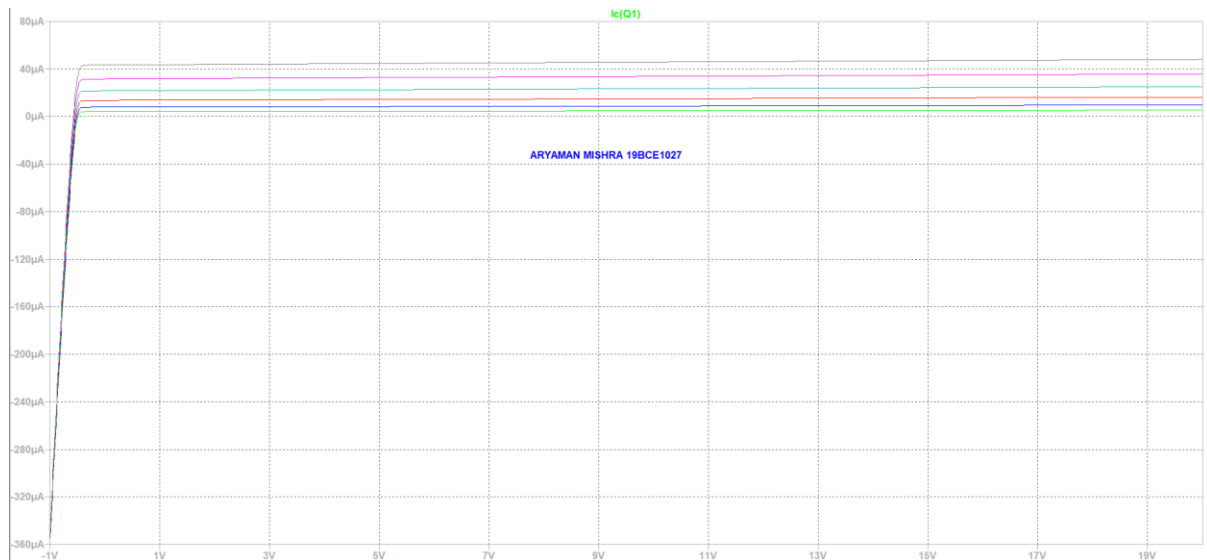
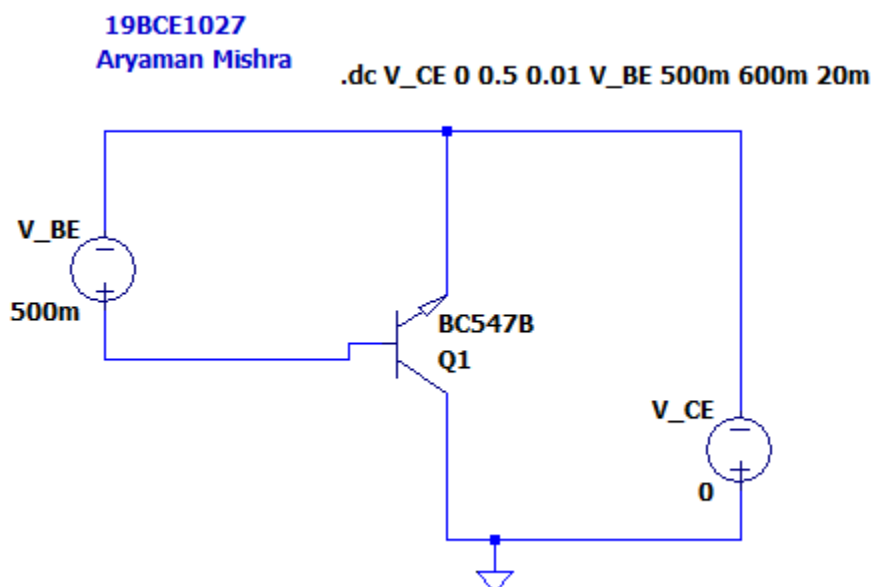
Plot 4 (Transistor in CB: Output Characteristics)**Circuit 5 (Transistor in CC: Input Characteristics)**

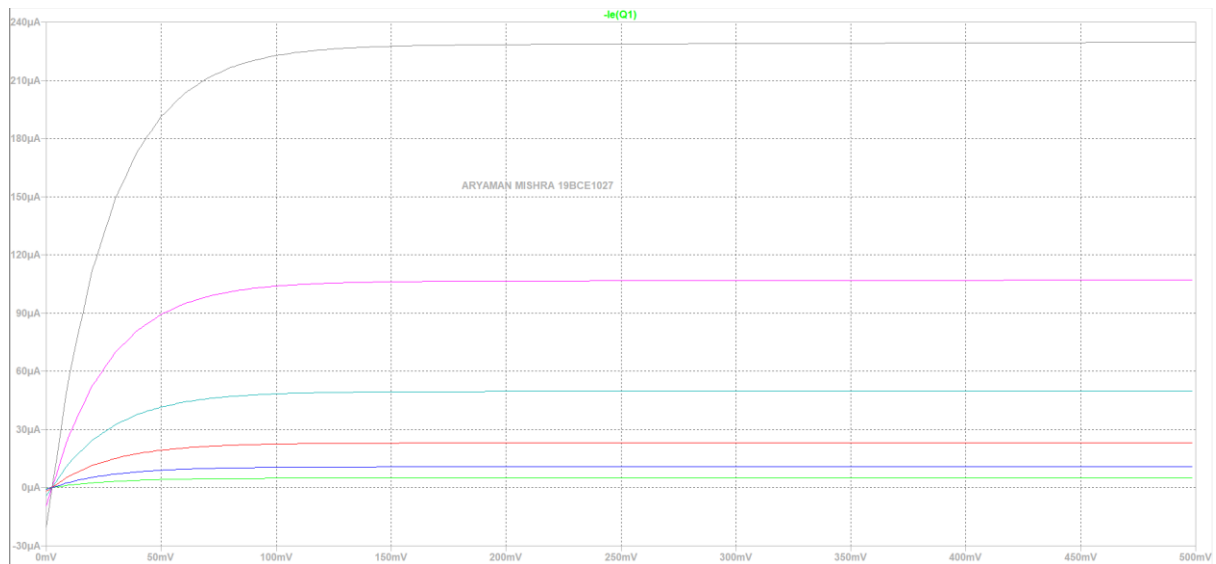Plot 5 (Transistor in CC: Input Characteristics)

Circuit 6 (Transistor in CC: Output Characteristics)

19BCE1027
Aryaman Mishra

.dc V_CE 0 0.5 0.01 V_BE 500m 600m 20m

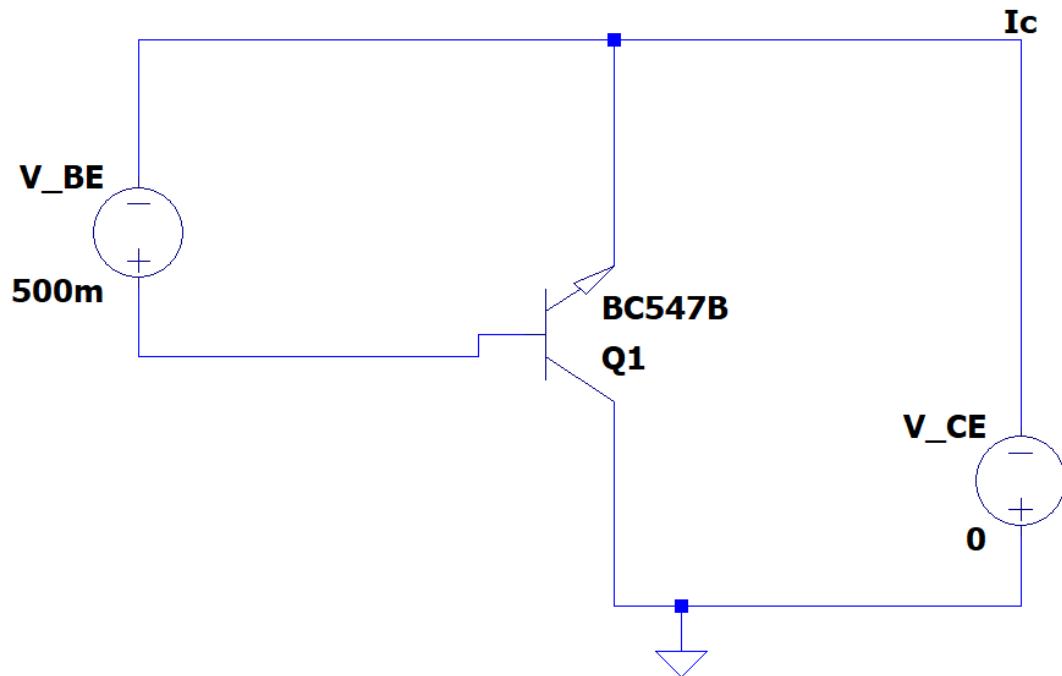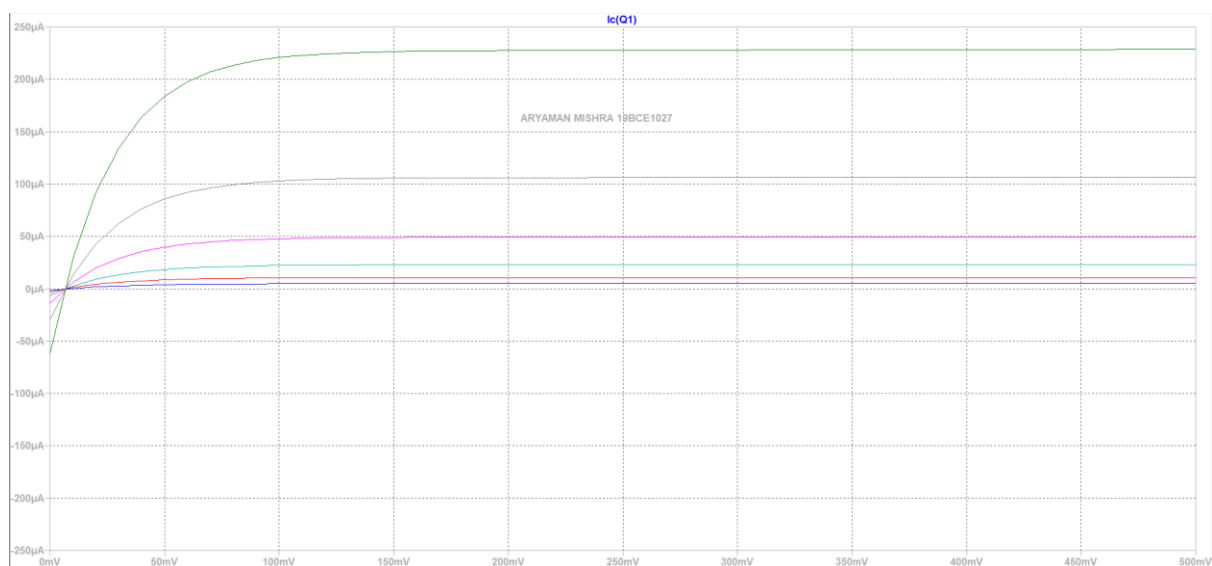**Plot 6 (Transistor in CC: Output Characteristics)**

INPUT AND OUTPUTS:

Components Used	Value
V _{CE}	12 Start Value: 0 Stop Value: 16 Increment: 4
V _{BE}	0 Start Value: 0 Stop Value: 1 Increment: 0.01
RB	2k Ohm
RC	62k Ohm
Q1	BC547B
V _{BE}	500mV CE Output Characteristics: Start Value: 500mV Stop Value: 600mV Increment: 20 CC Input and Output Characteristics: Start Value: 500mV Stop Value: 600mV Increment: 20mV
V _{CE}	0 CE Output Characteristics: Start Value: 0 Stop Value: 20 Increment: 0.01 CC Input Characteristics: Start Value: 0 Stop Value: 2 Increment: 0.01 CC Output Characteristics: Start Value: 0 Stop Value: 0.5 Increment: 0.01
V _{EE}	500mV Input Characteristics: Start Value: 0 Stop Value: 5V Increment: 0.01 Output Characteristics:

	Start Value: 500mV Stop Value: 600mV Increment: 20mV
V _{CC}	0 Input Characteristics: Start Value: 0 Stop Value: 4 Increment: 1 Output Characteristics: Start Value: -1 Stop Value: 20 Increment: 0.01
R1	1k
R2	1k

Conclusion: Hence we obtain the Input and output characteristics of NPN Transistor circuits.