

Name: Aryaman Mishra

Reg. no: 19BCE1027

Date: 23-08-2021

EXPERIMENT NO: 4

Design and Troubleshooting of Bridge Rectifiers with RC filters


Aim: Design Half wave rectifier and plot input voltage and output voltages

Software used: LTSpice


Components required: Resistors, voltage source, inductors, diode.

Task 1.1: In phase windings (2m:1m)

Circuit:

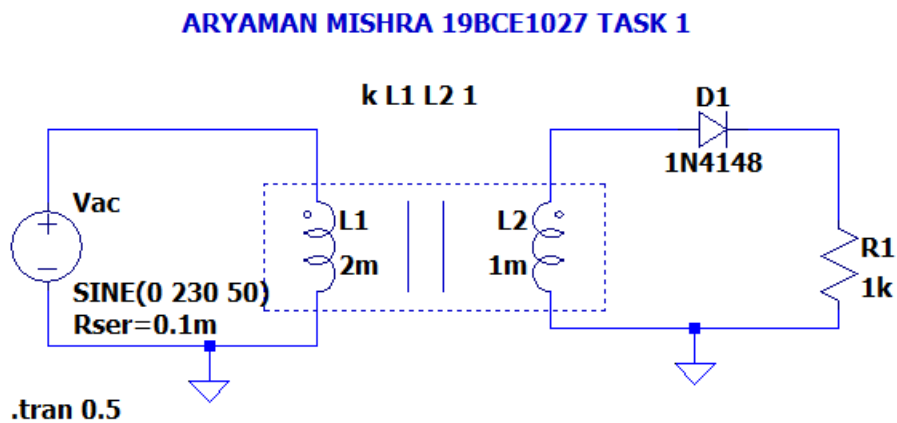


Output:

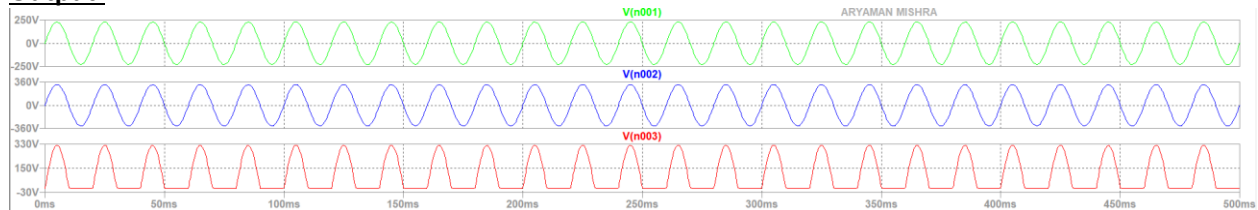


Task 1.2: In phase windings (1m:1m)

Circuit:

ARYAMAN MISHRA 19BCE1027 TASK 1

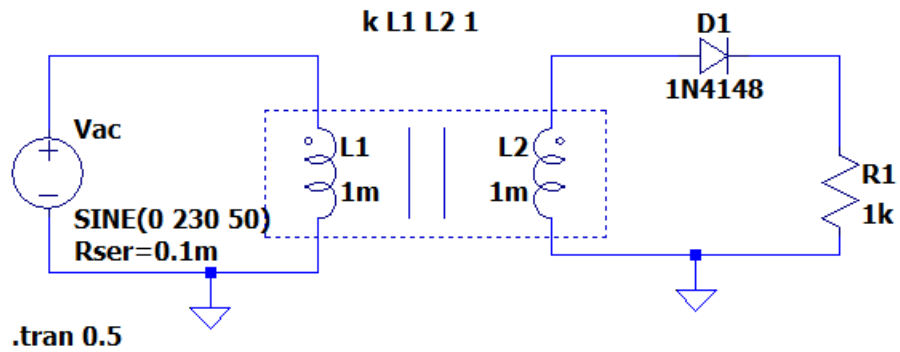


Output:

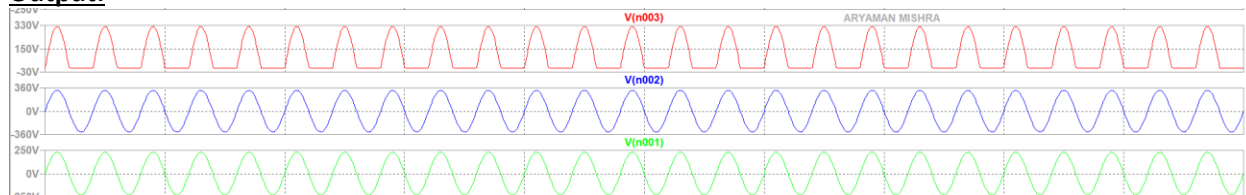


Task 1.3: n phase windings (1m:2m)

ARYAMAN MISHRA 19BCE1027 TASK 1

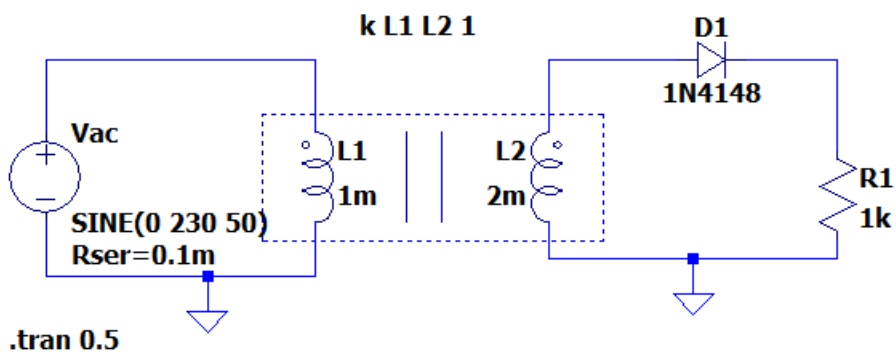


Output:

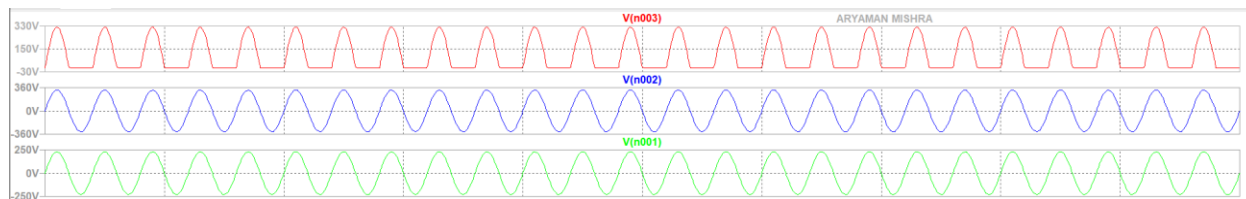


Task 1.4: 180° out of phase windings (2m:1m) 1.5

ARYAMAN MISHRA 19BCE1027 TASK 1

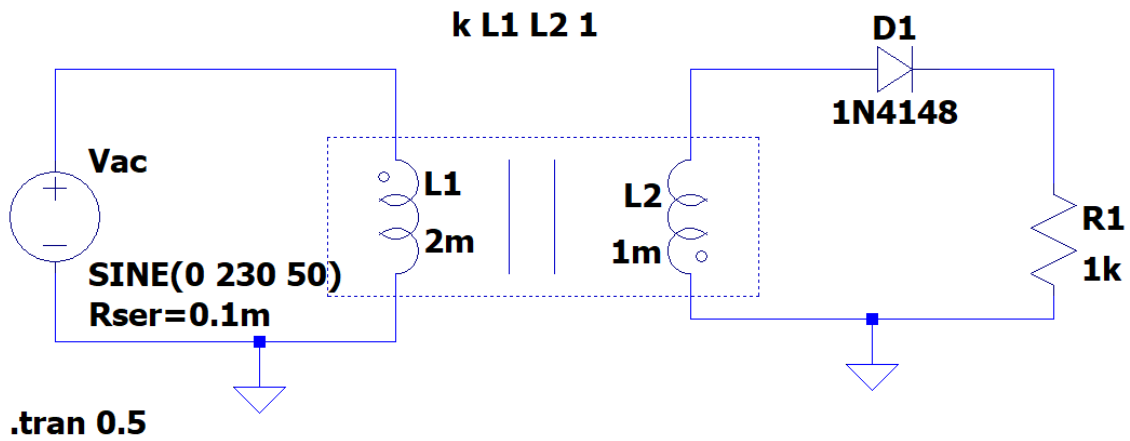


Output:

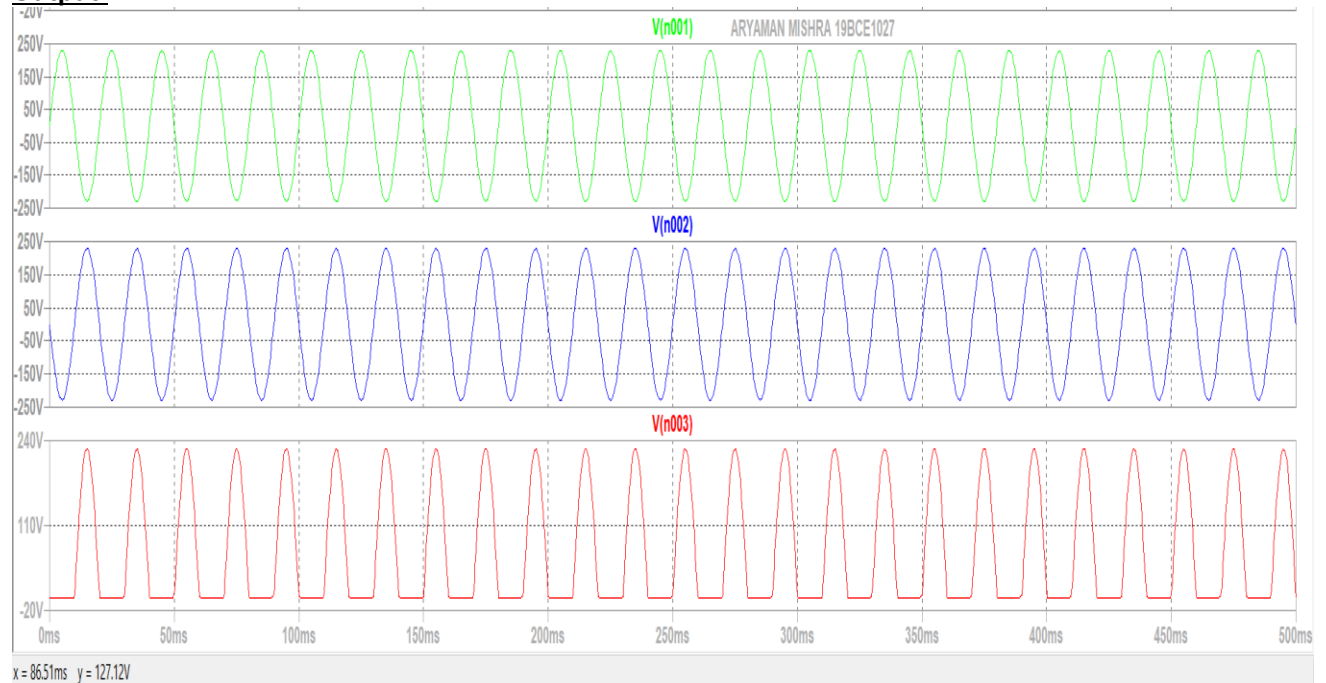


Task 1.5: 180° out of phase windings (1m:1m)

ARYAMAN MISHRA 19BCE1027 TASK 1

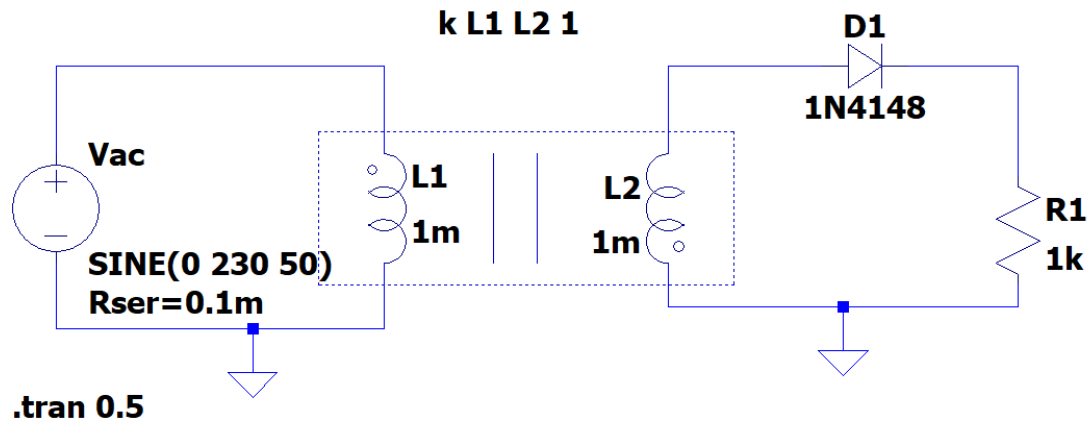


Output:

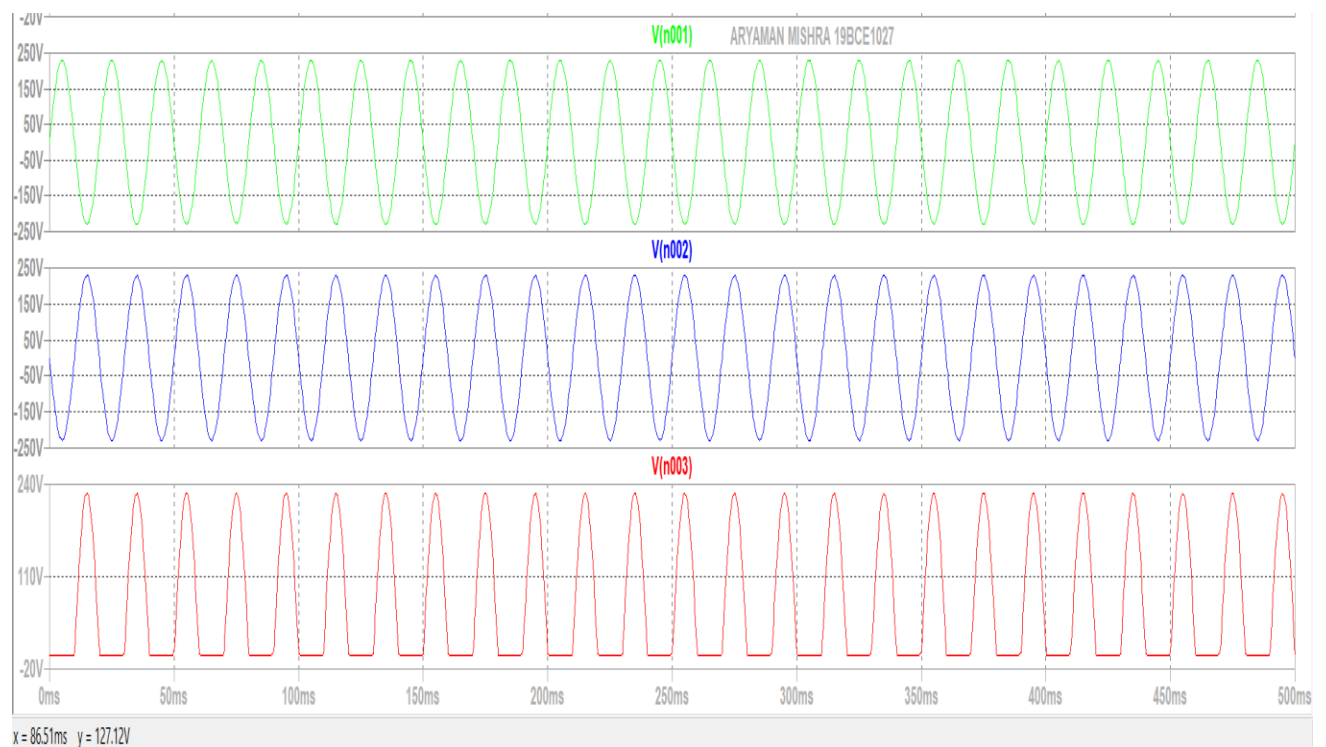


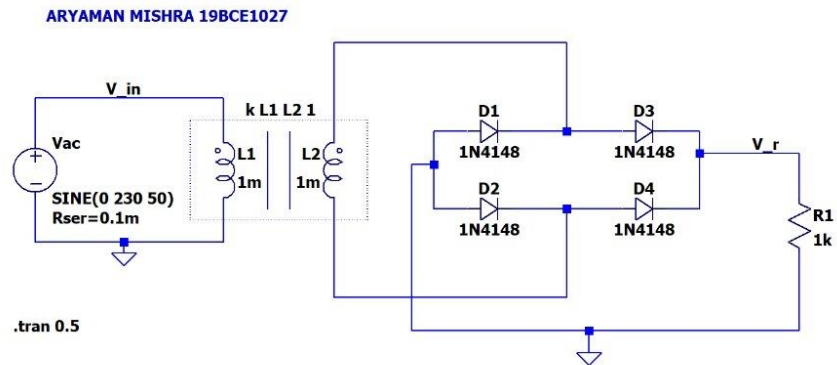Task#02: Full wave rectifier Design


Full wave rectifier and plot input voltage and output voltages : (across the load – resistor) with
2.1 In phase windings (1m:1m)




Output:

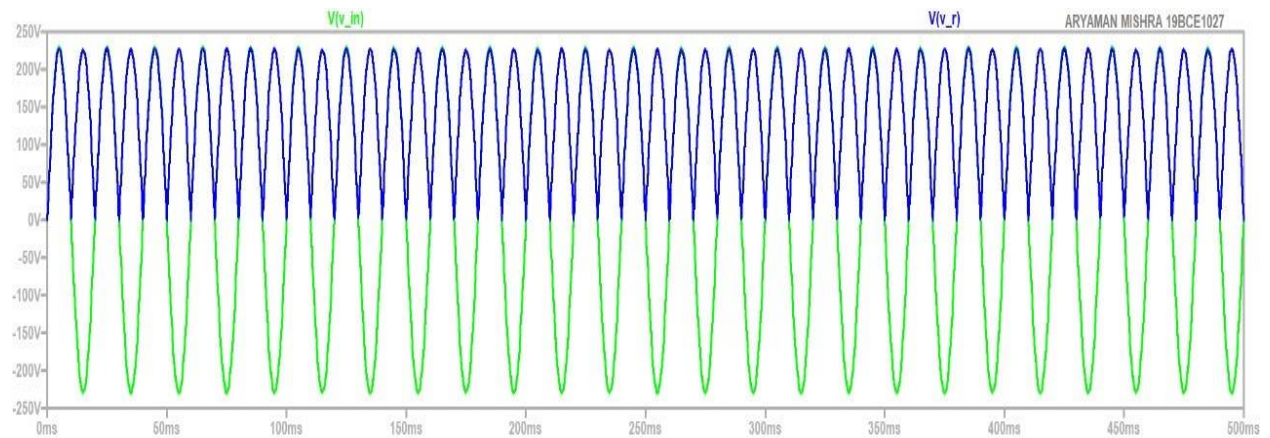

2.2 180° out of phase windings (1m:1m)

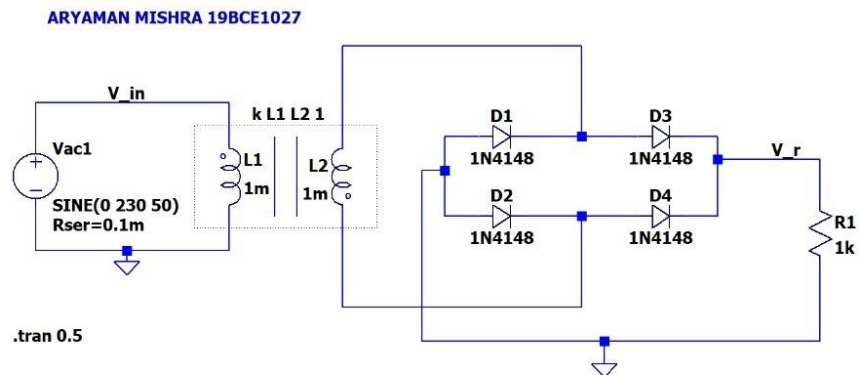

Output:

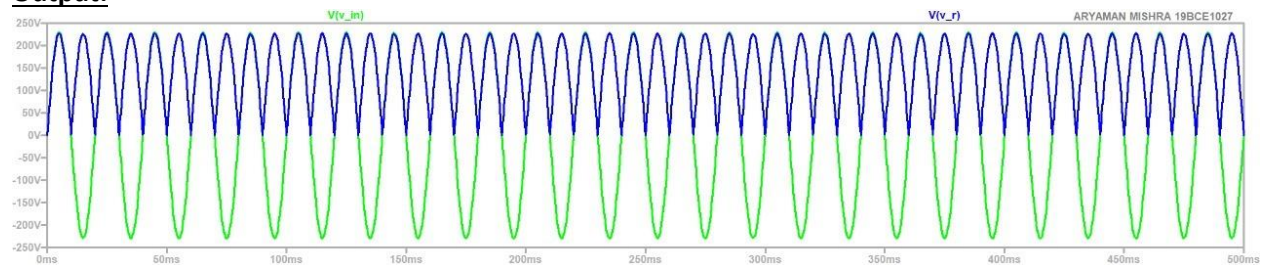


Task#03: DC Power supply

Obtain output voltage plot for the tasks

3.1 to 3.4 given in table below and enter observation

ARYAMAN MISHRA 19BCE1027

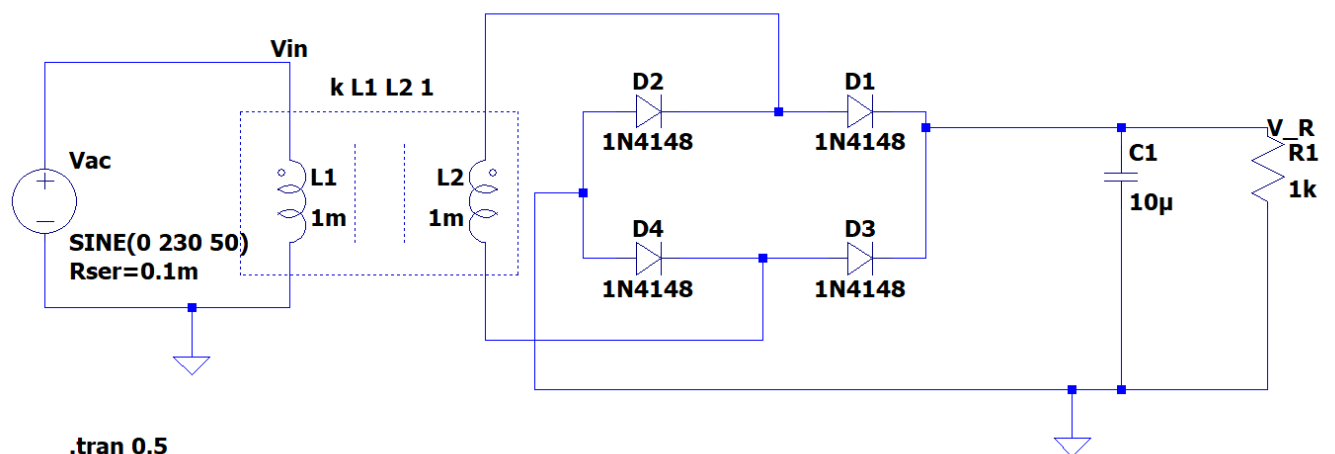


10uf = 122.498V, 226.589V
 1m = 223.709V, 225.405V
 100uf = 209.498 V, 227.85 V
 10m = 224.23V, 224.23V

Task	Capacitor	Comment on charging	Comment on discharging	Comment on attainment of 100% of peak of input and saturation (constant) of output.
3.1	10uF	Increased voltage	Decreased voltage	No voltage gets passed
3.2	100uF	Increased voltage	Decreased voltage	No voltage gets passed
3.3	1mF	Voltage remains same	Voltage remains same	No voltage gets passed
3.4	10mF	Voltage remains same	Voltage remains same	No voltage gets passed

Conclusion:We designed and simulated the clippers and clampers circuits using LTspice tool. Thus experiment is successfully completed.

Task#04: Design a DC Power supply of 5V

ARYAMAN MISHRA 19BCE1027

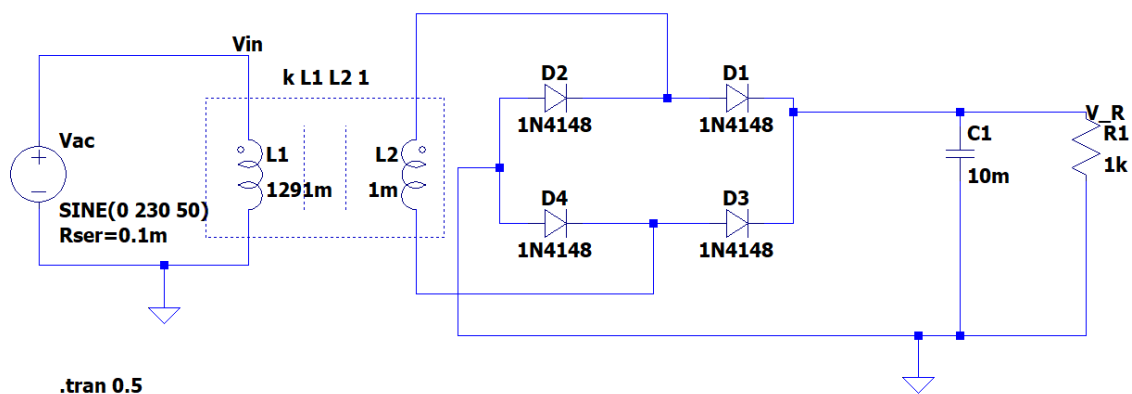

$$L_1:L_2 = V_1^2:V_2^2$$

$$\frac{L_1}{L_2} = \frac{2.30^2}{(5+1.4)^2} \quad \left(\begin{array}{l} \text{Voltage drops across diode} \\ \Rightarrow 0.7 \times 2 = 0.14 \end{array} \right)$$

$$\frac{L_1}{L_2} = \frac{1290.50}{1}$$

$$L_1 \approx 12.91 \text{ mH}$$

$$L_2 = 1 \text{ mH}$$

Conclusion: We designed and simulated the clippers and clampers circuits using LTspice tool. Thus experiment is successfully completed.