

# 9. Design of PCB for audio amplifier

**Course: ECE1008 – Electronic Hardware Troubleshooting LAB**

-Dr Richards Joe Stanislaus

Assistant Professor - SENSE

Email: 51749@vitstudent.ac.in



**VIT<sup>®</sup>**  


---

**Vellore Institute of Technology**  
(Deemed to be University under section 3 of UGC Act, 1956)  
CHENNAI



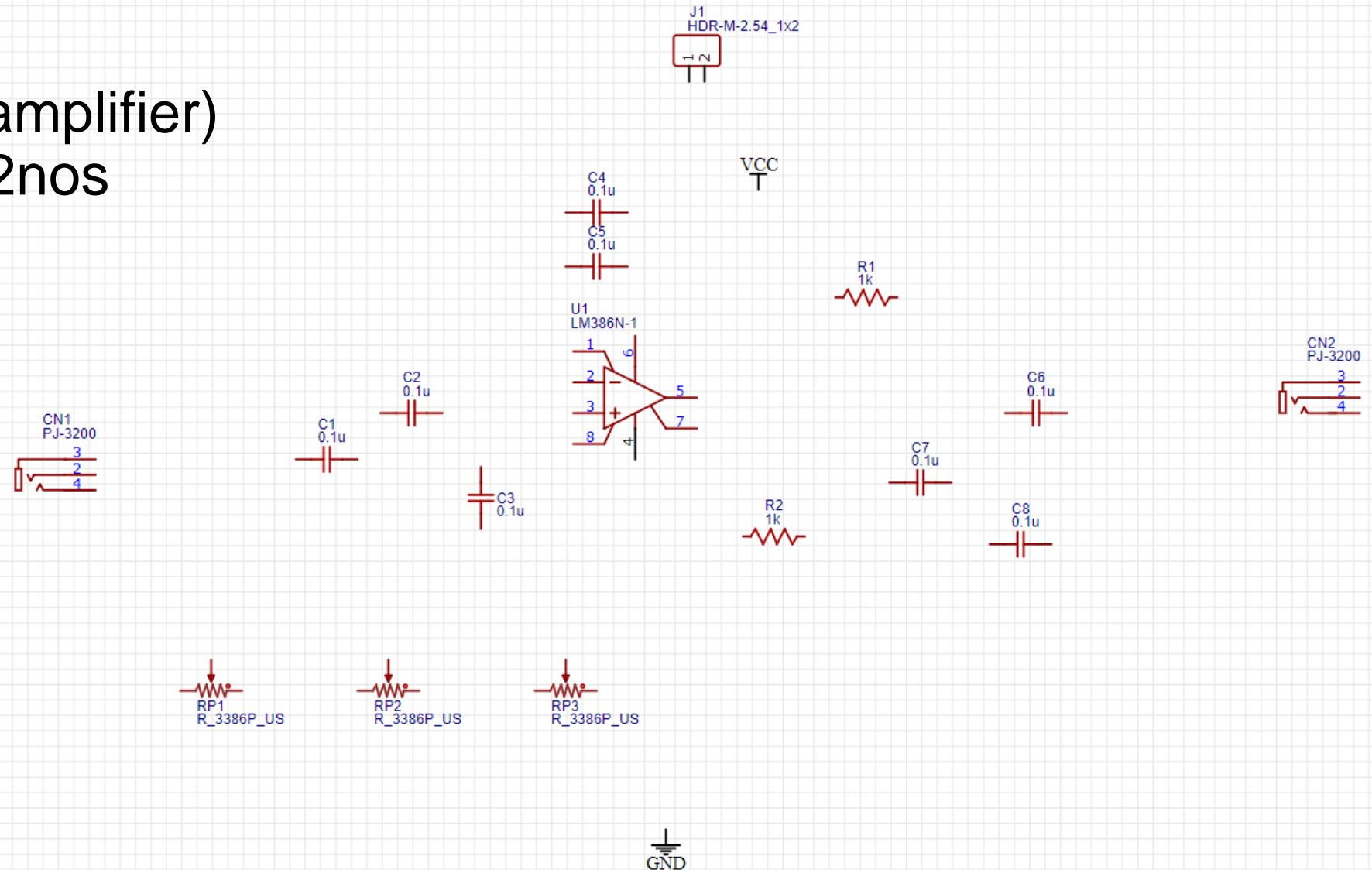
# 1. Place all the components from EELib or Library

- Library:  
LM386N-1 (Audio amplifier)  
PJ-3200 (Jack) - 2nos
- EELib:  
Connector (1x2) 1  
Capacitors: 8  
Potentiometers: 3  
Resistors: 2  
VCC  
GND


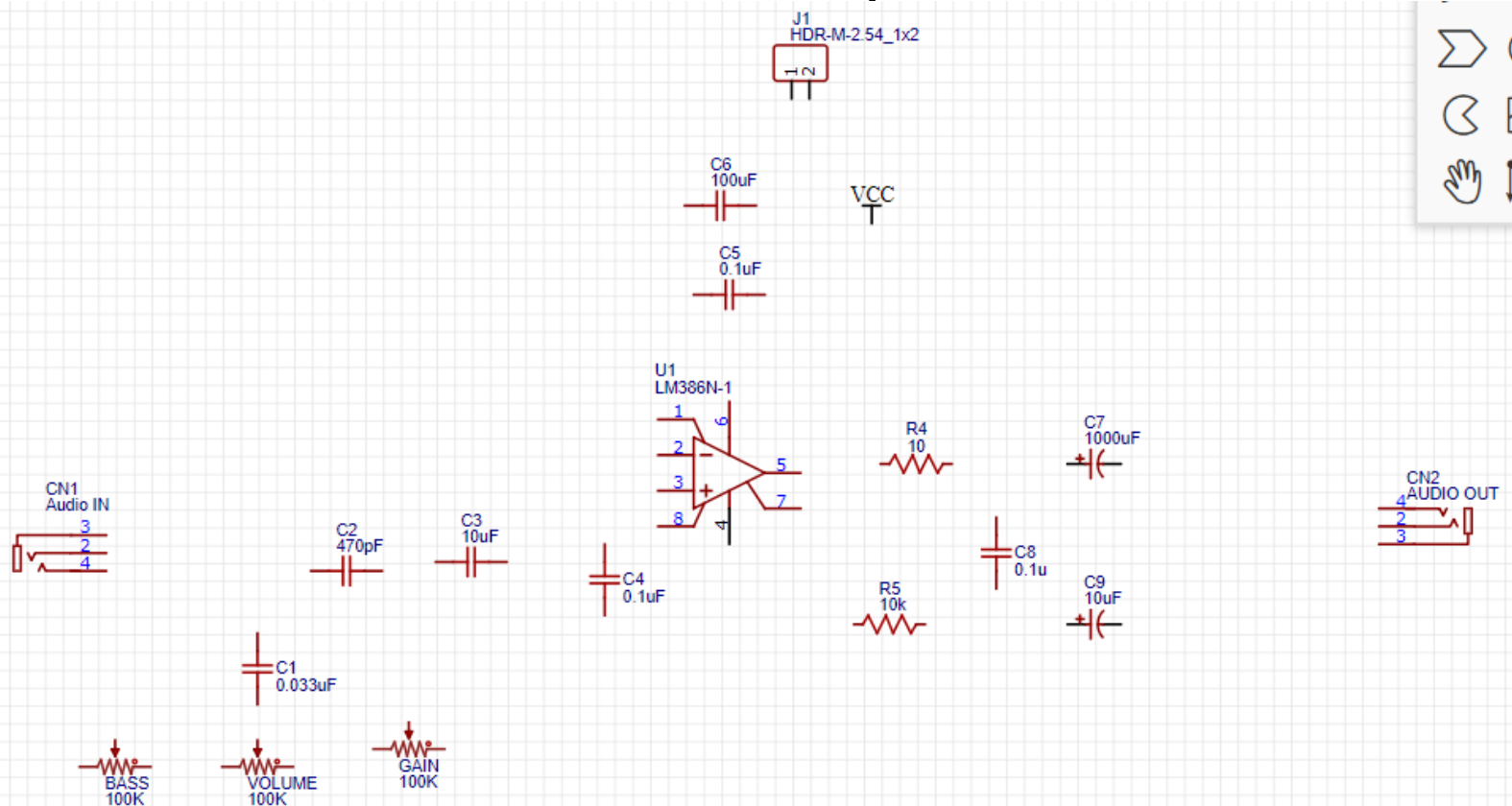
## 2. List of components selected for PCB

- First is Name  
Then either component name  
or Value and then component name



	BASS _ 100K _ POTENTIOMETER HEADER
	C1 _ 0.033uF _ C0603
	C2 _ 470pF _ C0603
	C3 _ 10uF _ C0603
	C4 _ 0.1uF _ C0603
	C5 _ 0.1uF _ C0603
	C6 _ 100uF _ C0603
	C7 _ 1000uF _ 1000UF 25V ELECTROLYTIC
	C8 _ 0.1u _ C0603
	C9 _ 10uF _ POLAR ELECTROLYTIC CAPACITOR
	CN1 _ Audio IN _ AUDIO-TH_PJ-3200
	CN2 _ AUDIO OUT _ AUDIO-TH_PJ-3200
	GAIN _ 100K _ POTENTIOMETER HEADER
	J1 _ HDR-M-2.54_1x2 _ HDR-M-2.54_1X2
	R4 _ 10 _ R0603
	R5 _ 10k _ R0603
	U1 _ LM386N-1 _ DIP-8_L10.0-W6.5-P2.54-LS7.1
	VOLUME _ 100K _ POTENTIOMETER HEADER

### 3. Connections in schematic

- IC's 1 goes to center of Gain and left of Bass
- 2 is grounded
- 3: Center of Volume and right of C2(470pF)  
left of C2 (470pF) to ground
- 4: Ground and bottom of C4(0.1uF)
- 6: to top of C4(0.1uF); VCC; Port J1's 2
- 5: Left of R4 (10) and to top of C1 (0.033uF)  
bottom of C1 (0.033uF) to center of BASS  
Right of R4 to left of C7(1000uF)  
Right of C7(1000uF) to 2 of Audio Out.  
Right of R4 to top of C8 (0.1uF)  
bottom of C8(0.1uF) to ground.




### 3. Connections in schematic

- 7: left of R5 (10K)  
Right of R5(10K) to left of C9(10uF)  
Right of C9(10uF) to ground
- 8: Right of C3(10uF)  
Left of C3(10uF) to Left of GAIN
- Right of Volume to Ground  
Left of Volume to Center(2) of AUDIO IN.  
4 of AUDIO IN to ground.
- 4 of AUDIO OUT to Ground
- Right of both C5(0.1uF) and C8(100uF) to VCC  
Left of both C5(0.1uF) and C8(100uF) to Port J1's 1 and Ground




# 3. Connections in schematic

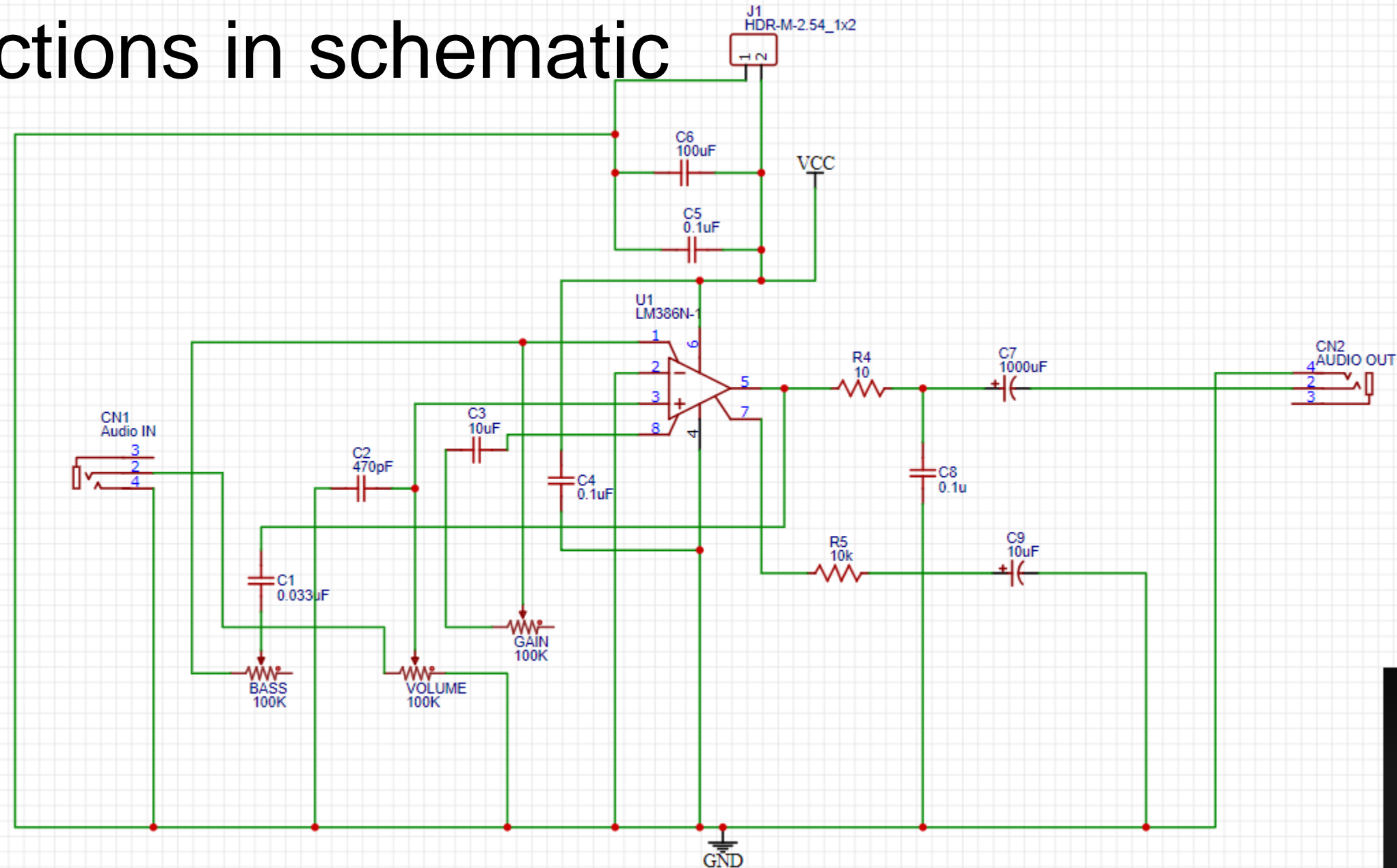

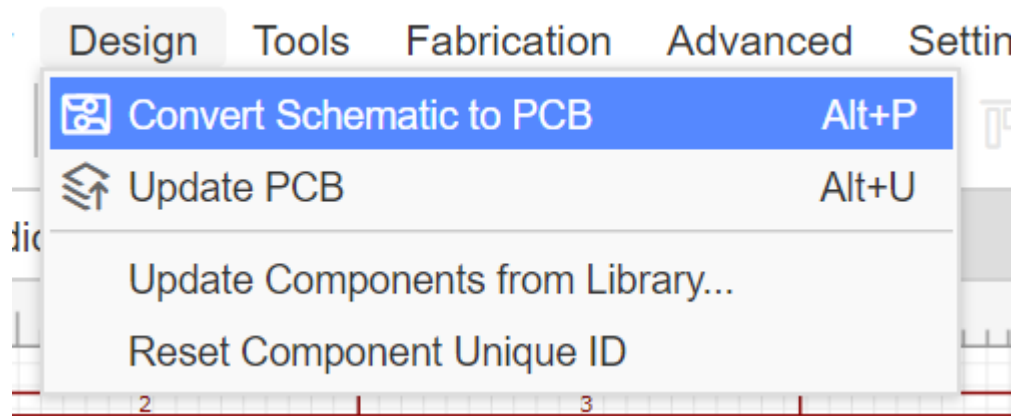
# 4. Conversion to PCB

- Click convert schematic to PCB and click No keep going and apply




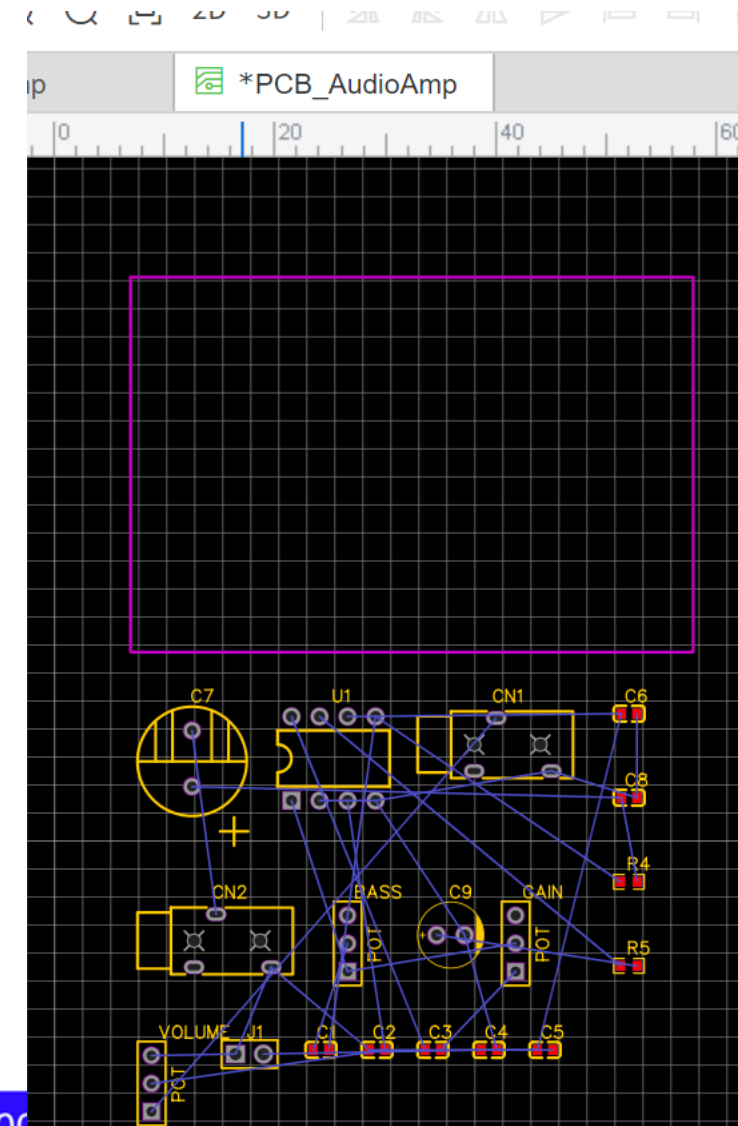- All footprints are transferred to PCB with virtual wires for connections
- Need to move components to PCB


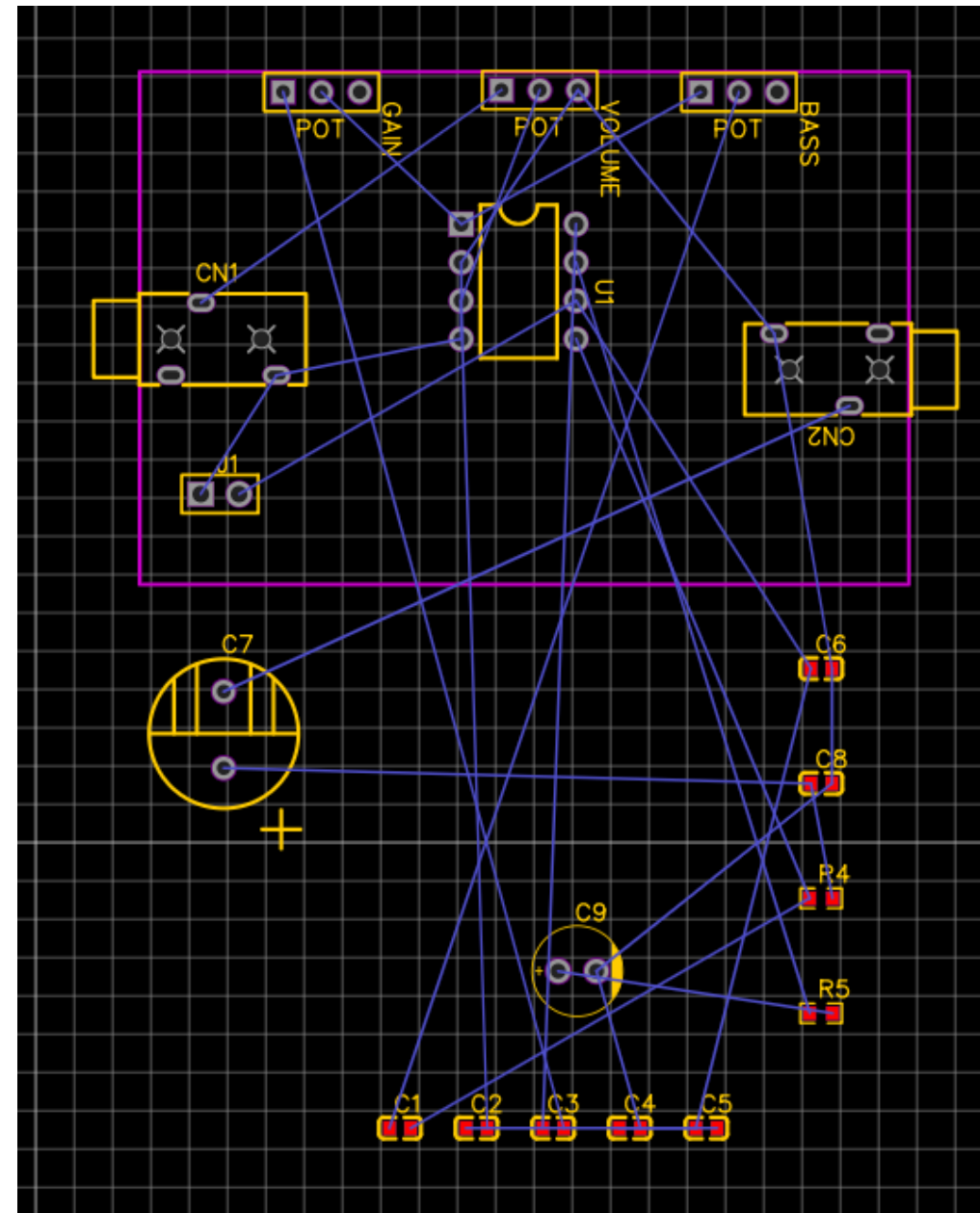
# 5. Arrange in PCB



- Try to arrange properly without zig-zag paths
- Try for Star configuration with supply  
From supply to all components
- Place all components in close proximity, to reduce the radiation from the connection lines.






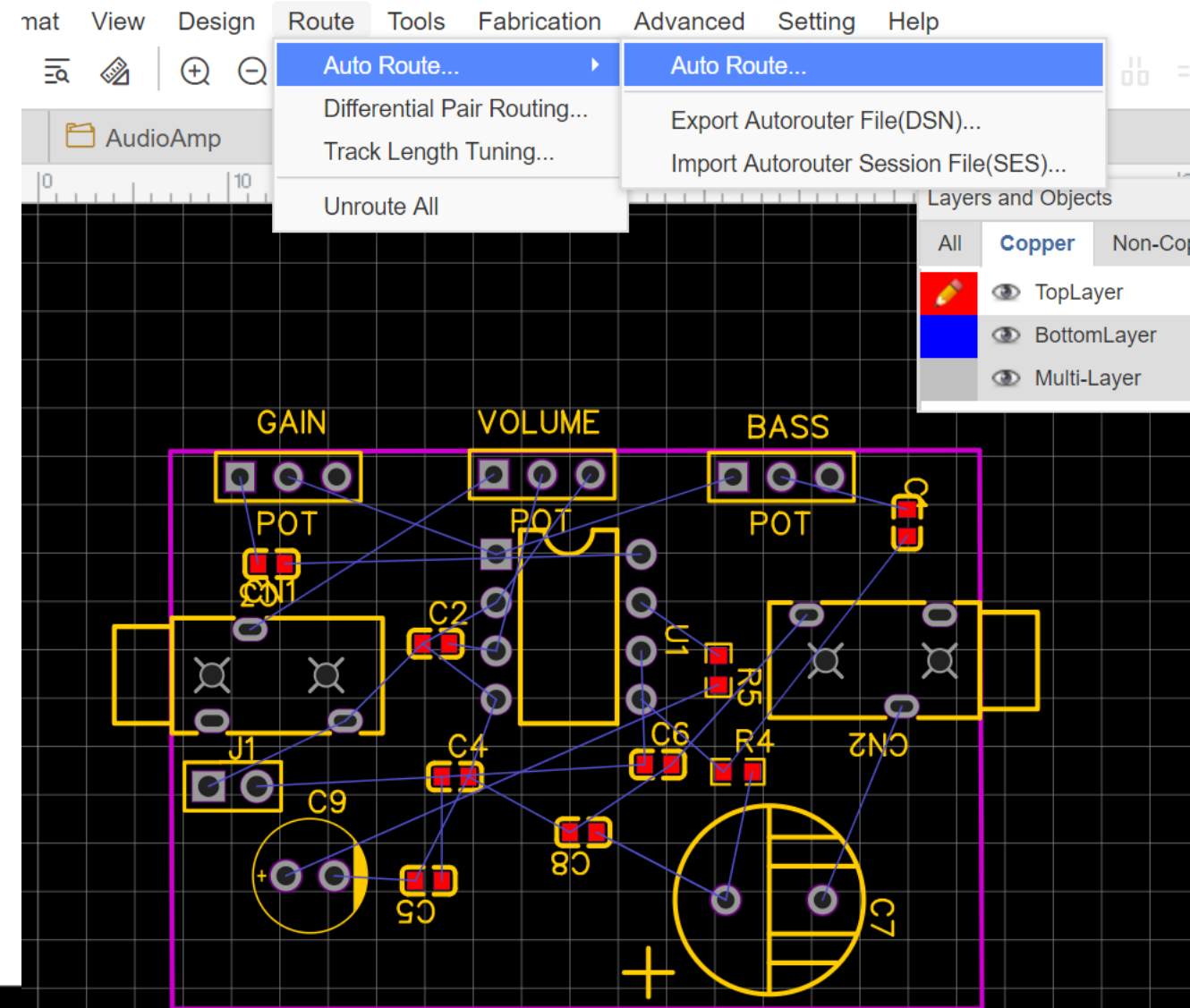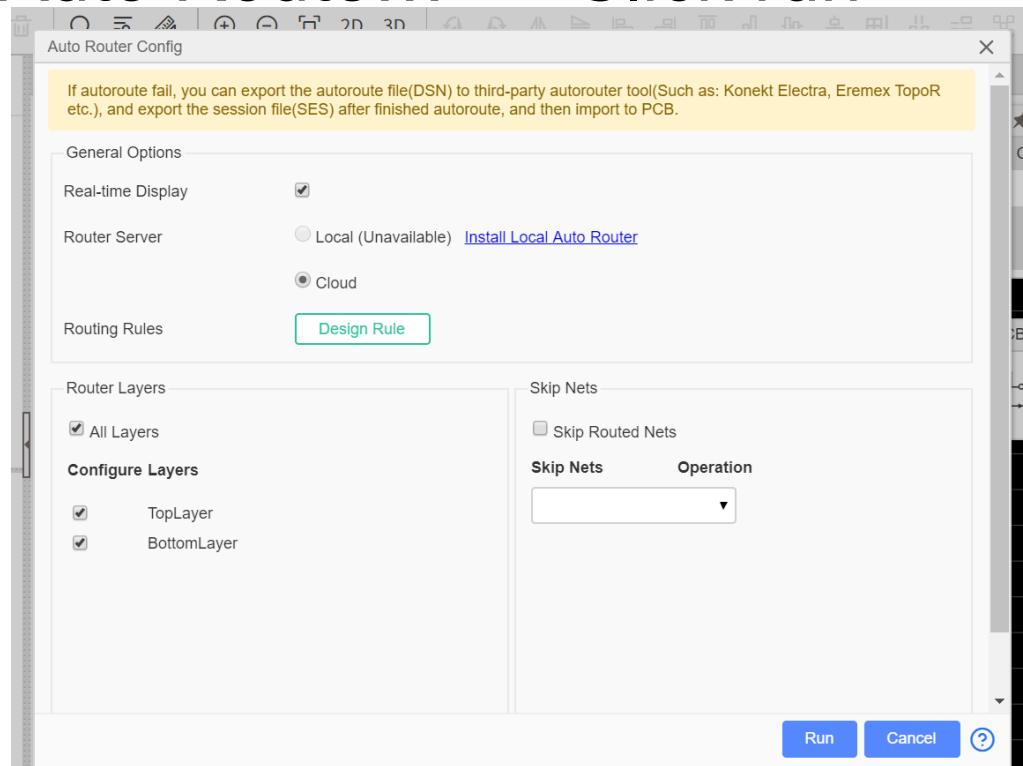
# 5. Arrange in PCB


- Save the circuit
- After arranging components, Route-> Auto Route -> Auto Route... Click run




# 5. Arrange in PCB

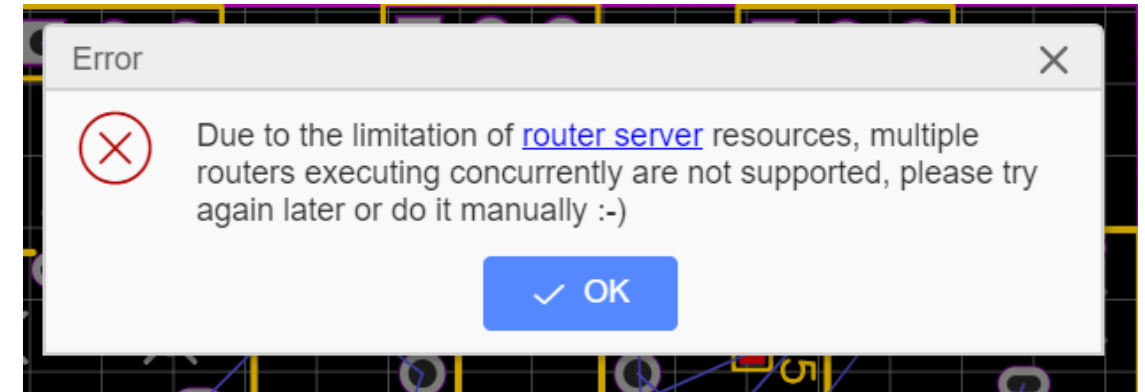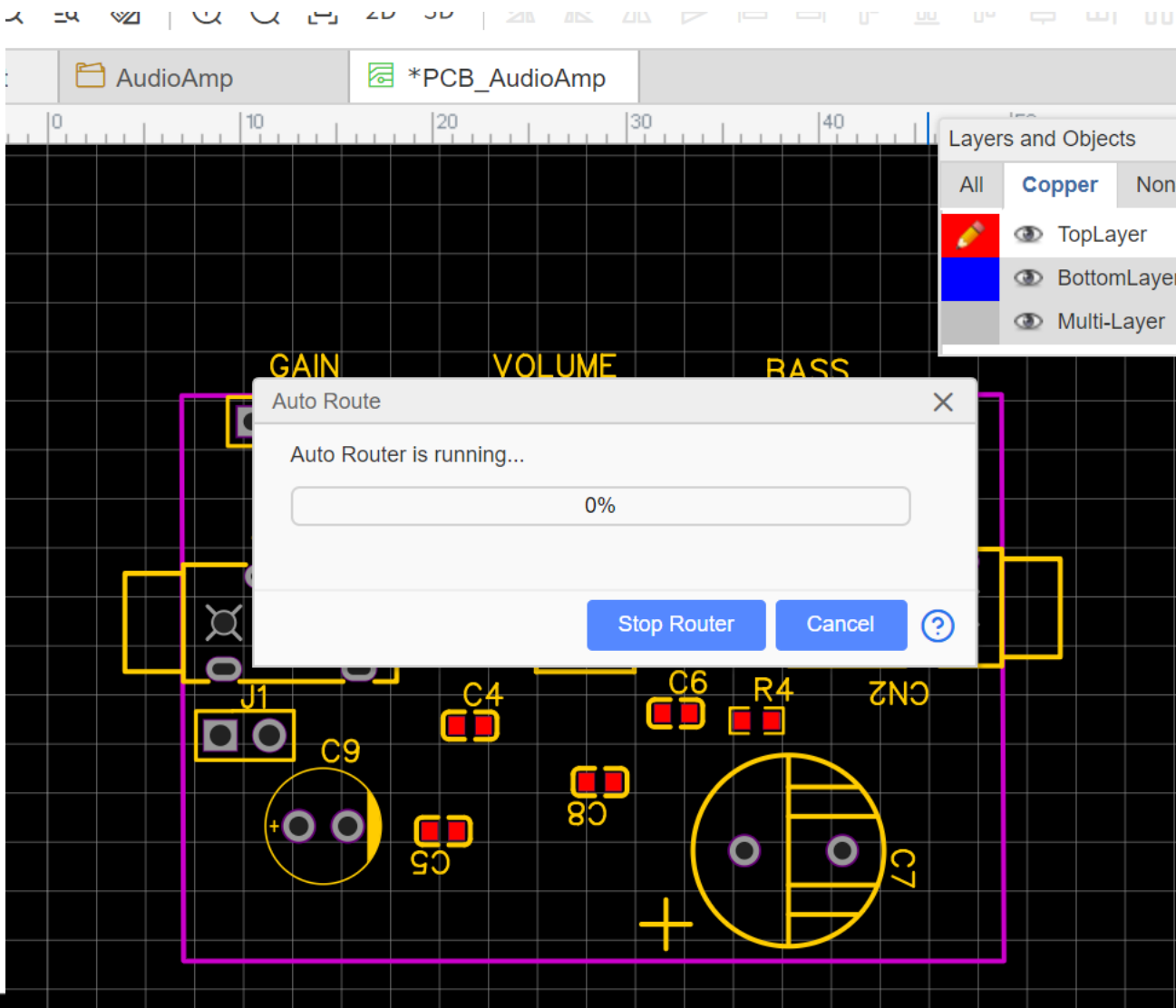

If error comes, then repeat until:

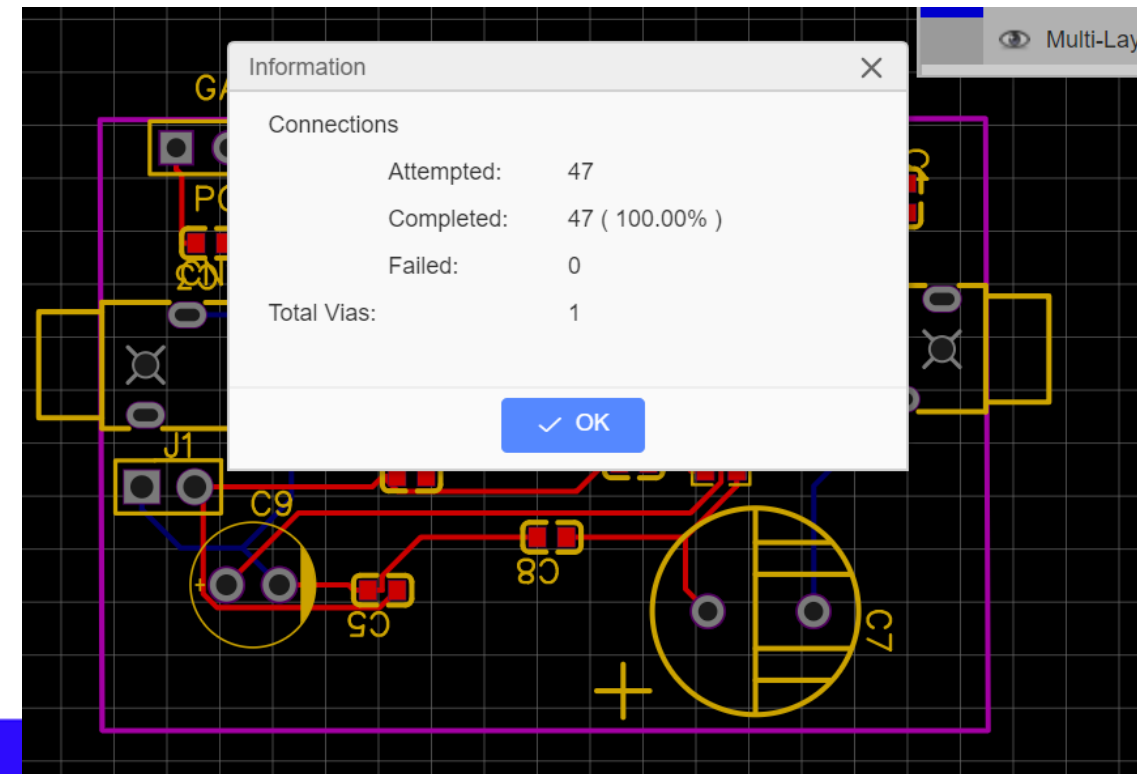


# 5. Arrange in PCB

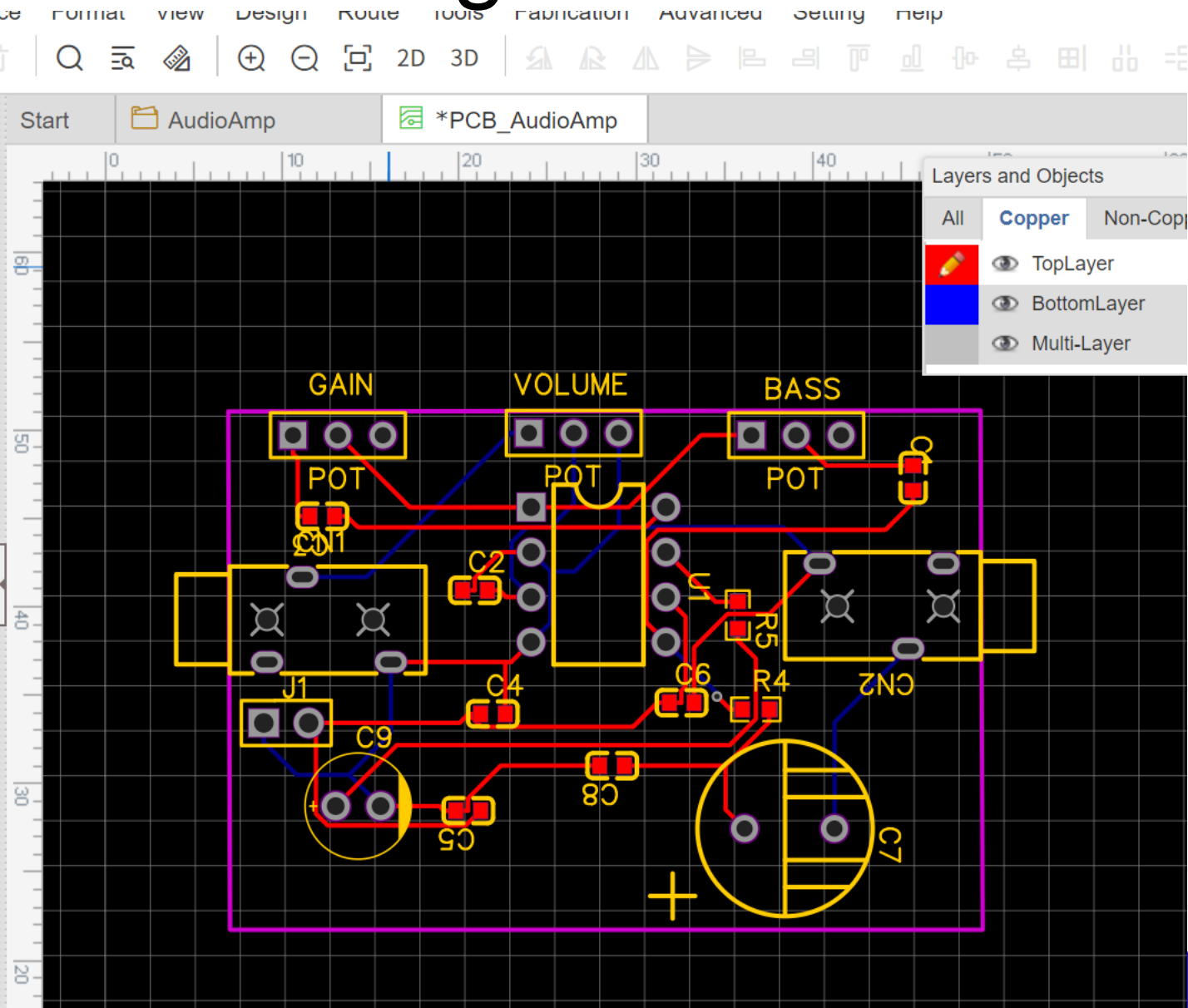

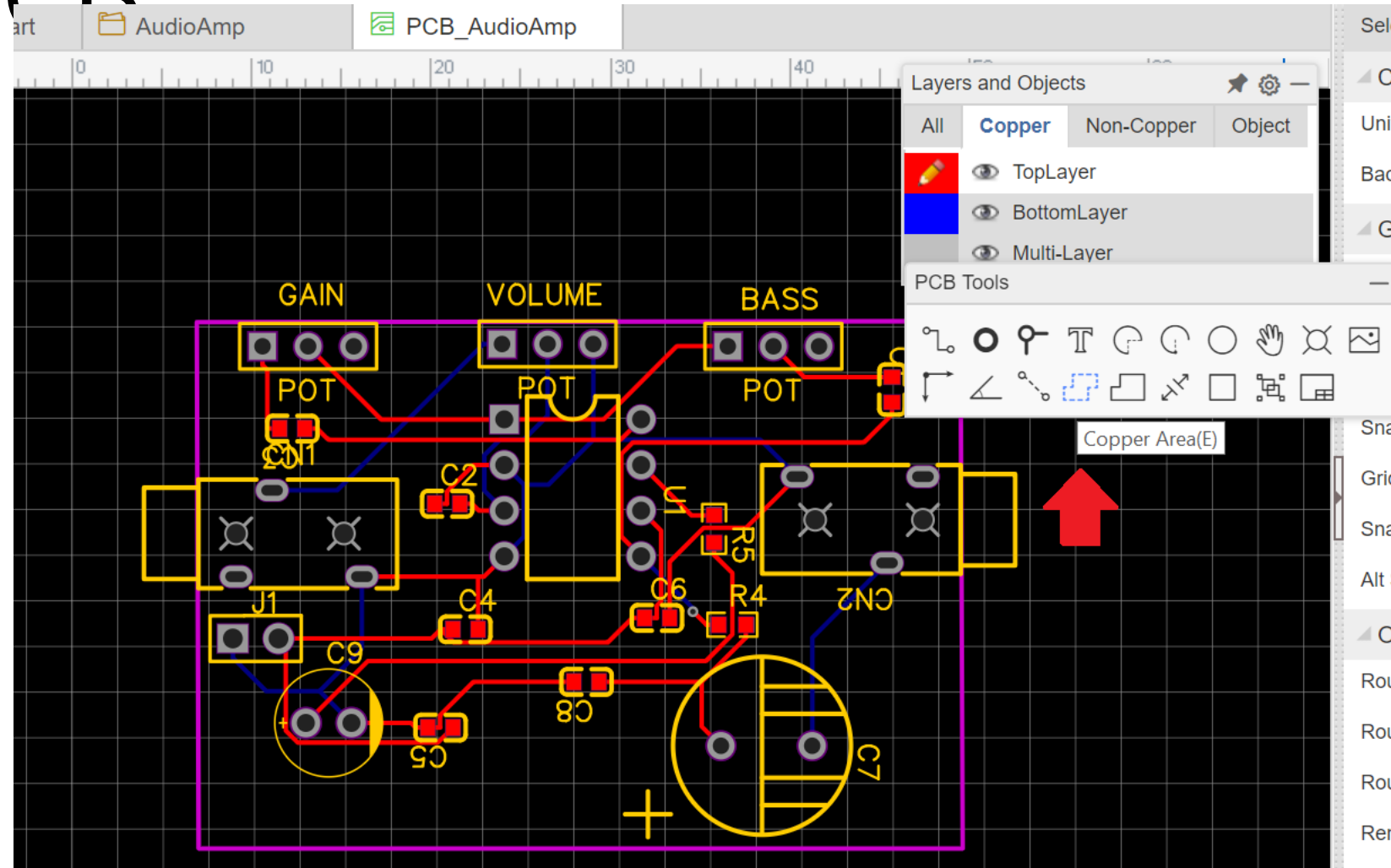
# 5. Arrange in PCB

- Select copper area  
Select all four corners  
and  
complete the ground



# 5. Arrange in PCB

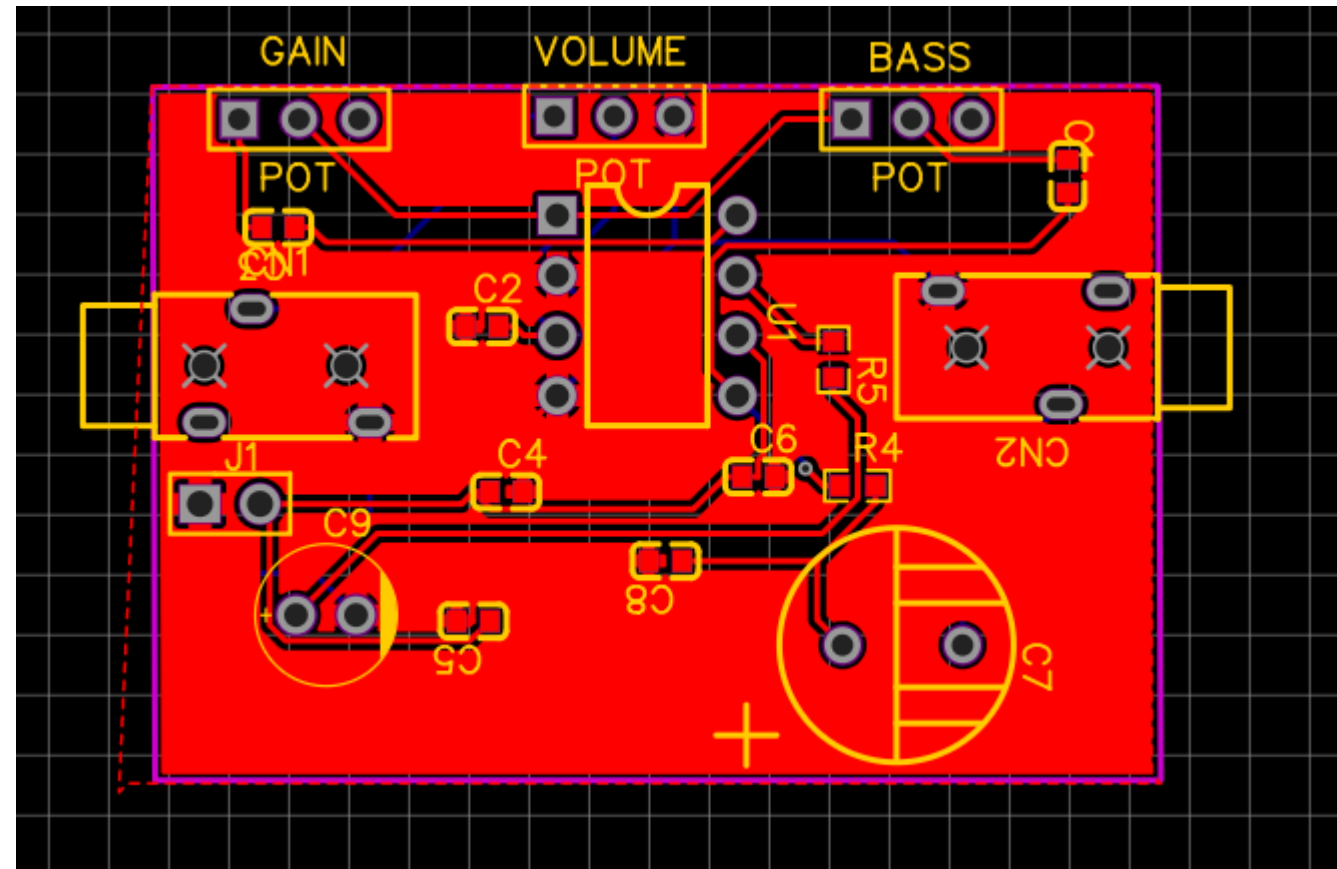

# Important NOTE

- Enter your **registration number** and **Full Name** next to **all your circuits, PCB** and the **output plots**.



# LAB record instructions:

For the lab experiment,

- Write the **Aim**.
- Complete the **Software/Hardware components used**.
- **Obtain the expression for the outputs.**
- Place the respective **circuits in EasyEDA**.
- Connect the inputs and outputs. Name them and **write the same in the lab copy(inputs and outputs section)**.
- Use probe in LT spice to plot all possible combinations.
- Write a **concluding statement for each circuit**.
- **Submit** the document's soft copy **on time** in [lms.vit.ac.in](https://lms.vit.ac.in) when available.

