

Name: Aryaman Mishra
Reg. no: 19BCE1027
Date: 08-11-2021

EXPERIMENT NO: 11
Design and analysis of Emergency Lamp


Aim: To design an emergency lamp in LTSpice with the following specifications: Input: 230V 50Hz ac supply Battery: 4.8V (four 1.2 V batteries connected in series) 2 LEDs (in series): NSCW100 with 5 V breakdown voltage.

Software used: LTSpice


Components required: Resistors, voltage source, NMOS, PMOS, inductor and capacitor.

Task 1: Design the input Supply unit with switch control.

Circuit:

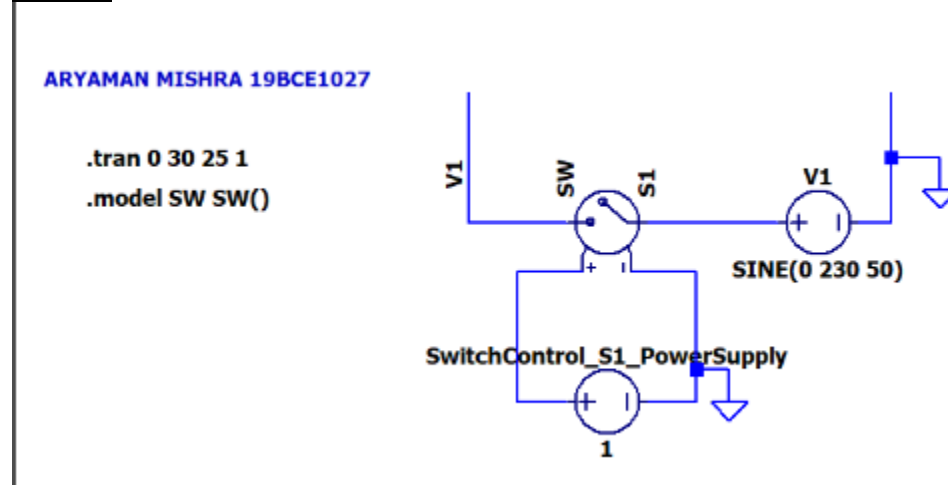

Output:

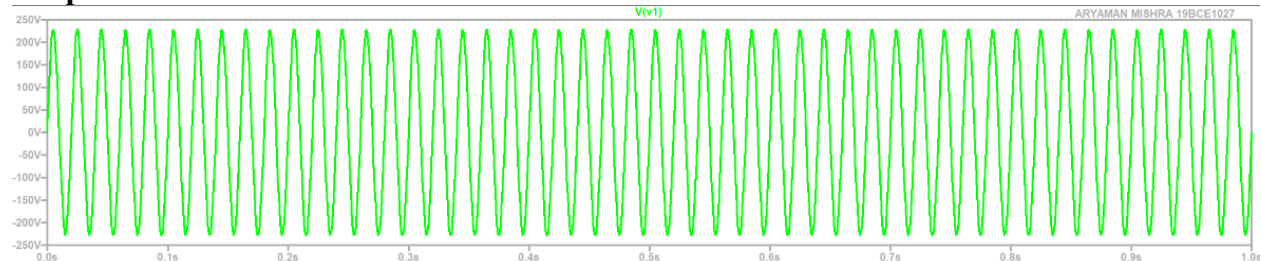


Result: Thus we have plotted voltage V1 using switch control S1.

Task 2: Design the step down transformer for reduced V2 voltage.


Circuit:

ARYAMAN MISHRA 19BCE1027
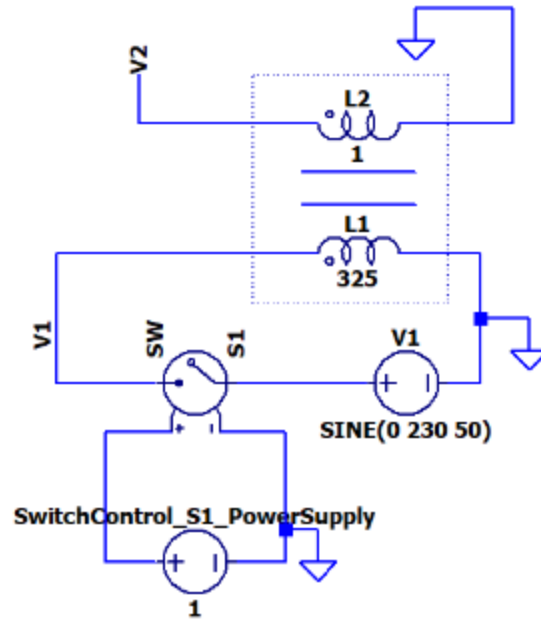
```
.tran 0 10 9 1  
.model SW SW()  
K L1 L2 1
```



Output:

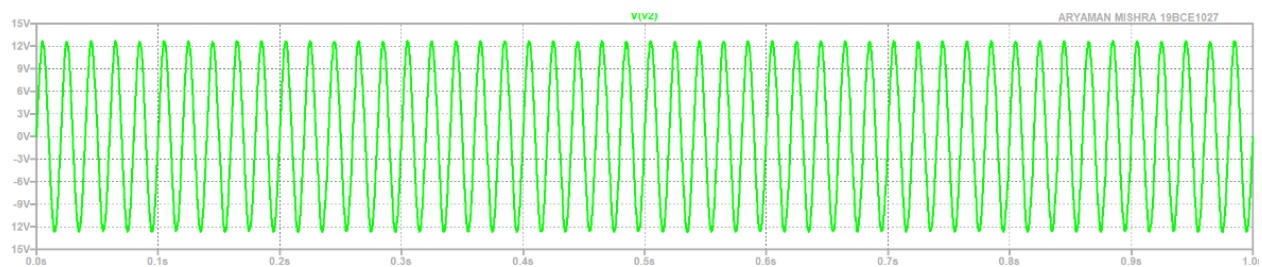


Result: From the graph we can observe that the voltage is reduced from 230v to 13v using step down transformer

Task 3: Design of Bridge rectifier circuit (without Capacitor).


Circuit:

ARYAMAN MISHRA 19BCE1027
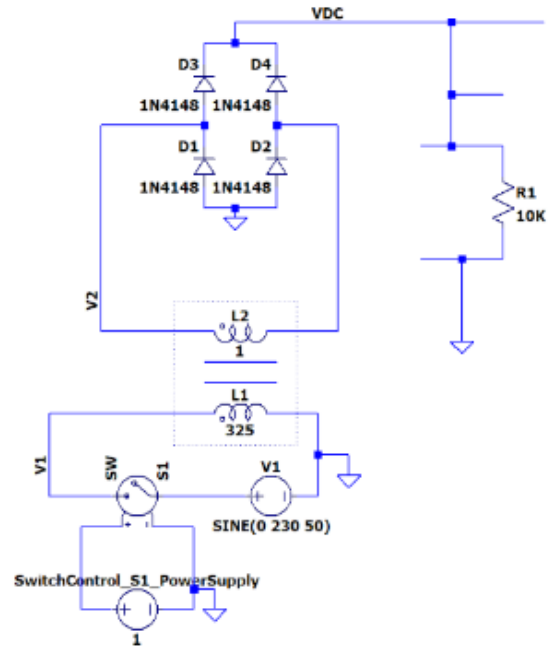
```
.tran 0 10 9 1  
.model SW SW()  
K L1 L2 1
```



Output:

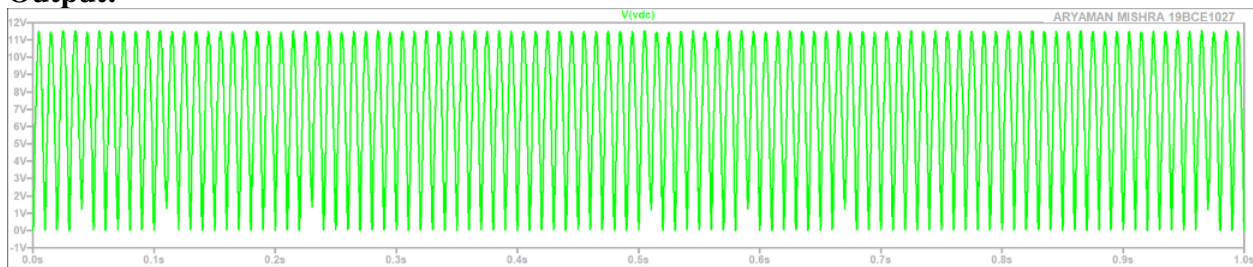


Result: Thus we plotted the voltage VDC without using capacitor.

Task 4: Design of Bridge rectifier circuit (with Capacitor).


Circuit:

ARYAMAN MISHRA 19BCE1027
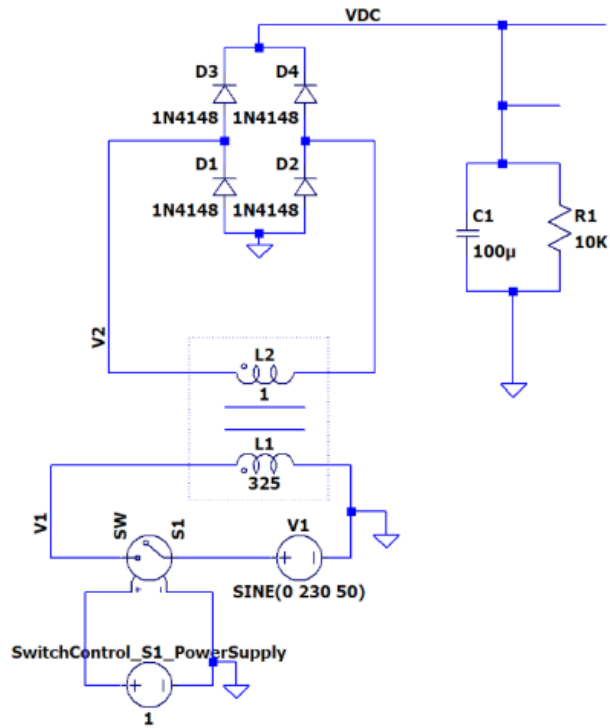
```
.tran 0 10 9 1  
.model SW SW()  
K L1 L2 1
```




Output:

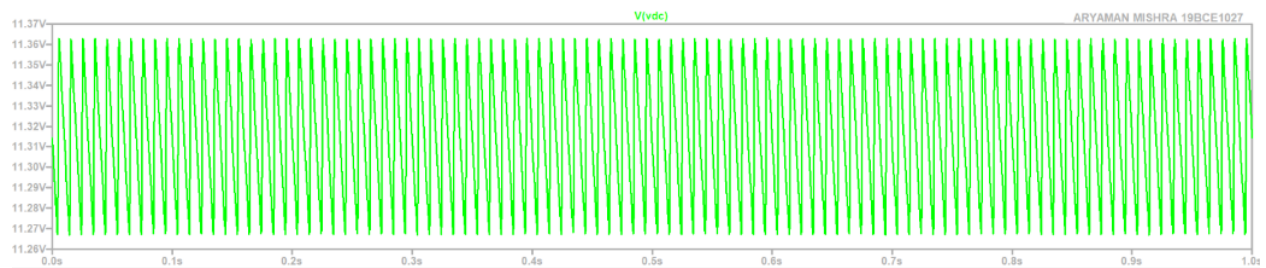

Result: Thus we have plotted the voltage VDC using capacitor of 100uf.


Task 5: Design of Charging circuit from 12V DC input supply.

Circuit:

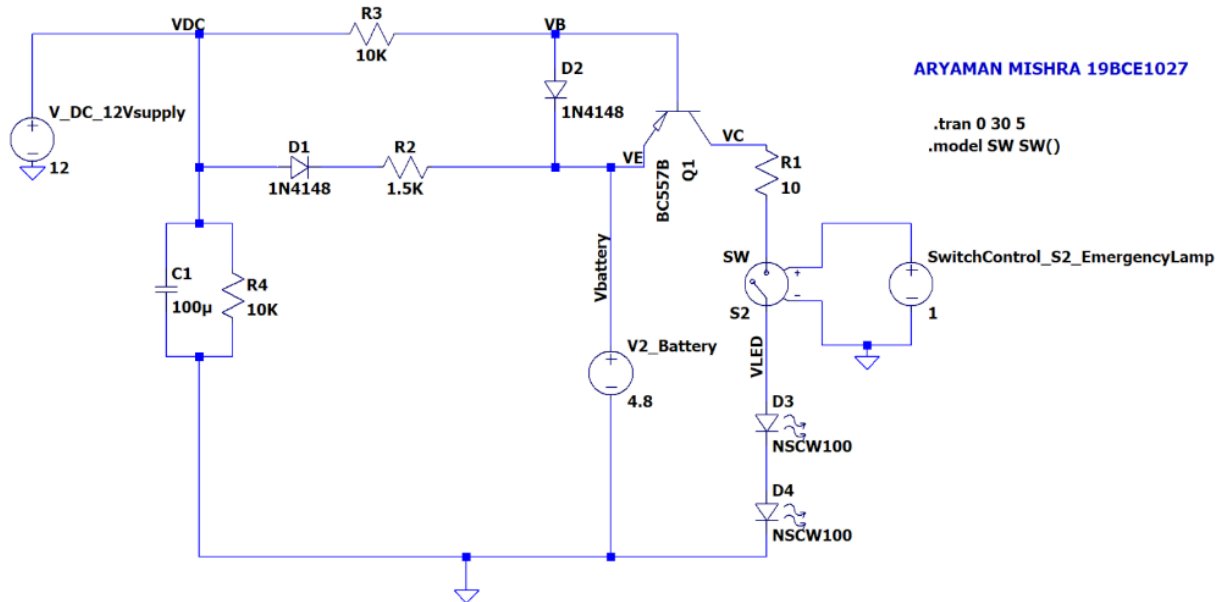


Output:

Case 1: Input DC is on:

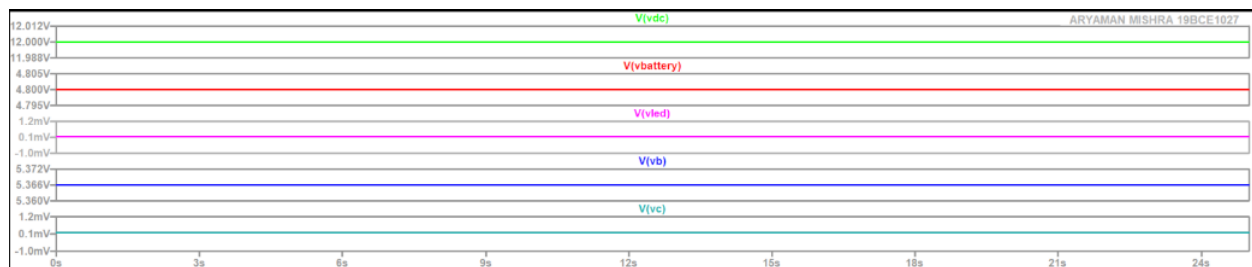

Case 2: Input DC is off:

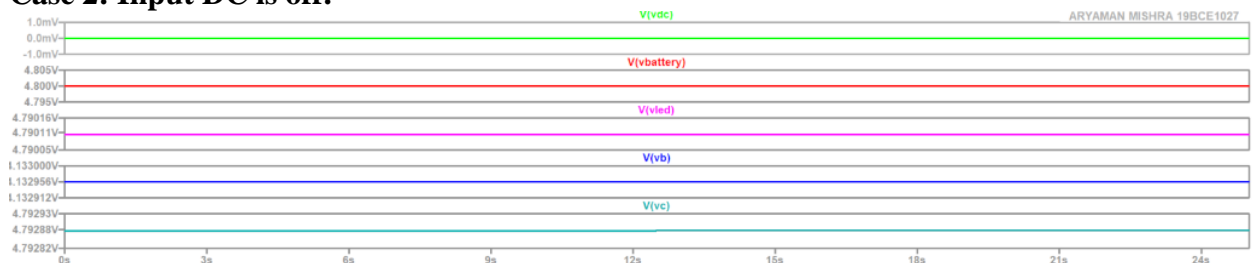


Result: From the plots we can observe that when the DC voltage is 12v which is given as a input supply $V_{DC}=12v$ and $V_e=V_{battery}$ is 4.8v $V_{led}=V_c=0.1mv$ so LED is almost in off state.

When the input supply is 0V VDC is 0 so the diodes are reverse biased and Vbattery value is given to Vc results it into turning ON the LED.


Task 6: Integrate Bridge circuit to Emergency Lamp: Complete the circuit

Circuit:

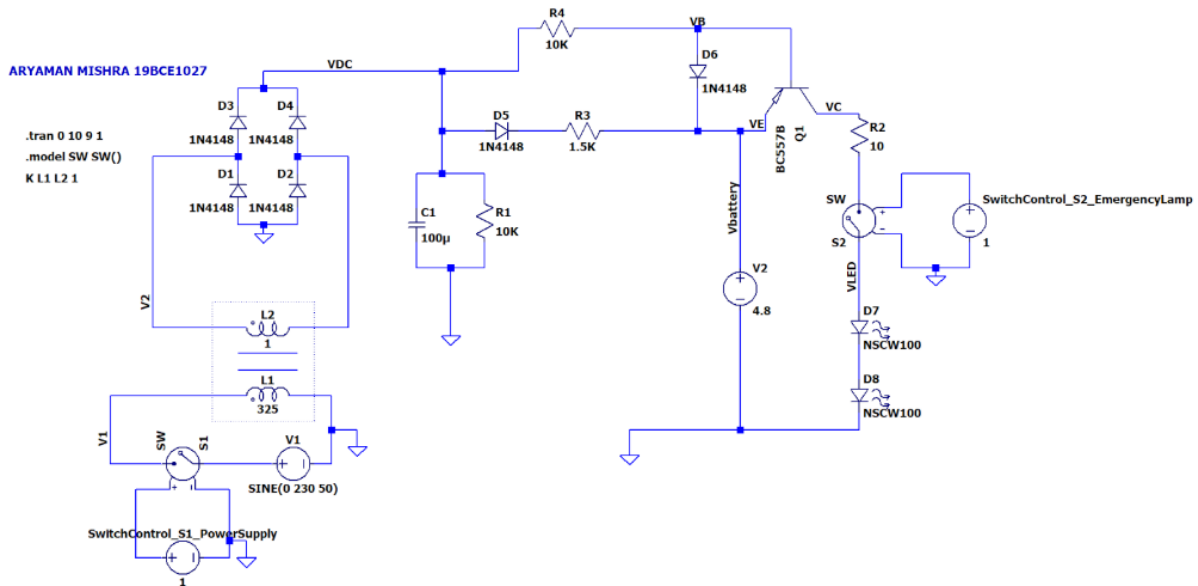


Output:

Case 1: With S1 ON, S2 ON:

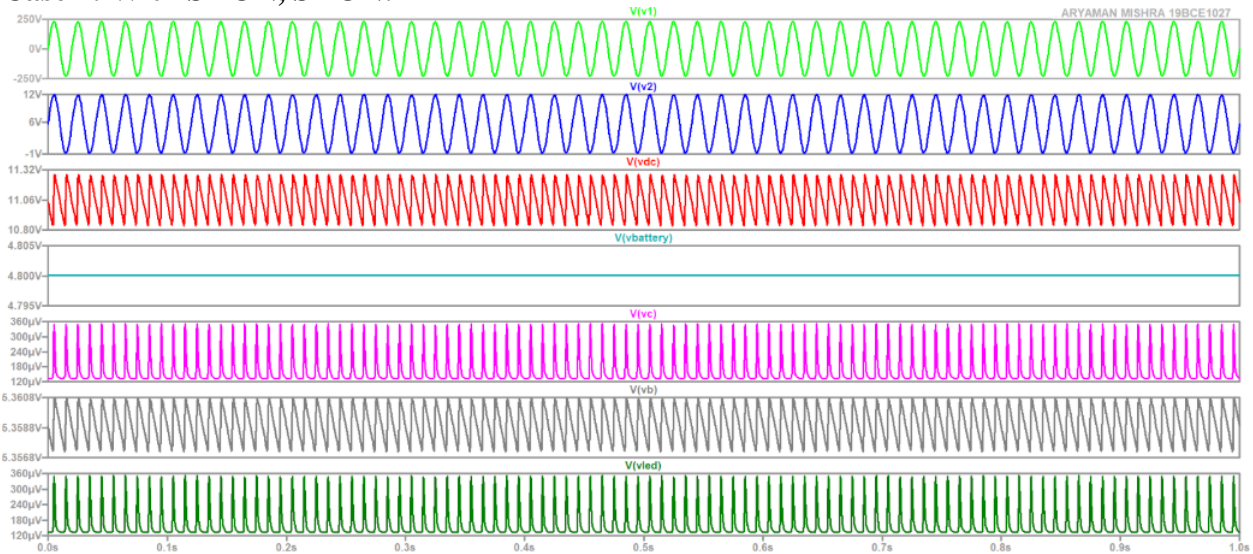


Result: Thus we have plotted the graph of where both S1 and S2 are on, we can observe that Vc and VLED are equal.

Case 2: With S1 OFF, S2 ON:

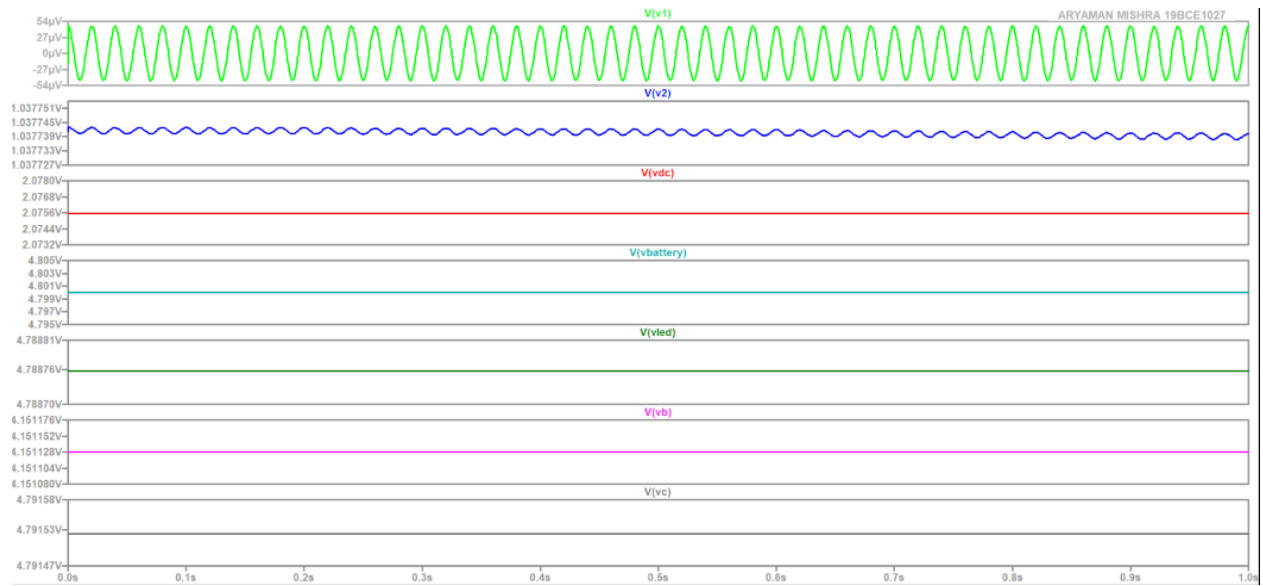

Result: Thus we have plotted the graph when the S1 is off and S2 is in on condition, here also we can observe that Vc and VLED are equal

Case 3: With S1 OFF, S2 OFF:

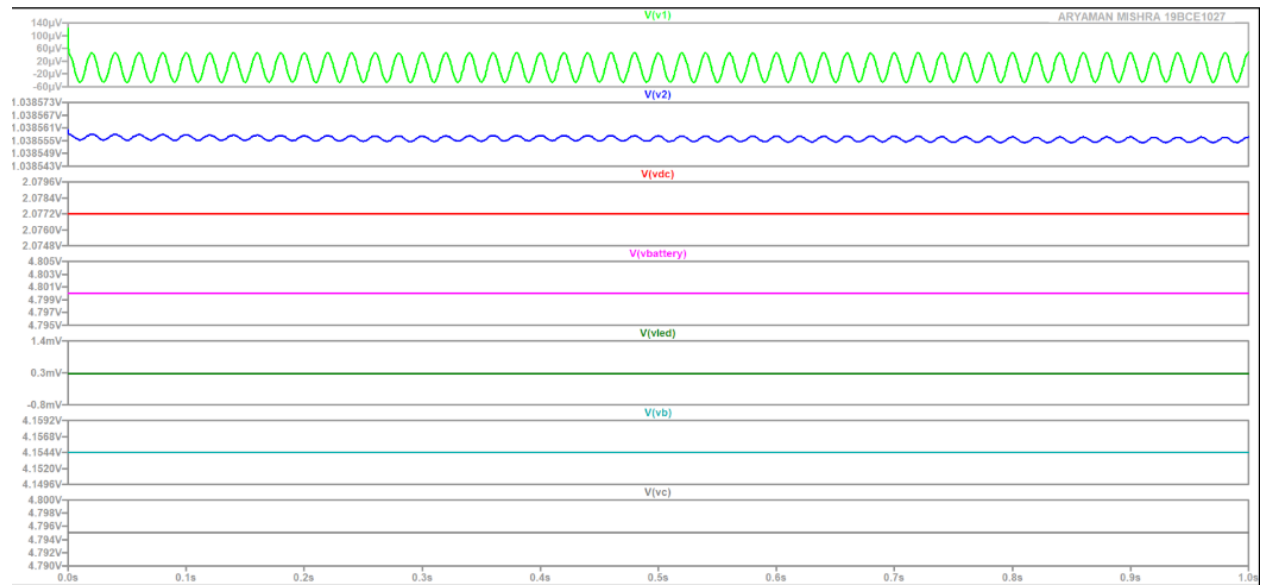

Result: Thus we have plotted the graph when the both switches are in off, here Vc and VLED are not equal