

**Aryaman Mishra**

**19BCE1027**

**Date-6/12/21 LAB FAT**

**Aim:**


For an input sinusoidal voltage of 120V(peak), obtain a full wave rectified output voltage with a peak value of 28.8V. Obtain the turns ratio of the transformer to be used in the circuit. Note: Use 1N4148 diodes.


**Software used:** LTSpice

**Components required:** Resistors, voltage source, inductors, diode.

**Circuit:**



ARYAMAN MISHRA 19BCE1027 LAB FAT 6-12-21

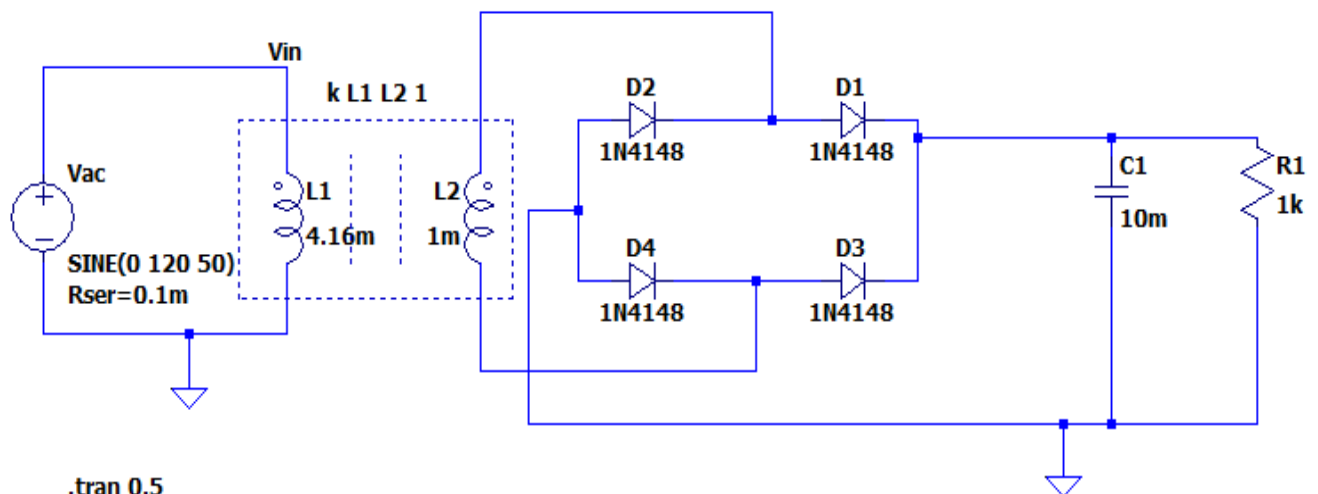

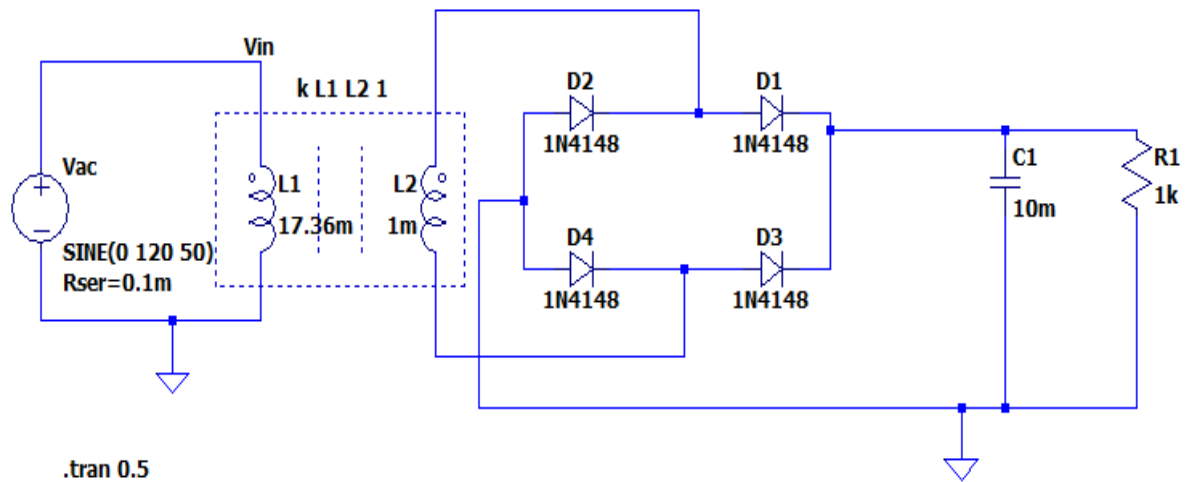


**Output:**

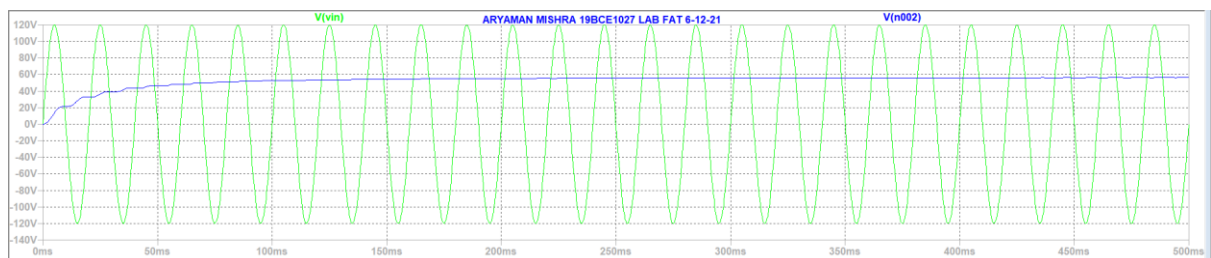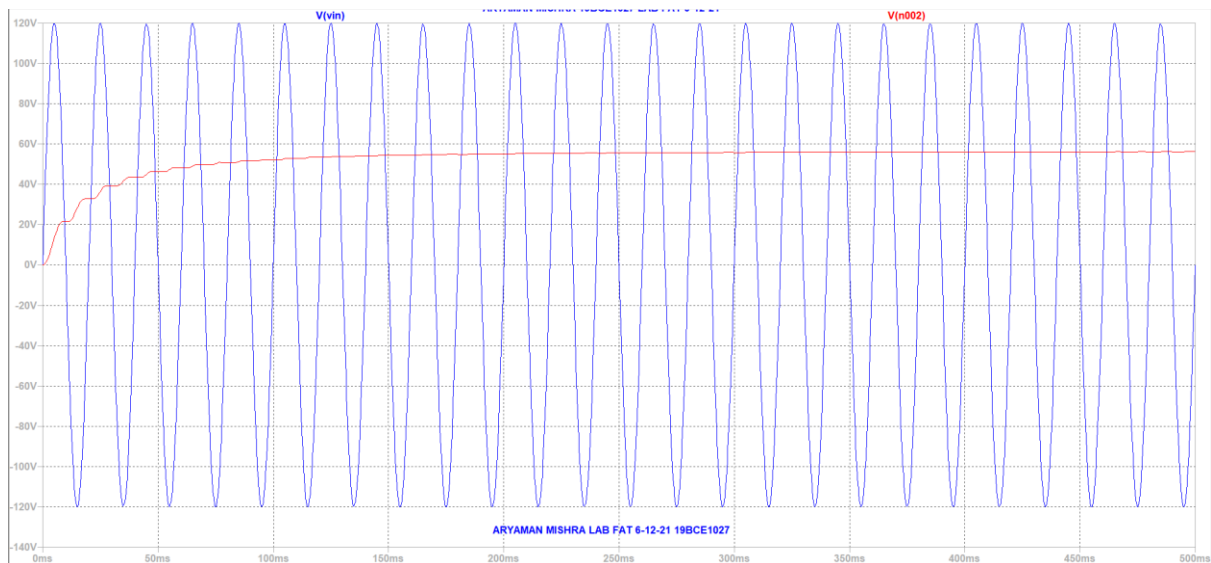**Taking voltage and number of turns only:**



## Taking inductance as factor:

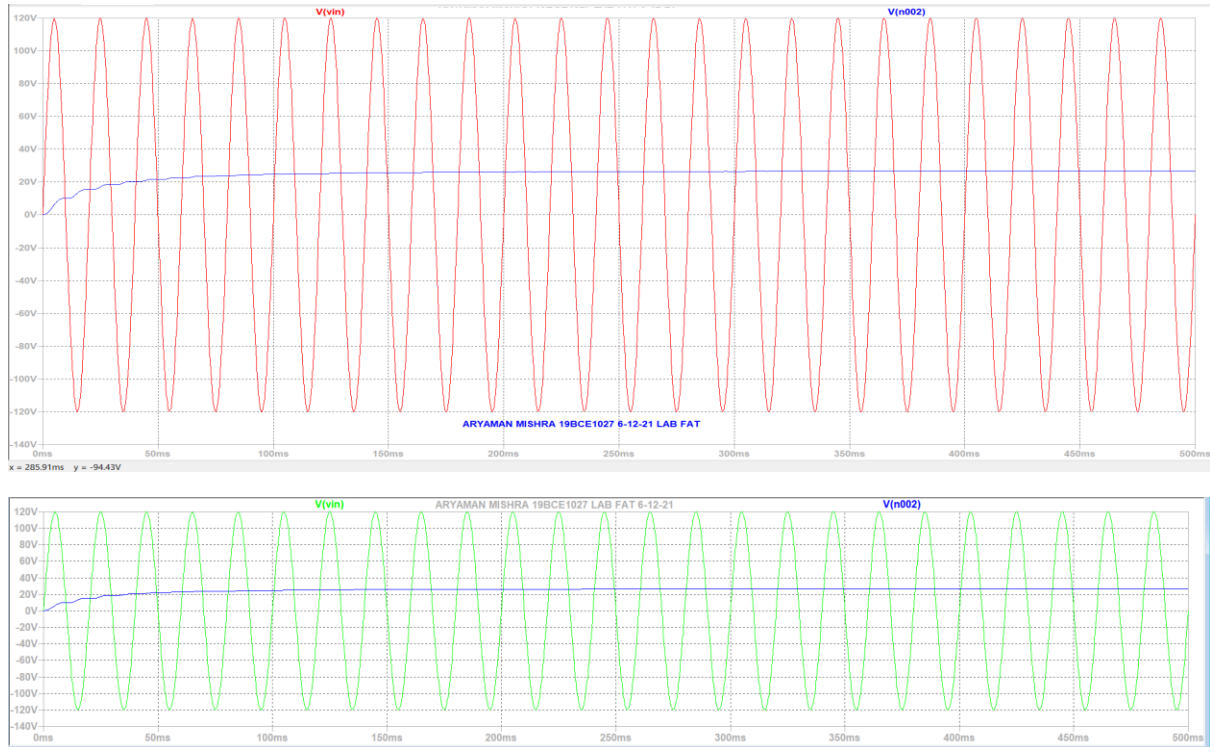

## Taking Voltage and Number of Turns:

V<sub>p</sub>:Input Voltage on Primary Coil

V<sub>s</sub>:Input Voltage on Secondary Coil

N<sub>s</sub>:Number of Turns on Secondary Coil

N<sub>p</sub>:Number of Turns on Primary Coil

Turn Ratio Formula:(V<sub>s</sub>/V<sub>p</sub>)=(N<sub>s</sub>/N<sub>p</sub>)

Turn Ratio=120/28.8=4.16

Therefore:Turn Ratio=4.16:1

## Taking Inductance as factor:

L<sub>1</sub>:L<sub>2</sub>=(v<sub>1</sub>\*v<sub>1</sub>)/(v<sub>2</sub>\*v<sub>2</sub>)

L<sub>1</sub>:L<sub>2</sub>=(120\*120)/(28.8\*28.8)=17.36:1

**Conclusion: On taking L<sub>1</sub>:L<sub>2</sub> as 17.36:1,the threshold voltage peaks at 28.8V.Thus experiment is successfully completed.**