

Date: 02/08/2021 Exp. 1 Study of Measuring, Testing, Power Supply Instruments and Bread Board



TASK 1

Aim: To simulate the circuits and find voltages across resistors and currents through the source and resistances.


Software/Hardware Components used: LTSpice, 3 Resistors, 1 Voltmeter, Ground, Wire

Expression:


$$\text{Voltage (V)} = \text{Current (I)} * \text{Resistance (R)}$$

Circuits and Plots:


Circuit 1

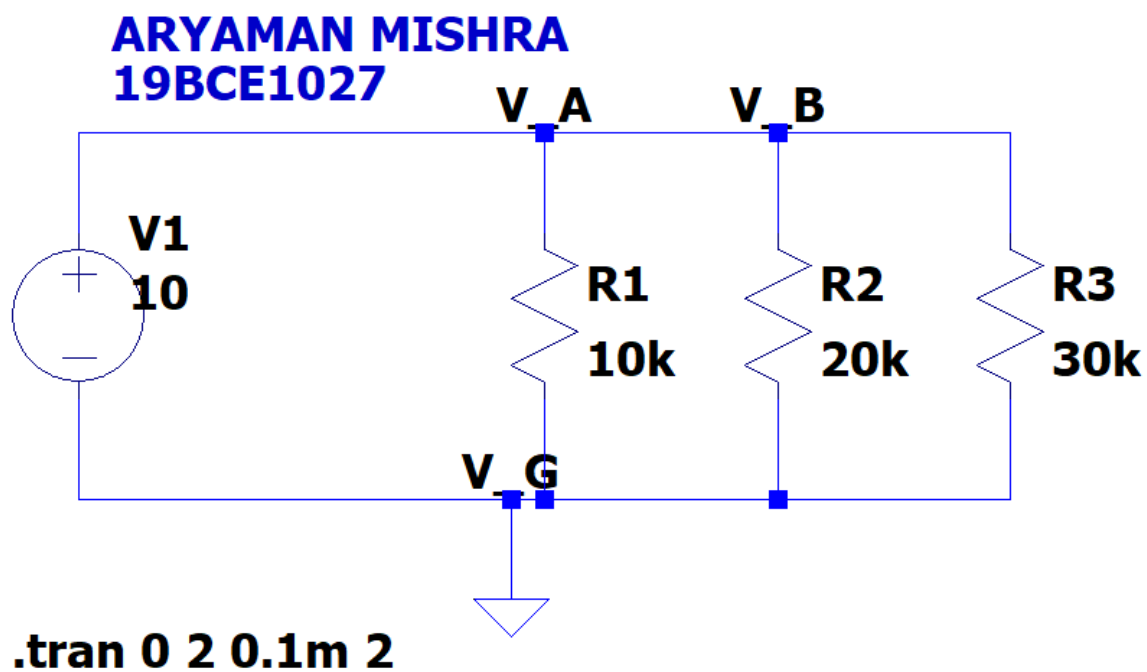


Plot 1

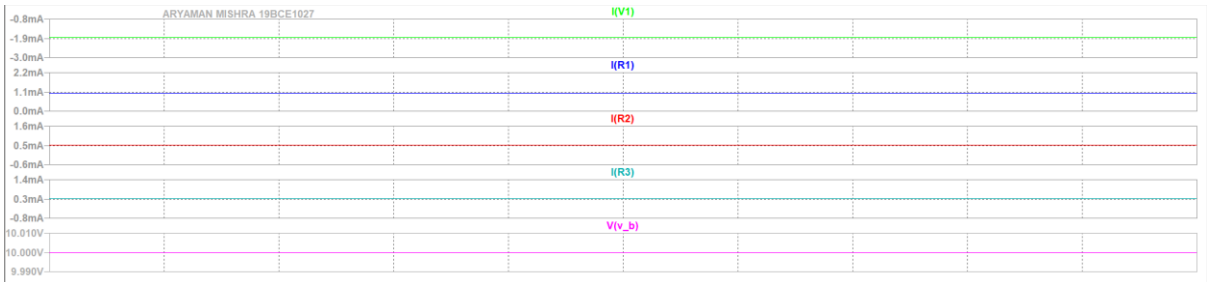

Circuit 2

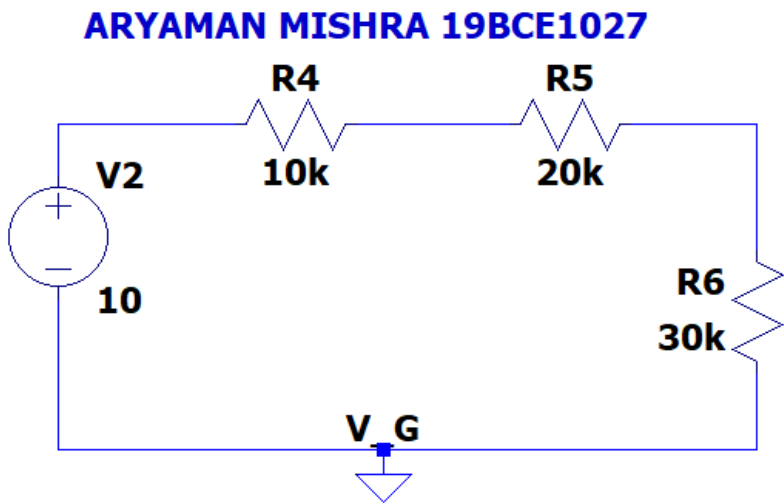

Plot 2

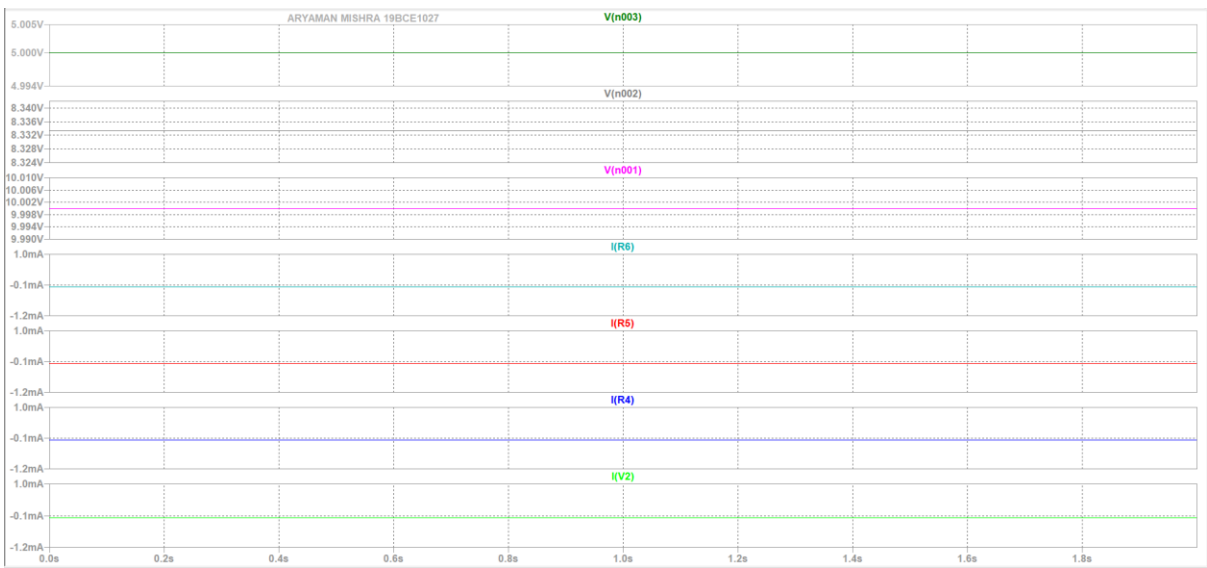

INPUTS AND OUTPUTS:**Inputs**

Components Used	Input Value
V1	10V
R1	10K Ohm
R2	20K Ohm
R3	30K Ohm

OUTPUTS (Circuit 1)

Node	Resultant Value
I(R1)	1mA
I(R2)	0.5mA
I(R3)	0.3mA
I(V1)	1.83mA
V(v_b) Through all resistors	10V

OUTPUTS (Circuit 2)

Node	Resultant Value
I(R1)	0.16mA
I(R2)	0.16mA
I(R3)	0.16mA
I(V1)	0.16mA
V(n001)	1.6V
V(n002)	3.3V
V(n003)	5V

Conclusion:Hence we successfully simulate the given circuits and find out the accurate voltage across the resistors and the current through the sources and resistors.

TASK 2

Aim: To find color code of resistors (4 band system)

Expression:

1st: 1st Digit

2nd : 2nd Digit

3rd : Multiplier

4th: Tolerance

	<u>Colour 1</u>	<u>Colour 2</u>	<u>Colour 3</u>	<u>Colour 4</u>
330k Ω with 5% tolerance	Orange	Orange	Yellow	Gold
470k Ω with 10% tolerance	Yellow	Violet	Yellow	Silver
66k Ω with 10% tolerance	Blue	Blue	Orange	Silver
3.2k Ω with 5% tolerance	Orange	Red	Red	Gold
540 Ω with 10% tolerance	Green	Yellow	Brown	Silver
27 Ω with 5% tolerance	Red	Violet	Black	Gold


TASK 3

Aim: To simulate low pass filter (Capacitance)


Software/Hardware Components used: LTSpice, 1Resistor, 1 Voltmeter, 1 Capacitor, Ground, Wire

Circuits and Plots:

Circuit

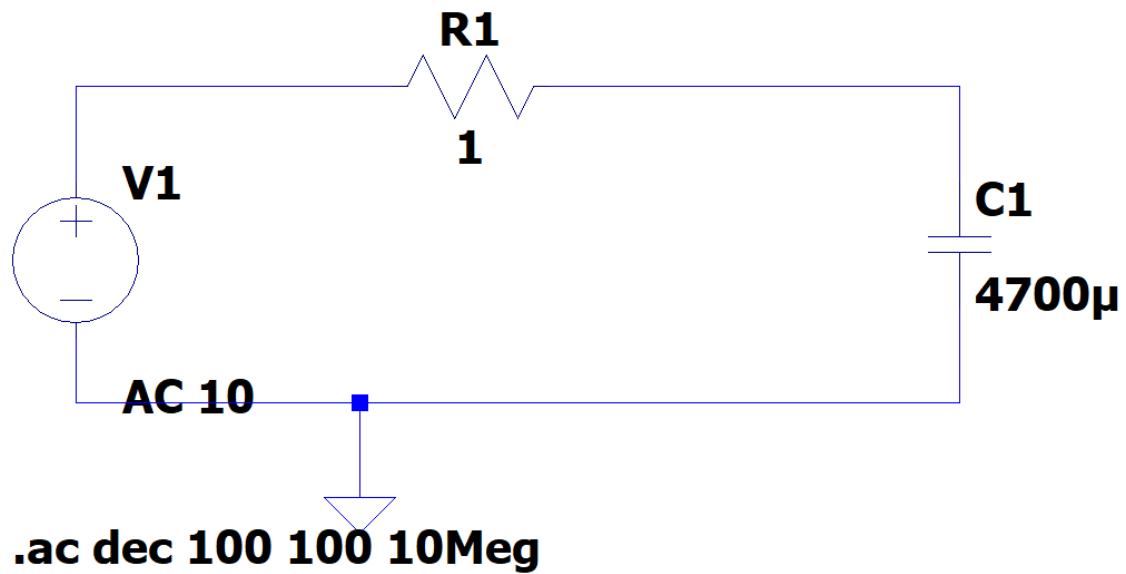ARYAMAN MISHRA 19BCE1027

Plot

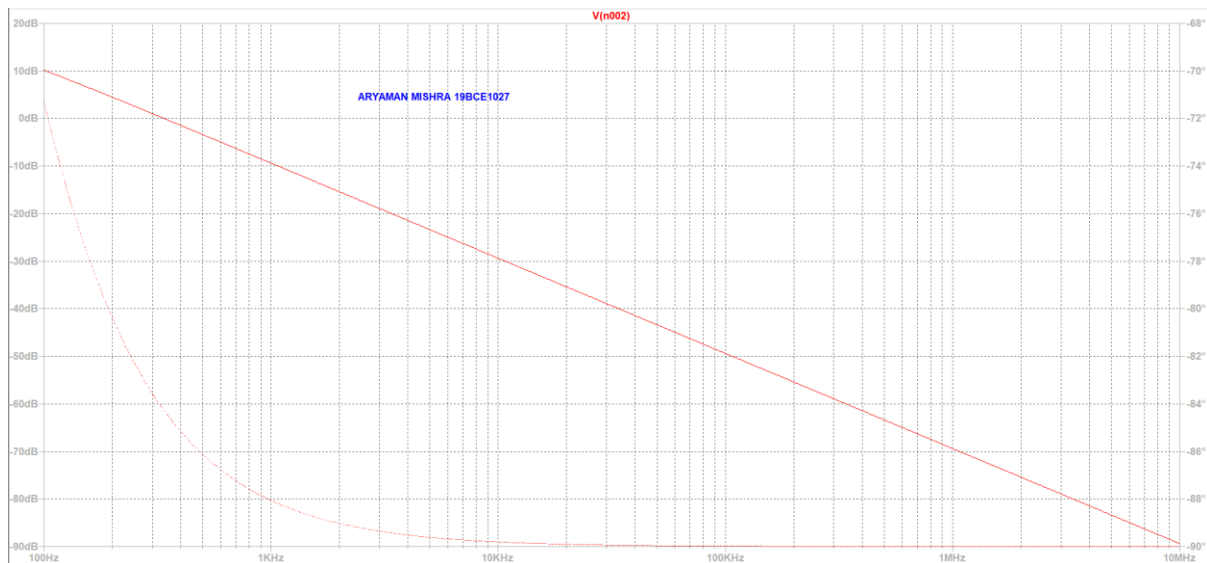

INPUTS AND OUTPUT:

INPUT

Components Used	Value
V1	AC Amplitude: 10 Type of Sweep: Decade Number of points per decade: 100 Start Frequency: 10

	Stop Frequency: 100 Meg
R1	1 Ohm
C1	4700 micrometer

OUTPUT

NODE	Value
V(n002)	20 to (-110) dB, 10 Hz to 100MHz

Conclusion: Hence we are able to simulate the circuit to show low pass filter in a capacitor.

TASK 4


Aim: To simulate low pass filter (Inductance)

Software/Hardware Components used: LTSpice, 1 Resistor, 1 Voltmeter, 1 Inductor, Ground, Wire


Circuits and Plots:

Circuit

ARYAMAN MISHRA 19BCE1027

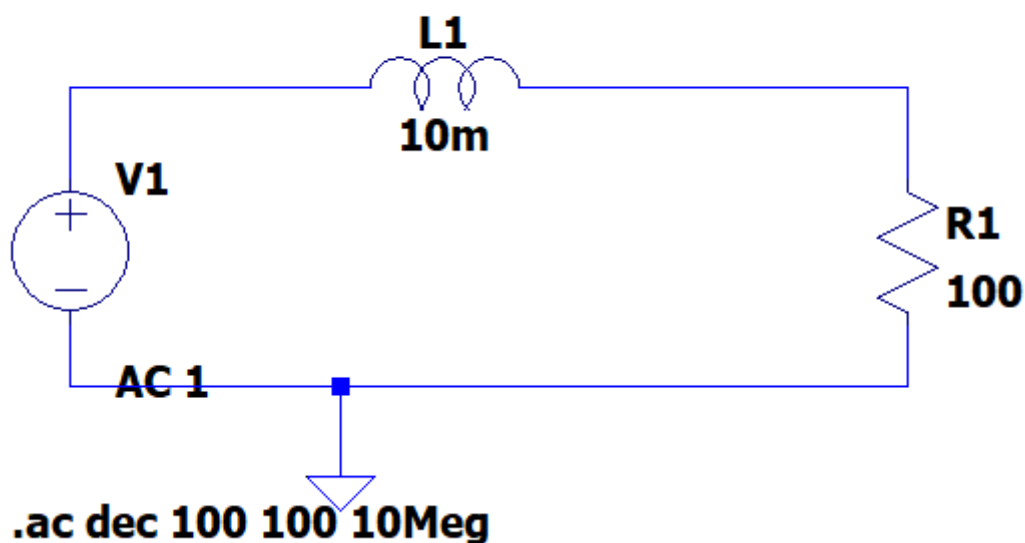

Plot

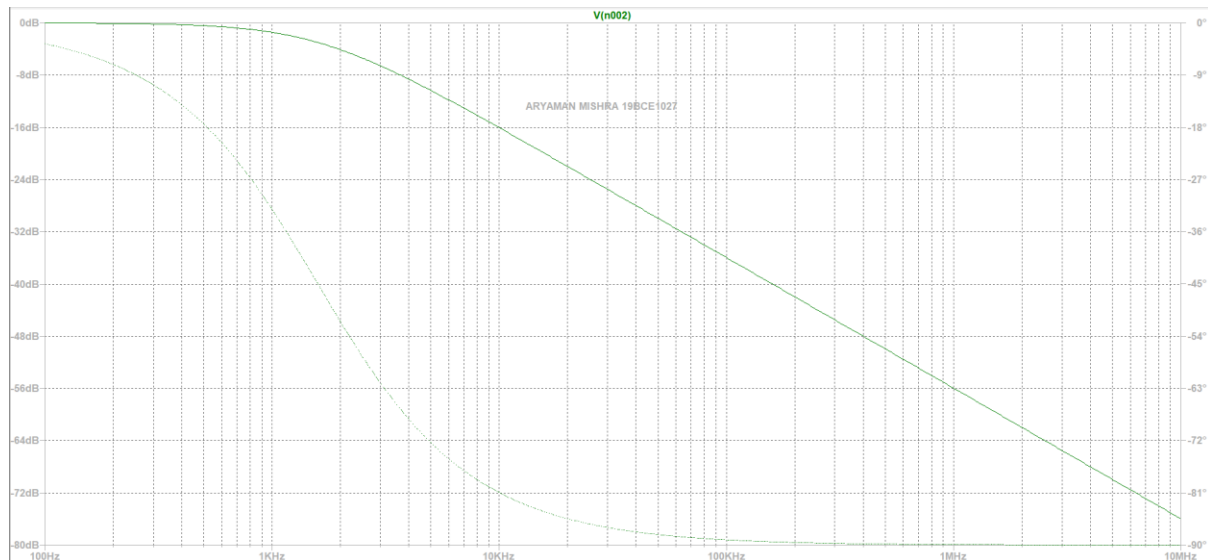

INPUTS AND OUTPUT:

INPUT

Components Used	Value
V1	AC Amplitude: 1 Type of Sweep: Decade Number of points per decade: 100 Start Frequency: 100 Stop Frequency: 10 Meg
R1	100 Ohm
L1	10 m

OUTPUT

NODE	Value
V(n002)	0 to (-80) dB, 100Hz to 10MHz

Conclusion: Hence we are able to simulate the circuit to show low pass filter in an inductor.

TASK 5

Aim: To find the total resistance of the circuit seen from the source. (Through formula and with V/I).

Circuit and Expressions:

Task 5:

Method 1

Since R_1, R_2, R_3 are connected in parallel

$$\frac{1}{R_{net}} = \frac{1}{10(10^3)} + \frac{1}{20(10^3)} + \frac{1}{30(10^3)}$$

$$\frac{1}{R_{net}} = \frac{6 + 3 + 2}{60 \times 10^3}$$

$$R_{net} = \frac{60 \times 10^3}{11} = 5.45 \times 10^3 \Omega = \boxed{5.45 \text{ K}\Omega}$$

Method 2

$$\frac{1}{R_{net}} = \left(\frac{V}{I_1} \right) + \left(\frac{V}{I_2} \right) + \left(\frac{V}{I_3} \right)$$

$$I_1 = \frac{V}{R_1} = \frac{10}{10 \times 10^3} = 10^{-3} \text{ A}$$

$$I_2 = \frac{V}{R_2} = \frac{10}{20 \times 10^3} = 0.5 \times 10^{-3} \text{ A}$$


$$I_3 = \frac{V}{R_3} = \frac{10}{30 \times 10^3} = 0.3 \times 10^{-3} \text{ A}$$

$$\therefore \frac{1}{R_{net}} = \left(\frac{1/10}{10^{-3}} \right) + \left(\frac{1/10}{0.5 \times 10^{-3}} \right) + \left(\frac{1/10}{0.3 \times 10^{-3}} \right)$$

$$= (1/10^4) + (1/2 \times 10^4) + (1/3.3 \times 10^4)$$

$$\frac{1}{R_{net}} = 10^{-4} (1 + 0.5 + 0.3)$$

$$R_{net} = \frac{1}{1.8} \times 10^4 = 0.5 \times 10^4 = \boxed{5.5 \text{ K}\Omega}$$

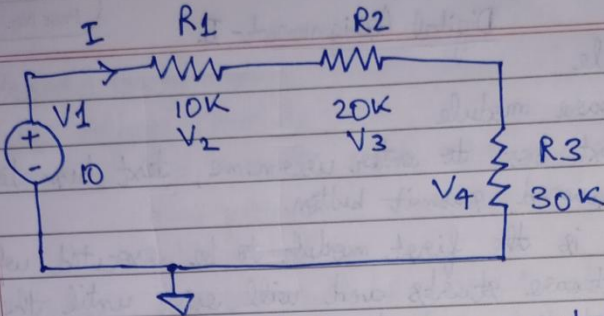

Method 1

Since R_1, R_2, R_3 are connected in series

$$R_{net} = 10(10^3) + 20(10^3) + 30(10^3) = 60 \times 10^3 \Omega$$

$$= \boxed{60 \text{ K}\Omega}$$

Method 2

$$I = \frac{V}{R_{net}} = \frac{10}{60 \times 10^3} = 0.1\bar{6} \times 10^{-3} \text{ A}$$

Voltage drops

$$V_2 = IR_1 = 0.1\bar{6} \times 10^{-3} \times (10^3)10 = 1.6 \text{ V}$$

$$V_3 = IR_2 = 0.1\bar{6} \times 10^{-3} \times (10^3)20 = 3.3 \text{ V}$$

$$V_4 = IR_3 = 0.1\bar{6} \times 10^{-3} \times (10^3)30 = 4.9 \text{ V}$$

Hence,

$$R_{net} = \frac{V_2 + V_3 + V_4}{I}$$

$$= \frac{1.6 + 3.3 + 4.9}{0.1\bar{6} \times 10^{-3}} \approx 60 \times 10^3 \Omega$$

$$= \boxed{60 \text{ K}\Omega}$$

Hence $R_{net} = 60 \text{ K}\Omega$


Conclusion: Hence the net resistance of circuit 1 is 5.5 K ohm and circuit 2 is 60 K ohm.

TASK 6

Aim: To find total capacitance of the circuit.

Circuit and Expressions:

Task 6:

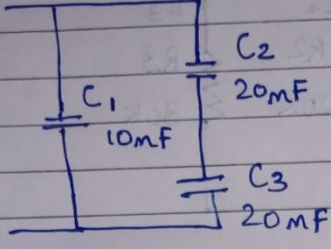

Since C_2, C_3 are in series, we add their reciprocals with C_1 which is in parallel.

$$C_{eqv} = C_1 + \frac{C_2 \times C_3}{C_2 + C_3}$$

$$= 10 + \frac{20 \times 20}{20 + 20}$$

$$= 10 + \frac{400}{40} = 10 + 10 = 20 \text{ mF}$$

$\therefore C_{eqv} = 20 \text{ mF}$

Conclusion: Hence the net capacitance of circuit is 20nF.

TASK 7

Aim: To find total inductance of the circuit.

Circuit and Expressions:

7)

L_2 and L_3 inductors are in series
 therefore total inductance $L' = L_2 + L_3$
 $= 4\text{mH} + 8\text{mH}$
 $= 12\text{mH}$

L' and L_1 are in parallel
 Total inductance $L'' = \frac{1}{\frac{1}{L'} + \frac{1}{L_1}}$
 $= \frac{1}{\frac{1}{10} + \frac{1}{12}} \text{mH}$
 $= \frac{1}{\frac{22}{120}} = \frac{120}{22} \text{mH}$
 $= 5.4545\text{mH}$

Conclusion: The net inductance of the circuit is 5.45mH.

TASK 8

Aim: To find the capacitance values with codes.

Circuit and Expressions:

1) 492 = $49 \times 10^2 = 4.9\text{nF}$
 2) 103 = $10 \times 10^3 = 10\text{nF}$
 3) 352 = $35 \times 10^2 = 3.5\text{nF}$
 4) 104 = $10 \times 10^4 = 100\text{nF}$
 5) 285 = $28 \times 10^5 = 2.8\text{μF}$
 6) 681 = $68 \times 10 = 680\text{pF}$